

# Chapter 28

28-1

## Direct Current Circuits

### DC circuits

I'm going to go a bit out of order from the text — I just can't bear it's order

§28.3

### Kirchhoff's Laws (or rules)

— they are really ~~so~~ easy to understand and apply (at least in simple cases)

— they apply to time invariant direct currents.  
↳ but they also apply when current is varying or long

28-2

not too fast  
↳ but "too fast"  
is really, ~~not~~ really  
fast.

→ they work ~~even up to~~  
for AC (alternating current)  
even up to radio frequencies  
( $\sim 10^6$  Hz or 1 MHz)!  
(GrEM-292)

1) Kirchhoff Voltage Law (or loop law)

① The changes in electric  
potential around any  
closed path ~~is~~ sum to

zero ~~of the circuit~~ (in the physical  
or by any other path)

— or the sum of potential rises  
and drops is zero.

$$\sum \Delta V_i = 0$$

- this law is just a manifestation of the fact that the electric force of a static charge ~~(or even quasi static)~~ distribution is a conservative force. (Gr EM-293)  
130-216

$$V_{\text{closed loop}} = -\oint \underline{E} \cdot d\underline{s} = 0$$

Believe to or not in DC electric circuit (and in AC ones too viewed at an instant in time) there is ~~an~~ a distribution of ~~net charge~~ +ve and -ve charge. The sum of it

28-4)

it all is usually zero but the charge is separated.

— where this separated static array of charge is exactly is in general hard to say.

→ Much must be in the source of electric energy

→ the emf device (electromotive force = emf) — we'll describe in a bit)

like a battery with +ve & -ve

~~terminals~~


terminals

— probably a lot of charge is on surfaces of terminals.

→ but maybe some inside too

The emf is the thing that separates the static charges and keeps them separated and drives the current.

— we'll come to it.

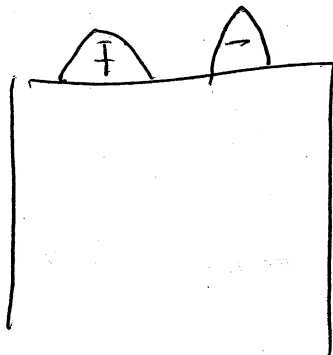


28-5

- but there is also some in the wires and other outer parts

Not a lot, but needed to make current go around bends (e.g.)

(BO-216)

the "guiding charge"

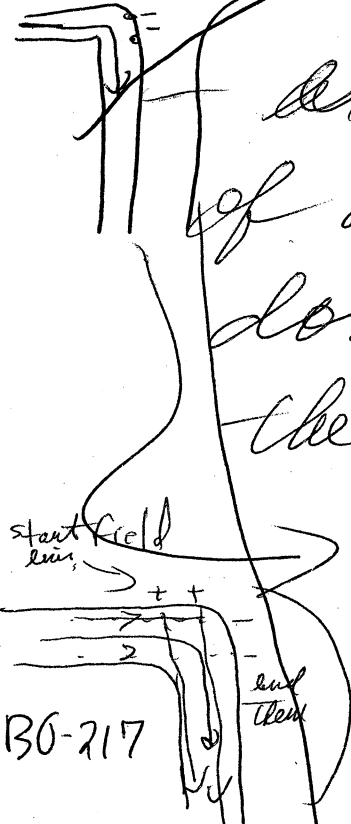

except at highest level of detailed understanding, you don't know where exactly the <sup>separated static</sup> charge is in detail

and you don't need to know for most circuit calculations.

Note the charge in the current itself is not part of this separated charge.

the current is flowing (of negative electrons)

E-field outside wires in general are complex but usually you don't need to know anything about

28-6)

against a background  
of positive charge.

~~the~~ - in the interior  
of the conductors  
the net charge density  
is zero. (Ohanian-260)

- the separated charge is  
on the surfaces of the conductors.

- We proved this for electrostatic  
cases.

→ It is also true for ~~time~~  
time-independent flow

cases  
+ cases where the flow can  
be so approximated (i.e., AC  
cases)  
But unlike electrostatic  
cases  $\underline{E} \neq 0$  inside conductor.

- it is just a bit beyond our scope to prove it here

(but it can be done Ohm's law - 260)

2) Kirchhoff's current law (or the junction law)

- in steady flow or node law


there is no build up of charge anywhere (not counting the already established separated charge)

- Thus all the current flowing into a junction must be matched by current flowing out.

- in equation form  $\sum_i I_i = 0$  for any junction.

28-8

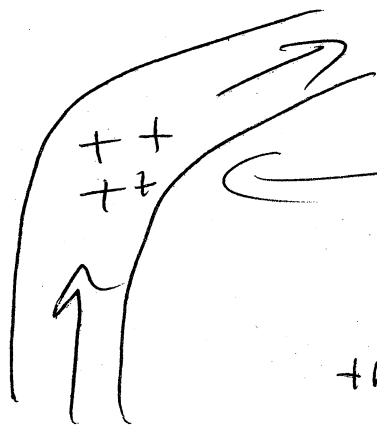What keeps ~~the~~ any  
net charge from piling  
up — beyond what  
it takes to establish  
the DC current (the  
separated electrostatic  
distribution.)



say there was  
a build up of  
+ve charge here  
— it would <sup>tend</sup> repel  
more +ve charge  
~~from~~ entering  
and tend push out  
more charge the other



way.

28-9

A steady state situation with steady inflows and outflows of energy is self-regulating.  
(amazingly so)



We'll show how to <sup>soon</sup> use Kirchoff's laws but let's return to emf's

## § 28.1 Electromotive force emf

— a misnomer. It's not a force. It's integral of a force per unit charge over a ~~distance~~ <sup>line</sup> — or work per unit charge

a line integral

28-10

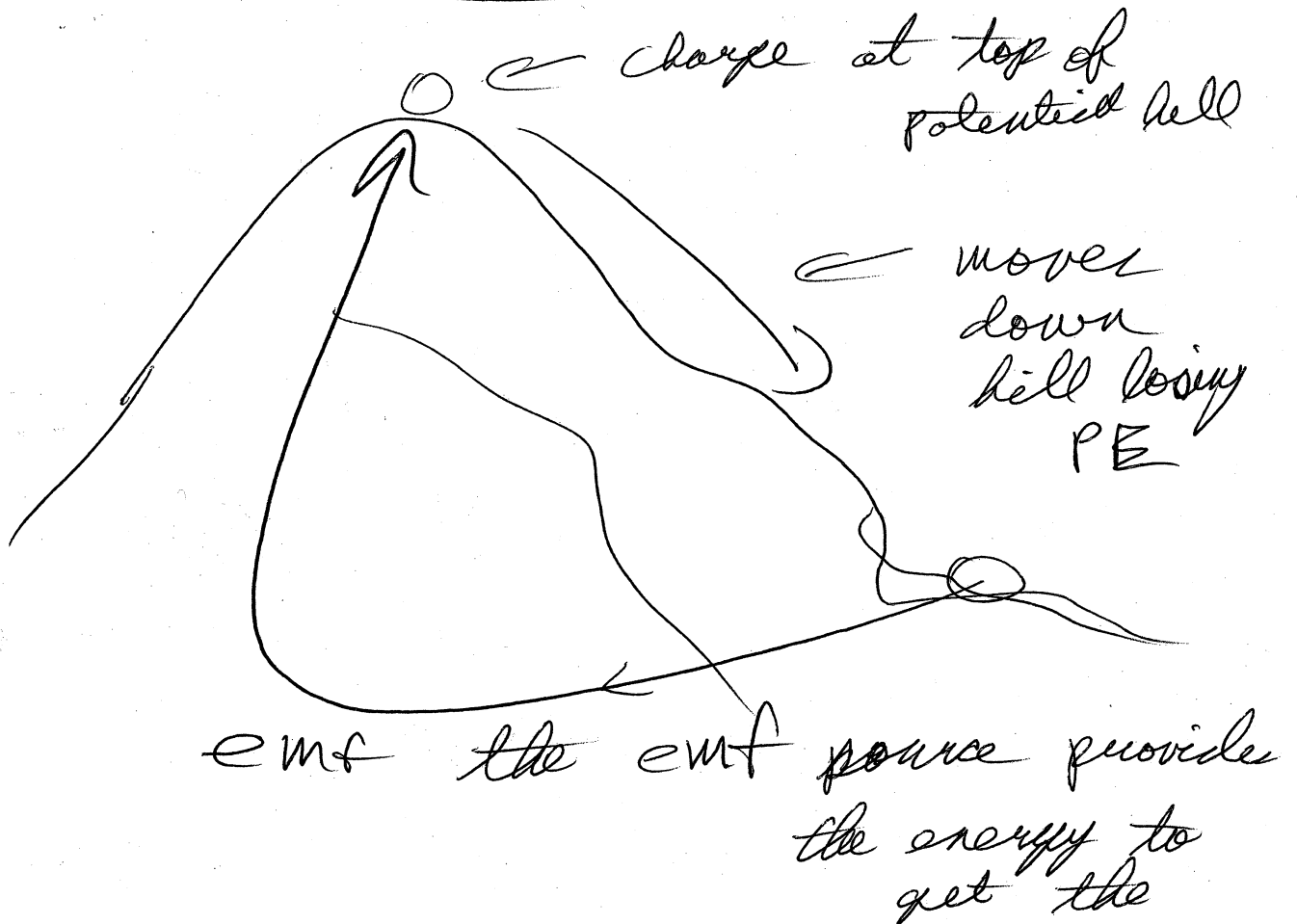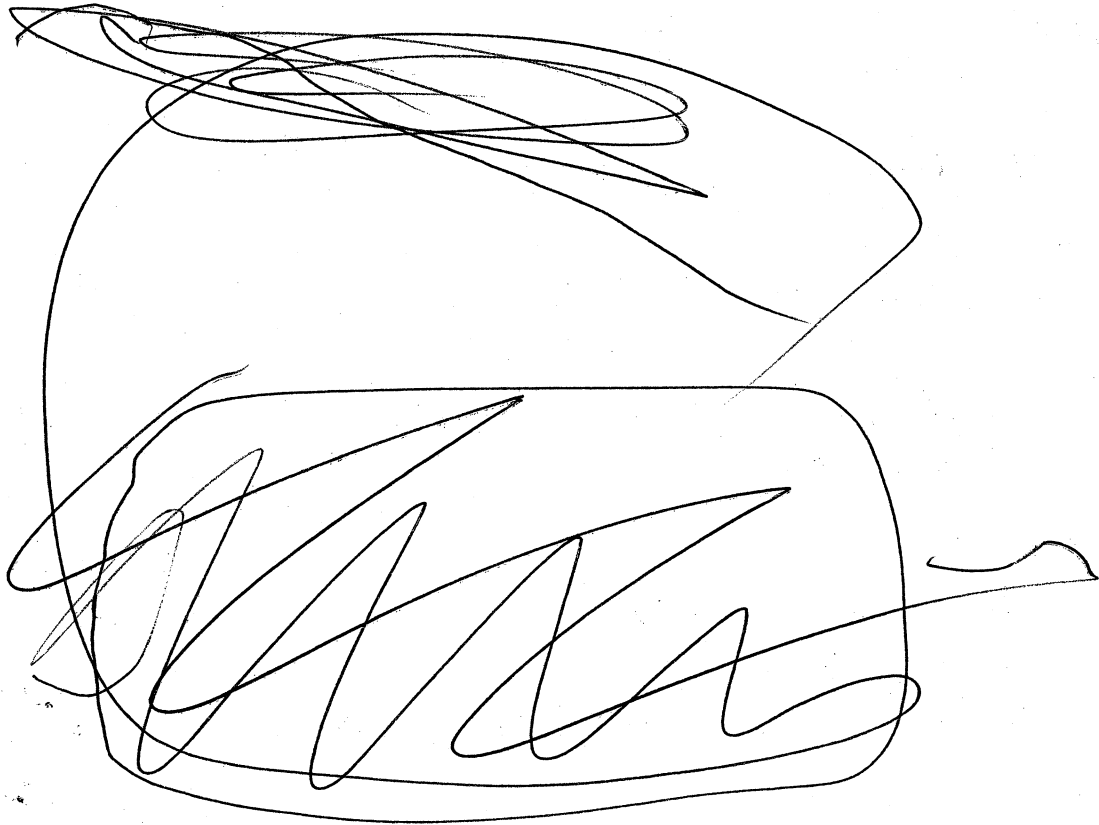


charge back up the hill.

28-11

We'll just consider a generic emf (though a chemical battery is the obvious

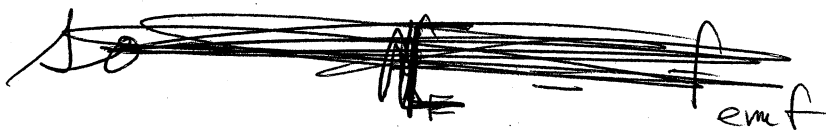In side in a steady state (which ~~could also~~ <sup>could also be the</sup> DC example, the charge is not accelerating <sup>no flow case</sup>)



for an ideal emf with no internal resistance,

$$\text{So } \underline{f_{emf}} = - \underline{E}_{electrostatic}$$

↑  
counteracting emf force pushing up the potential hill

↑  
electrostatic force per unit charge pushing charge down the potential hill.

Now we do a path integral through the emf device.

28-12

EMF  $\mathcal{E}$  = Potential

are ideally  
even though the  
two are not the same

(GrEM-293)

thing, but may look  
sort of loosely  
imply they are

$$\mathcal{E} \equiv \int_a^b \vec{f}_s \cdot d\vec{s} = - \int_a^b \vec{E} \cdot d\vec{s}$$

defined to  
be emf


$$= V_{ab} = V_{-ve \text{ to } +ve \text{ terminals}}$$

the work  
done pushing  
the charge  
up the PE  
hill.

the potential change  
from a to b.

the  
+ve &  
negative  
separated  
charge must be  
located

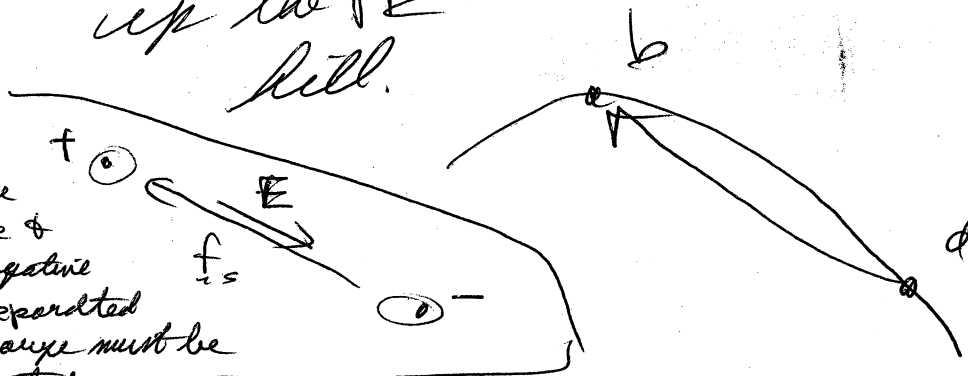where  
they  
can  
counter  
the  
emf  
force  $f_s$   
all along  
but where that  
is maybe  
a complex  
thing to  
know.



An ideal  
emf maintains  
potential no  
matter what current  
flows.

In a static case  
the emf builds  
up the charge  
separation causing

Actually real emf devices  
have internal resistance

the potential  
until  
 $\mathcal{E} = V_{ab}$   
and then  
the static  
case  
is  
established

So some of the energy  
coming from the emf supply  
goes into doing work against  
the resistance force

and gets lost as waste heat.

28-13

— usually one can treat this loss as due to an ohmic resistor of resistance  $r$  say. — an internal resistance

In this case,  $I r$  is the energy per charge lost to resistance (which get from Ohm's law).

$I r = \int_a^b f_{resistance} dx$   
still don't have perfect argument.

on  $\mathcal{E} = V_{ab} + I r$  more realistically,  
more physically  $\mathcal{E} - I r = V_{ab}$

What actually provides emf?

— well there are several sources

Examples

1 — Chemical batteries

we'll just mention, not go into their actual <sup>CGrEM -292 -293</sup> specifications

→ here a chemical force pushes the charge.

28-14)

this chemical force  
is really an  
electromagnetic force  
too — but not  
due to macroscopic  
 $\mathbb{E}$ -fields.

2) Photons ejecting electrons  
in photovoltaic cells

3) In a Van de Graaf generator  
(used as an emf), one <sup>literally</sup> loads  
electrons on a conveyor  
belt to transport them  
(~~ST~~ ST-710)

4) In ~~a non-DC~~ <sup>the usual AC case</sup> ~~case~~ (ST-880)

One uses an electric generator  
to create an induced electric  
field through Faraday's Law (or <sup>induced</sup> ~~Maxwell's~~ <sup>Maxwell's</sup> Law)

↳ this is not an electrostatic electric  
field and this induced field pushes  
the charge as the potential  $\Delta \phi$


There are others.

I don't really (or EM-293) pretend to know much about their operation.

Let us do ~~some~~ some examples

Ex 1

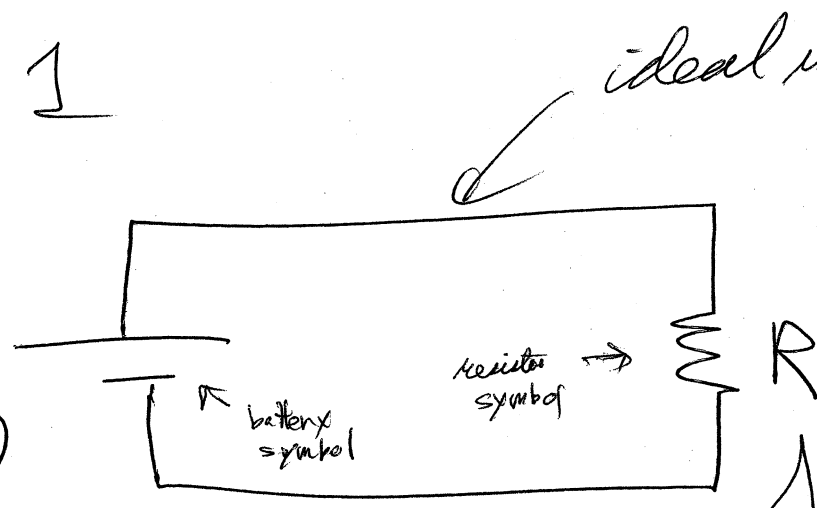$\mathcal{E}$   
an ideal battery  
so the potential here across it is  $\mathcal{E}$



ideal resistorless wires

— current flows with  $\mathcal{E} = \phi$  and so the ~~wire~~ wire segments are equipotentials

resistor R.

— a potential drop across it to ~~push~~ give enough  $\mathcal{E}$ -field ~~the charge does~~ to cancel the resistive forces.

~~$V_R = IR$~~   $V_R = IR$  by Ohm's law.

28-16

There is only one loop and so only one constant current  $I$  by Kirchhoff current law.

The ~~potential~~ voltage law tells us  $\sum V_i = 0$

$$\rightarrow \text{here } \sum V_i = \mathcal{E} - V_R = 0$$

$$\text{or } \mathcal{E} = IR$$

$\therefore$  Solving for  $I$

$$\text{we get } I = \frac{\mathcal{E}}{R}$$

$$\text{for } \mathcal{E} = 1\text{V} \text{ \& } R = 1\Omega$$

$$I = 1\text{A}$$



28-17

$$P_{\text{input from emf}} = I \mathcal{E} = 1 \text{ W}$$


$$P_{\text{output as heat in resistor}} = I V_R = I^2 R = \frac{\mathcal{E}^2}{R} = I \mathcal{E} = 1 \text{ W}$$

Note if  $R \rightarrow 0$   
~~out~~  $I \rightarrow \infty$   
 $P_{\text{out}} \rightarrow \infty$   
 and one has a short circuit

$\mathcal{E} \times 2$  ( $\mathcal{E} \times 28.2$  in text)

Load Matching.

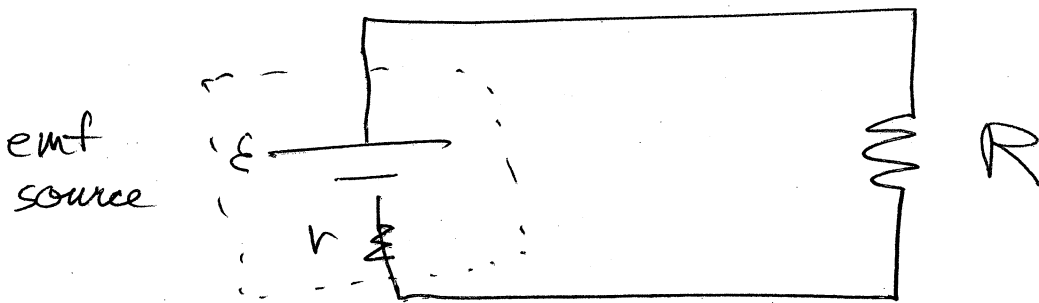Almost the same case, but now our emf is not ideal, but has internal resistance  $r$



This when your wires and insulation melt down and electrical fires start. Fuses and circuit breakers cut the

Potential rise

$$\mathcal{E} - Ir = IR$$

$$\mathcal{E} = I(R + r)$$

$$I = \frac{\mathcal{E}}{R + r}$$

Potential drops.

Current off it gets too high.

2A-18

$$P_{\text{input}} = I \mathcal{E} = \frac{\mathcal{E}^2}{R+r}$$

$$P_{\text{output in resistor}} = I V_R = I^2 R$$
$$= \frac{\mathcal{E}^2 R}{(R+r)^2}$$


Not equal in this case since some power is being up the internal resistance

The  $P_{\text{out}}$  actually has an interesting behavior as a function of  $R$ .

If  $R = 0$ , no resistance no power out.

But if  $R = \infty$ ,  $I = 0$  and no power out.

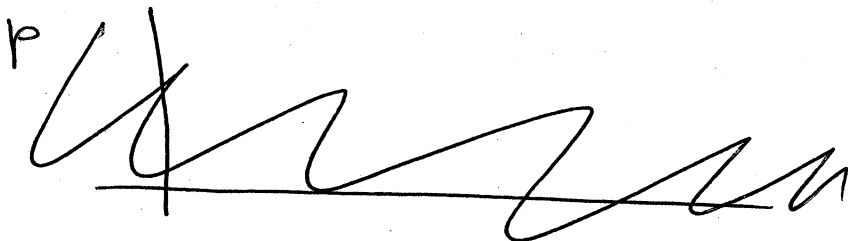So  $P_{\text{out}}$  must have a maximum (at least one) as a function of  $R$ .



28-19

$$P_{out} = \frac{\epsilon^2}{v^2} \frac{R}{(1 + \frac{R}{v})^2}$$

$$\approx \frac{\epsilon^2}{v^2} R \text{ for } \frac{R}{v} \ll 1$$

so rises linearly with R for R small.

$$\frac{1}{(1 + \frac{R}{v})^2} \approx 1 - 2\frac{R}{v}$$


by the Taylor ~~geometric~~ series



$$P_{out} = \frac{\epsilon^2}{R(1 + \frac{v}{R})^2}$$

$$\approx \frac{\epsilon^2}{R} \text{ for } \frac{v}{R} \ll 1$$

falls off as 1/R

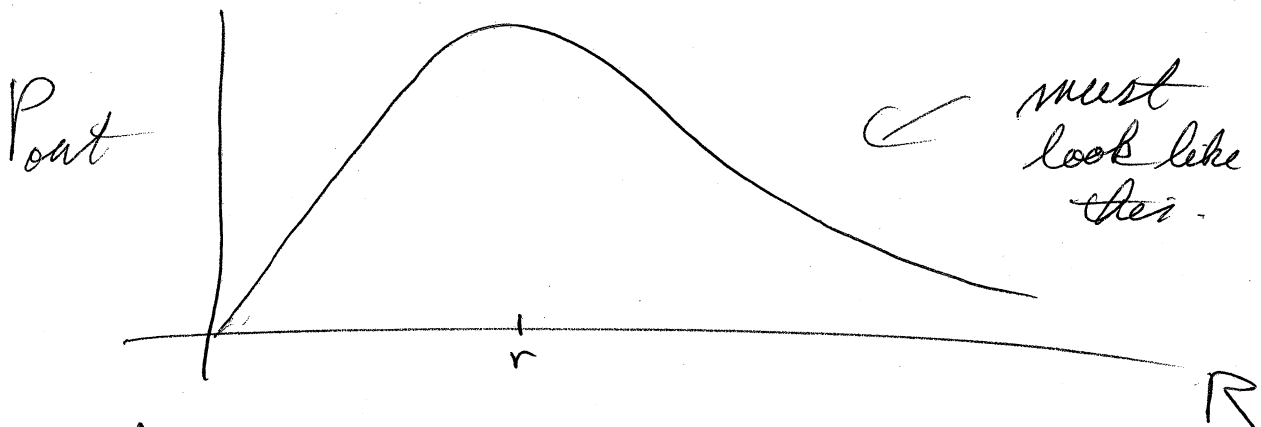

$$\frac{dP_{out}}{dR} = \epsilon^2 \left[ \frac{1}{(R+v)^2} - \frac{2R}{(R+v)^3} \right] = 0$$

for maximum

$$R + v - 2R = 0$$

or  $R = v$

28-20

So the maximum output power is for  $R = r$  external resistance (the load) matched to internal resistance.

— Hence the term  
load matching  
or resistance matching

$$P_{\text{out max}}^{(R=r)} = \frac{\mathcal{E}^2 r}{(2r)^2} = \frac{\mathcal{E}^2}{4r}$$

$$P_{\text{input}}^{(R=r)} = \frac{\mathcal{E}^2}{2r}$$

So the maximum power you can get is  $\frac{1}{2} P_{\text{input}}$ . So half is wasted in the internal resistance.

But there are a few other twists in the story.

$$P_{out} = \frac{\epsilon^2 R}{(R+r)^2} \quad \text{recall}$$

Clearly  $P_{out} \uparrow$  if  $r \downarrow$  ~~in~~ in all cases,

and so for  $r = 0$


$$P_{out}^{(r=0)} = \frac{\epsilon^2}{R}$$

which is  $P_{input}(r=0) = \frac{\epsilon^2}{R}$

In this case  $P_{out} = P_{input}$ .

$P_{output}$

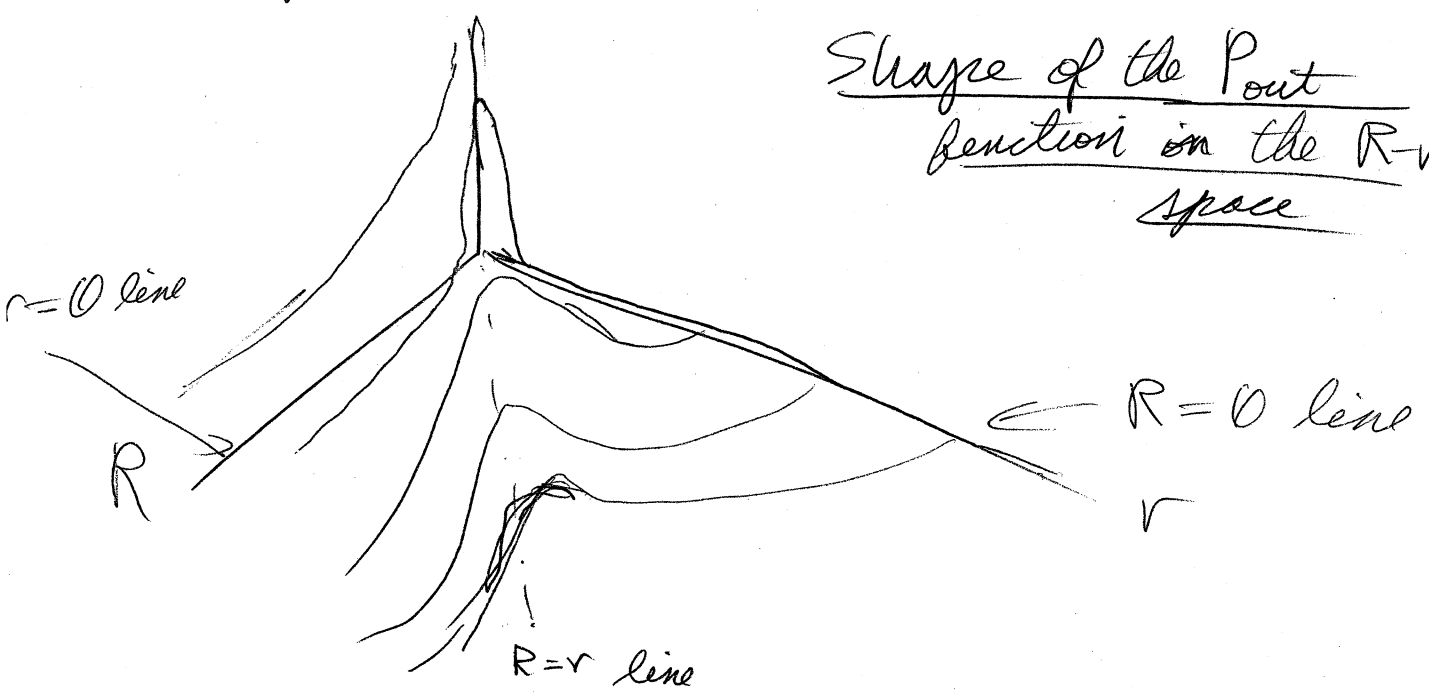Shape of the  $P_{out}$  function in the  $R-r$  space



28-22

The finiteness is because of the infinity

$$\text{for } \lim_{R \rightarrow 0} P_{\text{out}}(R=0) = \infty$$

$$\text{and } \lim_{r \rightarrow 0} P_{\text{out}}(R=0) = 0$$

The  $R = r = 0$  origin point is part of the infinity because of the infinity there. — a singularity where the function is undefined.

But this is just a mathematical conundrum.

Another aspect is total energy output.

$$E_{\text{input}} = P_{\text{input}} \Delta t$$

Let's hold this constant

$$\text{or } \Delta t = \frac{E_{\text{input}}}{P_{\text{input}}}$$

$$\begin{aligned}
\text{Now } E_{\text{out}} &= P_{\text{out}} \Delta t \\
&= \frac{P_{\text{out}}}{P_{\text{input}}} E_{\text{input}} \\
&= \frac{\frac{\epsilon^2 R}{(R+r)^2}}{\frac{\epsilon^2}{(R+r)}} E_{\text{input}} \\
&= \frac{R}{R+r} E_{\text{input}}
\end{aligned}$$

(see p. 28-18)

Then we get all energy if  $R \rightarrow \infty$  or  $r = 0$

Both conditions are a bit impossible.

But note  $P_{\text{out}} = \frac{\epsilon^2 R}{(R+r)^2}$ ,  $P_{\text{input}} = \frac{\epsilon^2}{R+r}$

both ~~goes~~ go to zero as  $R \rightarrow \infty$ .  
 So you get all the energy for infinite  $R$ , but it takes you infinite time since

28-24


your power is  
zero.

So there is a  
trade off between  
high power and not  
wasting any energy.

## § 28.2 Resistors in Series Parallel ~~and~~

Nothing to these with  
Kirchhoff's laws in hand.

Series  $I \longrightarrow$

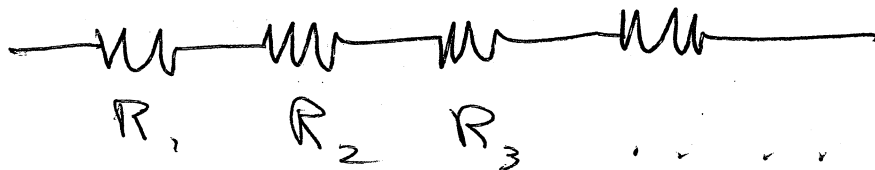



$$V = \sum_i V_i$$

↑  
drop across  
all

↑  
drop across the  $i$ th  
one of potential

but by Ohm's law

$$V_i = I R_i$$



Define

$$R_{eq} = \frac{V}{I}$$

Kirchoff's law  
tells us the same  
current  $I$  in all resistors.  
— no ~~bran~~ junctions  
or nodes.


$$\text{Then } I R_{eq} = \sum_i I R_i$$

$$\text{or } R_{eq} = \sum_i R_i$$

$R_{eq} \geq R_{max}$  of course.

28-26

# In Parallel

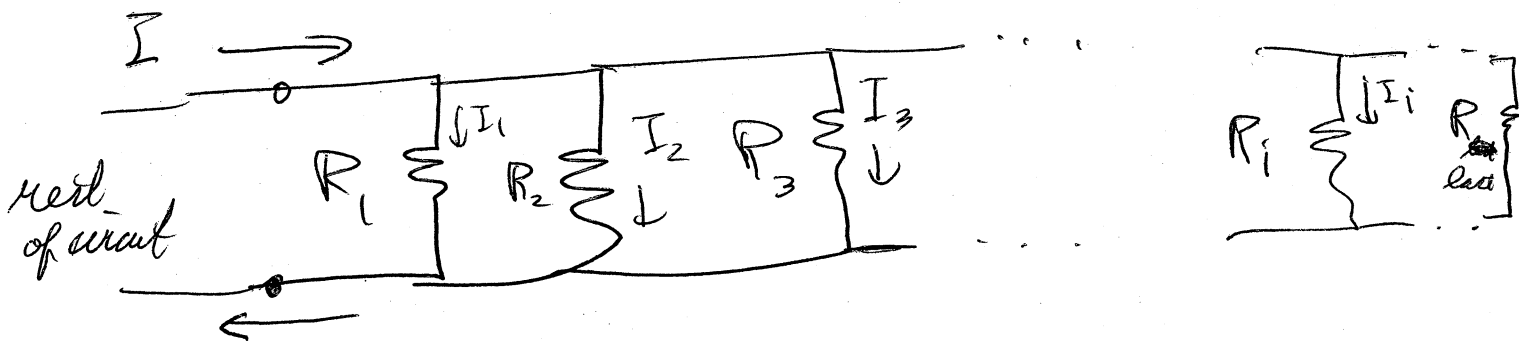

Ideal wires have no resistance

~~So the potential drop across~~

$$\text{So } V_{\text{rest of circuit}} + (-V_i) = 0$$

↑  
drop and rises

↑  
same for all

$V_i$   
- by choice  
 $V_i > 0$   
although a drop.

Current ?

By Kirchoff's current law

Let  $V = V_i$

$$I = \sum_i I_i$$

28-27

Now use Ohm's law  $V = I_i R_i$

and define  $R_{eq} = \frac{V}{I}$

$$\therefore \frac{V}{R_{eq}} = \sum_i \frac{V}{R_i}$$

or  $\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}$  is the rule

implies  $\frac{1}{R_{eq}} \geq \text{Max} \left( \frac{1}{R_i} \right)$

or  $R_{eq} \leq R_i$

So the more resistors one  
put in parallel the smaller  
the overall equivalent  
resistance.

28-28

Makes sense — there are more channels for current to flow thru.

A generalization of this situation is when you put too many devices on household ~~circuit~~ outlet

— They must go in parallel

since they are all designed to use AC with ~~AC~~ RMS voltage 120V

Root mean square  
— we'll discuss  
in Ch. 33

They may not all be resistors,

28-29

but they all  
make the ~~generalize~~  
effective resistance go  
down.

$$I = \frac{V}{R_{\text{eff}}}$$

— Thus the current  
goes up in the outlet

→ if it goes to high,  
then the wires in the wall  
could melt/burn

→ so the circuit breaker  
will break circuit.

It's not lack of power

— a whole power grid (or some  
big fraction) stands behind the outlet —

it's just the household wiring  
can't take it.

28-30

## Special Cases

Ex 1

all in parallel resistors  
have same resistance  
 $R$ . There are  $N$   
of them

In this case

$$\frac{1}{R_{eq}} = \sum_i \frac{1}{R}$$
$$= \frac{N}{R}$$

or  $R_{eq} = \frac{R}{N}$

Ex 2

Only two resistors

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

— all numerical examples are pretty easy.


# § 28.3 Again

28-31

## Kirchhoff's law 2

— Now we look at a few less simple circuit examples.

### Ex 28.6

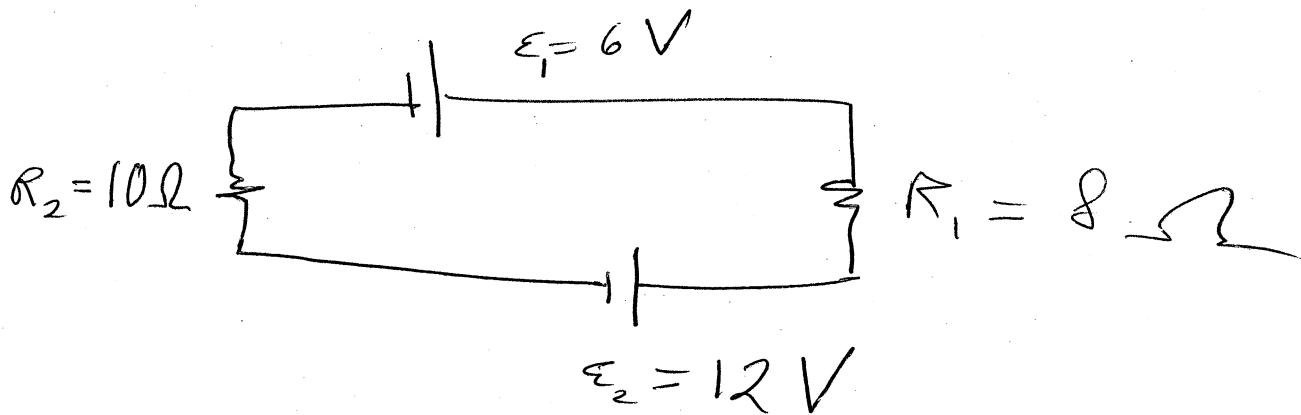

We assume ideal emf

— so no internal resistance.

Rules of thumb — that follow from Ohm's law and ideal emf

In ~~each~~ ~~country~~ up ~~the~~ potential rises and drops around a loop.

— Across a resistor — going with current, potential drops  
— going against current, potential rises.

28-32

~~for emfs — going with current~~  
~~there's a potential~~  
~~rise.~~  
~~— go~~

— for emfs from -ve to +ve  
is always  
~~at~~ a rise.

from +ve to negative  
is always a drop.

These rules almost going without  
saying — but it's still good  
to say them.

Now in this example we need  
to make a guess at which  
way the current flows.  
— if we are wrong, there is  
no problem, we just  
get a negative current.  
to set up for solving.



In this case, we

expect the  $\mathcal{E}_2 = 12\text{ V}$  to set the current direction because it's the biggest potential hill.

so we guess counterclockwise current

Just one loop and so Kirchhoff's current law trivially tells us that there's just one current  $I$ .

Going around the loop counterclockwise

$$\mathcal{E}_2 - IR_1 - \mathcal{E}_1 - IR_2 = 0$$

Solve for  $I$  which is our unknown.


$$I = \frac{\mathcal{E}_2 - \mathcal{E}_1}{R_1 + R_2} = \frac{12 - 6}{18 + 80} = \frac{6}{98} = \frac{1}{16.33} \text{ A}$$

§ 7-787 got  $-\frac{1}{3} \text{ A}$ , but they

28-34

defined the other direction around the loop as positive.

### Ex 28.7 generalized

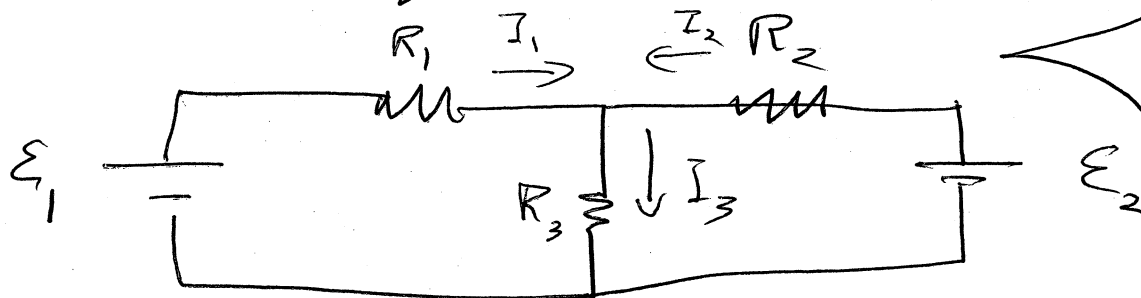

I've made a current choice which seems obviously right unless on emf is reversed

We are given  $\mathcal{E}_1, \mathcal{E}_2, R_1, R_2, R_3$

which ~~in practice is the usual case~~ may or not be the case in practice.

— after all in designing a circuit you may know the current you want and may need to find the emf's or resistors to give it.

But finding the current and resistors is not of the straightforward case.

28-35

3 unknowns  $I_1, I_2, I_3$ .

— we have ~~4~~ possible <sup>linear</sup> equations in the 3 unknowns.   
 { linear because ~~no~~ 3 loops occur linearly

↳ 3 loops equations and 2 node equations

↳ but actually only 3 independent equations

$$I_1 + I_2 = I_3 \text{ and } I_3 = I_1 + I_2$$

are trivially the same.

— proving the 3<sup>rd</sup> loop equation is ~~the~~ redundant gives no new constraint is a bit

28-36

trickier and I won't  
bother to show that.

I think it's true for  
any linear circuit problem,  
given all devices one can  
solve for all currents in  
all distinct branches  
and one has  
just enough  
independent equations  
to do that  $\rightarrow$  but  
the general proof is beyond  
our scope and my knowledge.

In solving such problems  
is best to take the  
most symmetrical equations,  
— usually that leads  
to simple expressions.

So

$$I_1 + I_2 = I_3$$

$$\varepsilon_1 = I_1 R_1 + I_3 R_3$$

$$\varepsilon_2 = I_2 R_2 + I_3 R_3$$

Experience (but also insight)

says let's solve for  $I_3$

first, ~~since~~ The insight is that it appears "unsymmetrically"

$$I_1 = \frac{\varepsilon_1 - I_3 R_3}{R_1}$$

$$I_2 = \frac{\varepsilon_2 - I_3 R_3}{R_2}$$

$$\frac{\varepsilon_1}{R_1} + \frac{\varepsilon_2}{R_2} = I_3 \left( 1 + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right)$$

$$I_3 = \frac{\varepsilon_1 / R_1 + \varepsilon_2 / R_2}{1 + R_3 / R_1 + R_3 / R_2} = \frac{\varepsilon_1 R_2 + \varepsilon_2 R_1}{R_1 R_2 + R_3 R_2 + R_3 R_1}$$

28-38

$$I_1 = \frac{\epsilon_1 (R_1 R_2 + R_1 R_3 + R_2 R_3) - \epsilon_1 R_2 R_3 - \epsilon_2 R_1 R_3}{R_1 (R_1 R_2 + R_1 R_3 + R_2 R_3)}$$
$$= \frac{\epsilon_1 (R_2 + R_3) - \epsilon_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

by symmetry, just interchange  
1 & 2 labels

$$I_2 = \frac{\epsilon_2 (R_1 + R_3) - \epsilon_1 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

### Special Cases

a) — the actual SJ-788 case

~~$\epsilon_1 = 10, R_1 = 6$~~

$$\epsilon_1 = -10, R_1 = 6$$

$$\epsilon_2 = 14, R_2 = 4$$

$$R_3 = 2$$

$$I_1 = \frac{-10(6) - 14.2}{24 + 12 + 8}$$

$$= \frac{-60 - 28}{44} = -\frac{88}{44} = -2 \text{ A}$$

but that okay since my fiducial current direction was opposite SJ-788's ( $I_1 = 2 \text{ A}$ )

$$I_2 = \frac{14(8) - (-10) \cdot 2}{44}$$

$$= \frac{112 + 20}{44} = 3 \text{ A}$$

~~the~~ SJ-788 get  $I_2 = -3 \text{ A}$  but they set their fiducial current direction opposite


$$I_3 = I_1 + I_2 = -2 + 3 = 1 \text{ A} \quad \left\{ \begin{array}{l} \text{SJ-788} \\ \text{get} \\ +1 \text{ A} \\ \text{of course} \end{array} \right.$$

28-40)

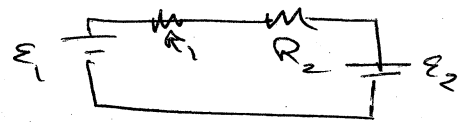b) Say  $R_3 \rightarrow \infty$

So that our circuit reduces to 1 loop really.

$$I_1 = \frac{\varepsilon_1 - \varepsilon_2}{R_1 + R_2}$$




Just the result of p. 28-33

$$I_2 = \frac{\varepsilon_2 - \varepsilon_1}{R_1 + R_2} = -I_1$$

$$I_3 = 0$$

c) Say  $R_3 \rightarrow 0$

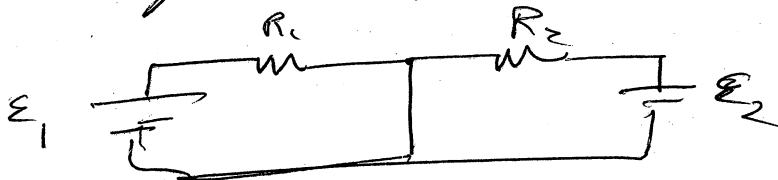

In this case it's like 2 independent loops almost except  $I_1 + I_2 = I_3$

$$I_1 = \frac{\varepsilon_1 R_2}{R_1 R_2} = \frac{\varepsilon_1}{R_1}$$

$$I_2 = \frac{\varepsilon_2}{R_2}$$



# § 28.4 RC Circuits

28-41


Now we put a capacitor in a circuit.

— This will give us NOT a linear equation for current.

but a differential equation

(a D.E.)

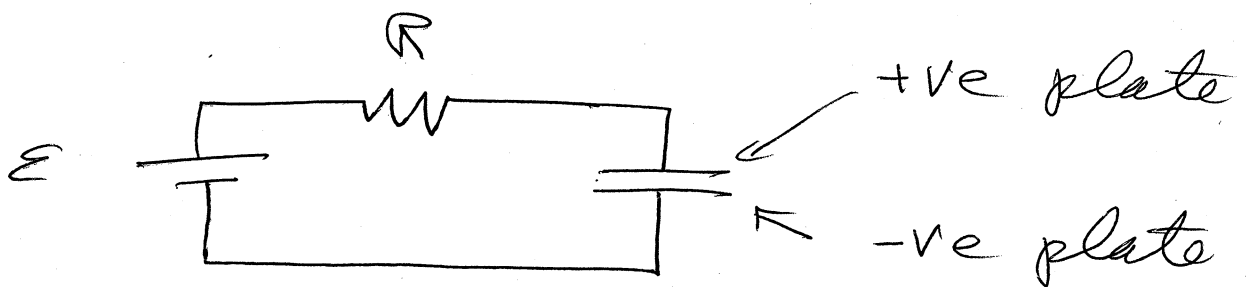~~Case 1~~ Charging a Capacitor <sup>+ Discharging a Capacitor</sup>



Using Kirchhoff voltage law

28-42

Recall  $C = \frac{q}{V}$   
 $V = \frac{q}{C}$

$$\mathcal{E} = IR + \frac{q}{C}$$

potential  
rise  
~~across~~  
across  
emf

potential  
drop  
across  
resistor

potential  
drop  
across  
the capacitor

Note  
 $C \rightarrow \infty$   
is the  
no capacitor  
case.  
No capacitor  
in infinite  
capacitors

$q$  will rise  
as current  
flows into  
capacitor.

— Kirchoff's  
voltage law  
can still be  
used since the  
time variation turns out to be  
slow enough.

— +ve in one side  
— -ve out the  
other.

(at any one instant a quasi electrostatic  
potential ~~loop~~ distribution  
exists.

~~The~~ If one just  
has an open circuit  
and an uncharged  
capacitor  $q = 0$

Close the circuit ~~and~~ at  $t = 0$ ,  $q = 0$   
 $I = \frac{\mathcal{E}}{R}$

and  $q = \int I dt'$   
as time passes.

we assume  
the current  
starts instantaneously  
Nearly true since  
the E-field changes  
~ at nearly

and when  $\frac{q}{C} = \mathcal{E}$  then  $I = 0$

for the Kirchoff  
voltage law  
to hold.

So we know  
end points and  
just need to find  
how  $I$  and  $q$   
vary in time.

the speed  
of light  
time.

I prefer to differential  
equation  $\mathcal{E} = IR + \frac{q}{C}$

28-44

This equation is valid

for  $E \neq 0$  ~~and~~

which would  
charging and  
 $E = 0$  which  
is discharging

$$\therefore 0 = \frac{dI}{dt} R + \frac{I}{C}$$

This is  
a famous  
DE  
with a  
simple  
solution  
for I

$$\begin{aligned} \frac{dq}{dt} &= \int_0^+ I dt' \\ &= \frac{d(q(t) - q(0))}{dt} \\ &= I \end{aligned}$$

$$\therefore \frac{dI}{dt} = -\frac{I}{RC} = -\frac{I}{\tau}$$

We define  $\tau = RC \Rightarrow \frac{V}{A} \frac{C}{V} = s$

$\tau$  is the time constant

or I prefer to

call it the

$e$ -folding time

for reasons

soon to be seen.

28-46

Case 1

In this case

at  $t = 0$ ,  $q = 0$

and Kirchhoff's voltage

law gives  $\mathcal{E} = I_0 R$

$$\text{or } I_0 = \frac{\mathcal{E}}{R}$$

Now at  $t = \infty$ , the capacitor should be fully

charged and  $I = 0$

$\therefore$  Kirchhoff's voltage law gives  $\mathcal{E} = \frac{q_{\infty}}{C}$

$$\text{or } q_{\infty} = C\mathcal{E}$$

So we have  $I = \frac{\mathcal{E}}{R} e^{-t/\tau}$

$$\begin{aligned} q &= -\frac{\mathcal{E}}{R} RC e^{-t/\tau} + C\mathcal{E} \\ &= C\mathcal{E}(1 - e^{-t/\tau}) \end{aligned}$$

$$\int \frac{1}{I} \frac{dI}{dt} dt = - \int \frac{1}{\tau} dt$$



indefinite integrals

$$\ln I = - \frac{t}{\tau} + \text{Constant}$$

$$e^{\ln I} = e^{-t/\tau + \text{Constant}}$$

$$I = I_0 e^{-t/\tau}$$


where  $I_0$  is set by the initial condition at  $t=0$ .

To get the charge ~~accumulation~~ on the capacitor we need to integrate again indefinitely.


$$Q = -I_0 \tau e^{-t/\tau} + Q_\infty$$

~~where~~ where  $Q_\infty$  is  $Q(t=\infty)$ .
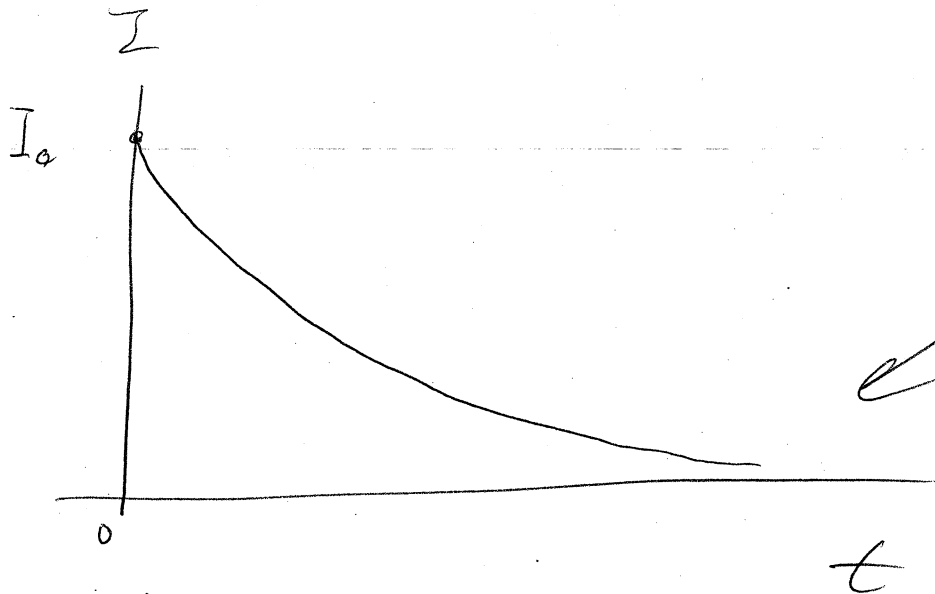
$$V_c = \frac{q}{C} = \mathcal{E} (1 - e^{-t/\tau})$$



asymptotically approaches zero

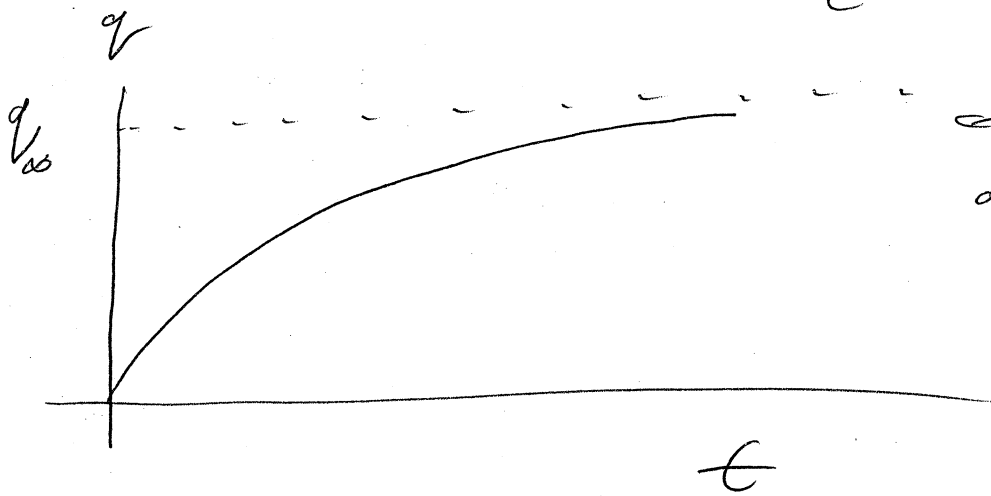

asymptotically approaches  $q_{\infty}$

Formally the ~~cap~~ capacitor never gets to  $q_{\infty}$  and the current never drops to zero.

28-48)

But practically  
in a finite time, the  
system ~~approaches~~ <sup>is closer to</sup> the  
final value than one's  
measuring error or  
than the size of perturbation  
affecting the system.

- generally a few  $e$ -foldings  
times.


Note  $e^{-t/\tau} = 10^{(\log e)(-t/\tau)}$   
 $\approx \left\{ \begin{array}{l} 10^{-0.434(-t/\tau)} \\ \sim 10^{-4.3} \text{ for } t = 10\tau \\ 10^{-43} \text{ for } t = 100\tau \end{array} \right.$



- relative differences of  $10^{-43}$  are immeasurably small in almost any context one can imagine.

Case 2 Discharging capacitor

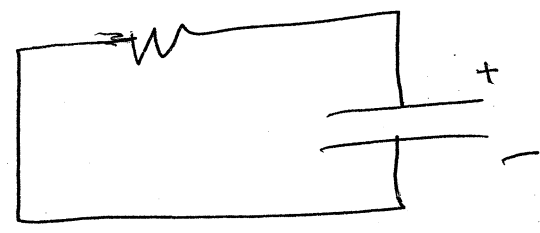from ~~the~~ ~~EE~~ of the charging phase



The emf has been removed from the circuit.

In this case the Kirchoff's voltage law gives

$$0 = IR + \frac{d}{c}$$

and so  $I < 0$  which

28-40

our convention  
means the current flows  
out of the capacitor.

$$I_0 = \frac{-q_0}{RC} = -\frac{q_0}{\tau}$$

$$I = -\frac{q_0}{\tau} e^{-t/\tau}$$

$$P = I^2 R = \frac{q_0^2}{\tau^2} R e^{-2t/\tau}$$


Sec. 28-95

$q_{\infty} = 0$  when capacitor  
is fully discharged  
which must  
happen because  
of the current  
Power output  
to resistor.

$$\begin{aligned} \therefore q &= -I_0 \tau e^{-t/\tau} \quad \text{from} \\ &= q_0 e^{-t/\tau} \quad \text{p. 28-45} \end{aligned}$$

If we assume we charged up using  
emf  $\mathcal{E}$ , then  $q_0 = C\mathcal{E}$ .

28-51

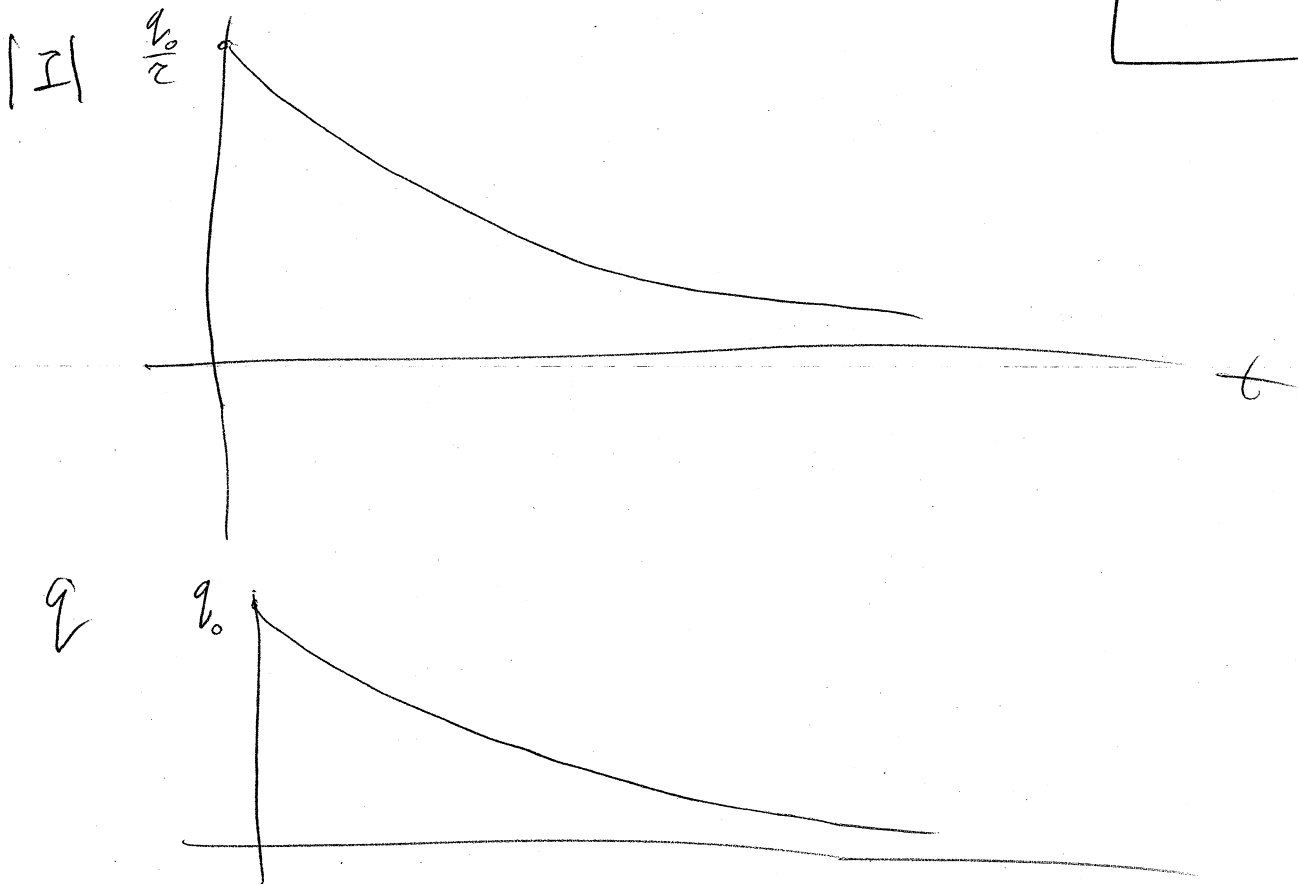

Again formally the capacitor is never fully discharged and current never goes to zero.

But practically in a few folding times the final values are reached effectively

Our RC circuits are used for

28-52

been charging up  
capacitors and using  
them — Not  
necessarily with the  
same circuit they were  
charged with.

In fact a charged capacitor  
can be used as a source of  
electrical energy.

It stores  $PE = \frac{1}{2} CV^2$   
 $= \frac{1}{2} \frac{q^2}{C}$   
recall.

~~It is usual~~

Capacitors are not usually  
considered emf's ~~or~~ because  
they do not

Maintain a constant potential across their terminal as they discharge

28-53

$$V = \frac{q}{C} \text{ recall.}$$

But you can store a lot of energy in capacitors and if the ~~time of the~~ ~~to~~ distribution of the release is not important or exponential release ~~is fine~~ of energy is OK then capacitors can be used.

e.g., 1) Some camera flashes are powered by capacitors. (WP-685)  
-626

2) Super powerful experimental lasers.

the now defunct NOVA laser

28-54) at LLNL

~~use~~ stored energy  
in a  $C = 2.3 \text{ F}$   
capacitor bank

for emitting ~~150 kJ~~

15 kJ pulses in .1 ns

$$P_{\text{ave}} = \frac{15 \times 10^3}{10^{-9}} \quad (\text{WP-626})$$

$$= 1.5 \times 10^{12} \text{ W}$$

$$= 1.5 \text{ TW}$$

which is just about the  
average commercial power consumption  
of the whole world. (Wik)

A capacitor ~~can~~ among other  
things is like a toilet cistern,

↳ ~~you~~ where you store up  
water slowly and then release it  
in burst (burst) of unsteady flow

(WP-625)

Of course, capacitors  
have lots of other  
uses — e.g., in tuning

25-85

for electronic signal reception  
but I'm not terribly knowledgeable.

## § 28.5 Electrical Meters

— optional reading

## § 28.6 Electrical Safety

— optional reading.

28-56