

Chapter 33

33-1

- AC circuits
- Alternating Current
- Electric generators naturally tend to produce AC as we seen & electric motors to use it.
But actually conversion between AC + DC can be done and there is no strong reason just based generation & production mode to favor one over the other.

Transmission efficiency
became the reason AC

33-2)

won out for the power grid in the 1880s
in the War of the Currents

Westinghouse and Tesla pro AC

Edison pro DC

AC won — but never totally.

~~For~~ High Voltage transmission
is ~~power~~ efficient in
not losing energy in transmission
(heating the wires)

- But that can be done with
either AC or DC.

But AC can use transformers

to step-up
↓ step-down potential
safely.
this allows
high potential for transmission
and lower less dangerous
potential for generation and use.

But that was in the 1880s

since then step-up
& step-down DC
technology has developed

more and high-voltage DC is
~~more~~ efficient ~~than~~ than AC for
very long-range transmission
and is used for remote communities
in Canada, Siberia, & Scandinavia.

33-4) In fact a new advanced power grid for the US (and maybe all of North America) could be HVDC.

§ 33.1

Typical AC is sinusoidal

— easy to generate,
is to transform.

So an AC emf could be


$$E = E_0 \sin \omega t$$

or $E_0 \cos \omega t$

→ the two functions have the

some shape — one is
just displaced from
the other

33-5

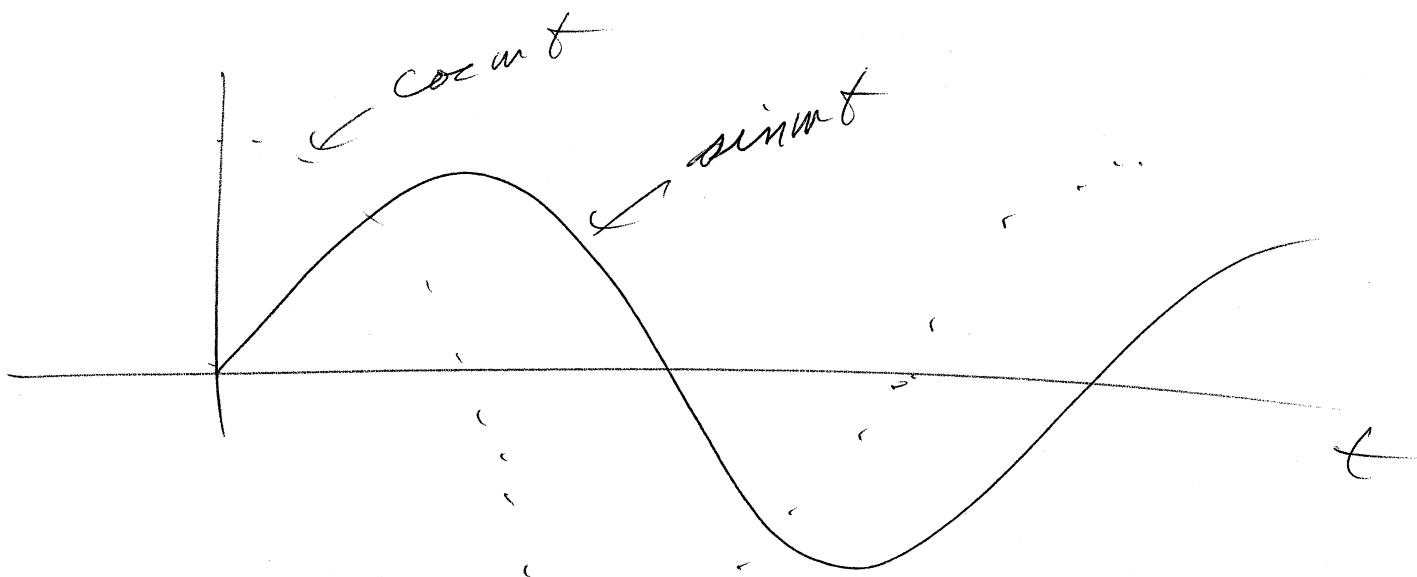

Since in steady state application
the ^{time} origin is unimportant, one
can use either one.

Say $E = E_0 \sin \omega t$

E_0 is the amplitude.

ω is the angular frequency.

If $\omega st = 2\pi$, then the

33-6]

~~cycle~~ function repeats.

∴ $T = \frac{2\pi}{w}$ is the period.

and $f = \frac{1}{T} = \frac{w}{2\pi}$

is the frequency
in cycles per
unit time.

In USA we use $f = 60 \text{ Hz}$

but some countries
use $f = 50 \text{ Hz}$

 hertz = $\frac{1}{s}$

(Japan was indecisive
on this and uses
both 50 Hz & 60 Hz (Wk))

- There are tradeoffs to using higher or lower frequencies, and probably no optimum choice.

Niagara Falls once ^{conveyed} [33-7]
 generate 25 Hz, but that
 was a bit low and caused
 light bulbs to noticeably
 flicker (W. K.).

E_0 is the amplitude
but this is not
= the voltage usually
 reported to characterize
 the potential.

Root-Mean-Square potential
^(RMS)
 is reported.

$$E_{\text{RMS}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} E_0^2 \left\{ \sin^2 \omega t + \cos^2 \omega t \right\} dt}$$

$$\begin{aligned} \alpha &= \omega t - \omega t_0 \\ dx &= \omega dt \\ T_w &= 2\pi \end{aligned}$$

$$= E_0 \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \left\{ \sin^2 \alpha + \cos^2 \alpha \right\} d\alpha}$$

33-8

$$= E_0 \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \frac{1}{2}(1 + \cos 2x) dx}$$

$$\left. \frac{1}{2}(x + \frac{\sin 2x}{2}) \right|_0^{\pi}$$


$$E_{\text{RMS}} = \frac{E_0}{\sqrt{2}}$$

Northern & South Am,
of Saudi Arabia & Japan
- Most others use $E_{\text{RMS}} = 110$

In North America we use

$$E_{\text{RMS}} = 120 \text{ V}$$

which implies $E_0 = \sqrt{2} E_{\text{RMS}}$

$$= 169,705.6 \dots \text{V}$$

Wk
Mains
Power
systems

§ 33.5 RLC Circuit

with an AC driver

- we're skipping 3 sections and phasor diagrams (I don't like them because I know nothing about them — which is a treacherous argument for a pedagogue to make)



We use Kirchhoff Voltage law for one loop

- the order of RLC is not important in the analysis.

Obvious
this is
just a

33-10)

series circuit with resistor, inductor, and capacitor but it is illustrative

Kirchhoff Voltage law

$$\text{emf rise} = \mathcal{E} = IR + L \frac{dI}{dt} + \frac{q}{C}$$

$$\mathcal{E} = \mathcal{E}_{\text{emf wt}}$$

\uparrow a driver

drop for $I > 0$	drop for $\frac{dI}{dt} > 0$	drop for $q > 0$
if $I < 0$, it's a negative drop	$\frac{dI}{dt} < 0$ it's a negative drop	$q < 0$ it's a negative drop.

This distinguishes the problem from our previous case.

→ the solutions we found there ~~are~~ have analogs here

33-11

— but those
are transient solutions

~~fact~~ \rightarrow they disappear

in time — ~~disappear~~

— often so rapidly
as to be negligible.

say $I_{\text{general}} = I_{\text{driven}} + I_{\text{transient}}$

$$\mathcal{E} = I_{\text{driven}} R + L \frac{dI_{\text{driven}}}{dt} + \frac{Q_{\text{driven}}}{C}$$

$$+ I_{\text{transient}} R + L \frac{dI_{\text{transient}}}{dt} + \frac{Q_{\text{transient}}}{C} = 0$$

If I_{driven} ,
solves the
~~so~~ part

because it is the
solution with no
driven.

then I_{general} is a solution

33-12

But since the transient disappears in time and such circuits are primarily of interest long after the transient is gone we only need to consider the driven solution.

So in DE given the homogeneous solution.

We do a solution by trial function since we have centuries of experience telling us what works.

First we really want I not q .

33 - 13

So let's differentiate once.

$$E_{\text{min}} \sin \omega t = IR + LI' + \frac{q}{C}$$

$$E_0 \sin \omega t = I'R + LI'' + \frac{I}{C}$$

The trial solution

is $I = I_0 \sin(\omega t - \phi)$

I_0 is amplitude of the current

ϕ is the phase shift from the driver.

Both of these are determined by E_0, R, L, C .

33-19

Here we just give the results


— the mathematics of the solution is a bit too involved.

$$I = I_0 \sin(\omega t - \phi)$$

$$I_0 = \frac{E_0}{Z} = \frac{E_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

impedance $\phi = \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$

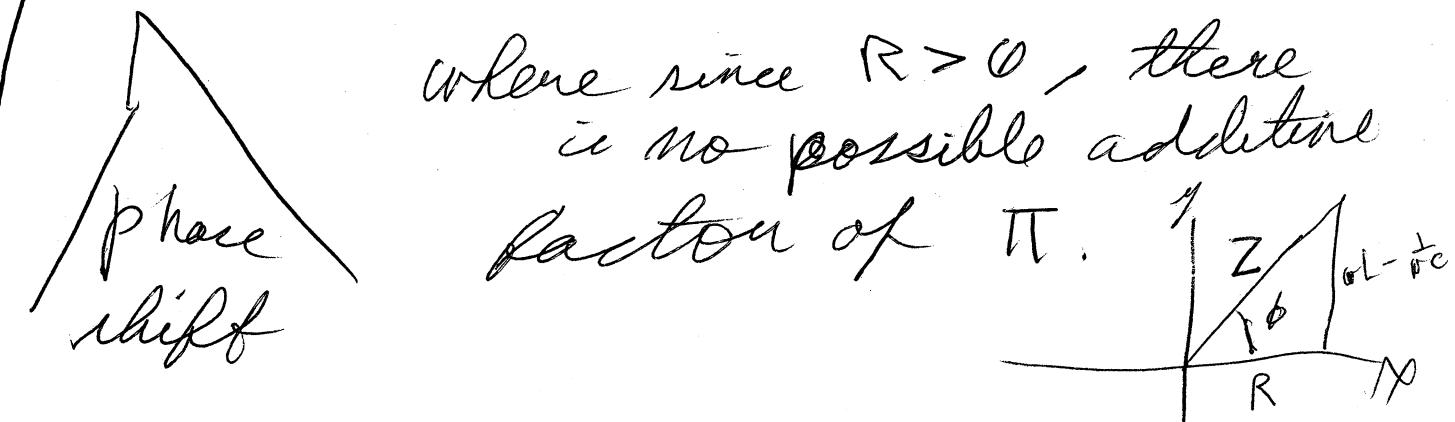where since $R > 0$, there is no possible additional factor of π .



Optional ComplexNumber Solution

Replace our trial solution
by a complex solution

$$\underline{I} = I_0 e^{i(\omega t + \phi)}$$

where we can restrict I_0
to be pure real. The ϕ
parameter gives us enough
freedom for a consistent
solution.

I_0 and ϕ are two
parameters ~~that~~ whose
values are set by the solution.

33-16)

Using Euler's formula
(Art-264)

$$e^{ix} = \cos x + i \sin x$$

where i is the imaginary unit,
we find

$$\text{Re}[I] = I_0 \cos(\omega t + \alpha) \quad \text{real part}$$

$$\text{Im}[I] = I_0 \sin(\omega t + \alpha) \quad \text{imaginary part}$$

In complex numbers ~~j~~ "real"
and "imaginary" are jargon terms
~~for~~ for the two components
of a complex number
— both are really real.

The original DE is

$$E_w \cos \omega t = I'R + L\dot{I}'' + \frac{I}{C}$$

The analog complex DE is

$$E_w e^{i\omega t} = I'R + L\dot{I}'' + \frac{I}{C}$$

33-17

The real part of
the trial solution solves
the original DE. This is
the solution we want.

Substituting the trial $I = I_0 e^{i(\omega t + \alpha)}$
into the complex DE gives

$$\mathcal{E}_0 w = R I_0 e^{i\alpha} + L(-w^2) I_0 e^{i\alpha} + \frac{I_0 e^{i\alpha}}{C}$$

canceling the common $e^{i\omega t}$
factor.

The solution for $I_0 e^{i\alpha}$ is

$$I_0 e^{i\alpha} = \frac{\mathcal{E}_0 w}{i\omega R - L\omega^2 + \frac{1}{C}}$$

$$= \frac{\mathcal{E}_0}{iR - L\omega + \frac{1}{\omega C}}$$

33-18]

$$I_0 e^{i\alpha} = \frac{\epsilon_0 [-iR - wL + \frac{1}{wC}]}{R^2 + (\frac{1}{wC} - wL)^2}$$

$$I_0 = \sqrt{(I_0 e^{i\alpha})(I_0 e^{i\alpha})^*}$$

Complex conjugation

$$= \sqrt{\frac{\epsilon_0^2 (R^2 + (\frac{1}{wC} - wL)^2)}{(R^2 + (\frac{1}{wC} - wL)^2)^2}}$$

$$I_0 = \frac{\epsilon_0}{\sqrt{R^2 + (\frac{1}{wC} - wL)^2}}$$

where $Z = \sqrt{R^2 + (\frac{1}{wC} - wL)^2}$
 is defined as impedance

33-19

$X_L = \omega L$ is inductive reactance

$X_C = \frac{1}{\omega C}$ is capacitive reactance.

Now $e^{i\alpha} = \cos \alpha + i \sin \alpha$

$$\tan \alpha = \frac{\sin \alpha}{\cos \alpha} = \frac{-R}{-\omega L + \frac{1}{\omega C}}$$

~~$\tan^{-1}(\omega L - \frac{1}{\omega C})$~~

$$\alpha = \tan^{-1} \left(\frac{R}{\omega L - \frac{1}{\omega C}} \right) + n\pi$$

Needed
because
of the
ambiguity of
the inverse tangent function.

where $n = 0$ for $\omega L - \frac{1}{\omega C} > 0$
and $n = 1$ for $\omega L - \frac{1}{\omega C} < 0$

33-20

Show the ^{real} solution which is the solution of the real part of the complex DE is the solution of the original ~~real~~ DE:

The real solution is the real solution.

$$I = I_0 \cos(\omega t + \alpha)$$

but our EMF was in terms of the sine function

$$E = E_0 \sin(\omega t)$$

and so it is convenient

to write I

33-21

in terms of sine for
easy comparison.

$$\sin(x + \frac{\pi}{2}) = \sin x \cos \frac{\pi}{2}$$

$$\text{and } \cos(x + \frac{\pi}{2}) = \cos x \cos \frac{\pi}{2} - \sin x \sin \frac{\pi}{2}$$
$$= -\sin x$$
$$= \cos x$$

$$\therefore I = I_0 \sin(\omega t + \alpha + \frac{\pi}{2})$$
$$= -\phi$$

$$\text{Now } \tan(-\phi) = \tan(\alpha + \frac{\pi}{2})$$

$$= \frac{\cos \alpha}{-\sin \alpha}$$

$$= -\cot \alpha$$

$$= -\left(\frac{wL - \frac{1}{wC}}{R}\right) = \cancel{\text{---}}$$

$$\phi = \tan^{-1}\left(\frac{wL - \frac{1}{wC}}{R}\right)$$

33-22]

where since $R \geq 0$

there is no additive π constant needed.

So to summarize.

$$I = I_0 \sin(\omega t - \phi)$$

$$I_0 = \frac{E_0}{Z} = \frac{E_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\phi = \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$$

Now that wasn't so bad.

What does the solution mean?

Well the current is also sinusoidal with the same ~~current~~ frequency as the driver.


But the inductor and capacitor cause a phase shift

$$\phi = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

which is frequency dependent

If $\omega \rightarrow 0$, $\phi \rightarrow 0$ dependent.

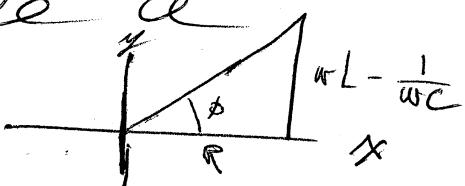but then E is constant E_0 and $J = J_0 = 0$ since the ~~capacitor~~



33-21]

capacitor is just all charged up

$$\rightarrow Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$\rightarrow \infty$$

$$I_o = \frac{E_o}{Z_o} = 0.$$

Inductance L , inductive reactance ωL
 Capacitance C , capacitive reactance $\frac{1}{\omega C}$


We ~~try~~ can ~~to~~ shift in opposite $\omega L > \frac{1}{\omega C}$
~~the~~ phases:

①

$$\omega L > \frac{1}{\omega C}$$

$$\phi > 0$$


and I write rightward

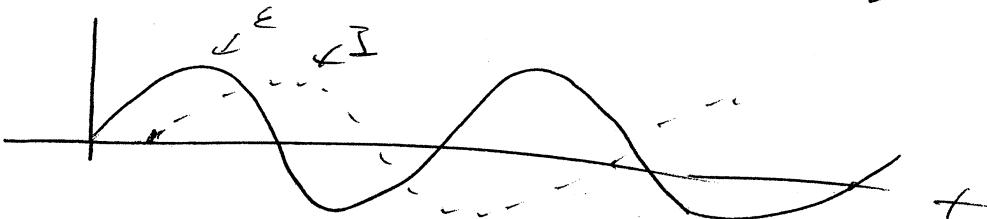

$$\textcircled{b} \quad wL < \frac{1}{wC}$$

33-25

and $\phi < 0$ and I
shifts leftward

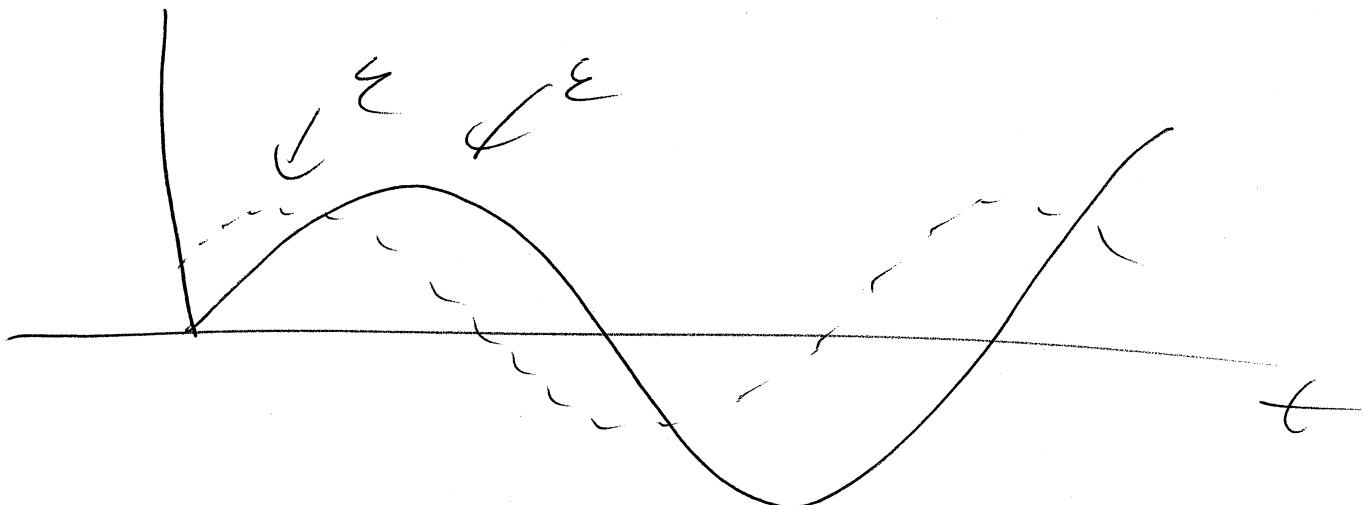

§ 33.6 Power in AC circuits

— As we saw in the single ^{driven} RLC circuit there can be a shift between current & voltage sinusoids. And such shifts are general in AC circuits.

33-26) not just the simple ^{driven} RLC circuit

This has an effect on the power output or input.

Recall

$$P = IV$$

P
power
output
or input.

\uparrow
drop or
rise in
potential
across
a device


— This expression is true even for time-varying ~~systems~~ systems.

Set at an instant the potential difference is V and current I .

In Δt the individual carriers don't move much perhaps, but ~~but~~

$$\Delta E = V \Delta t = I V \Delta t = dq V$$

is still the energy deposited

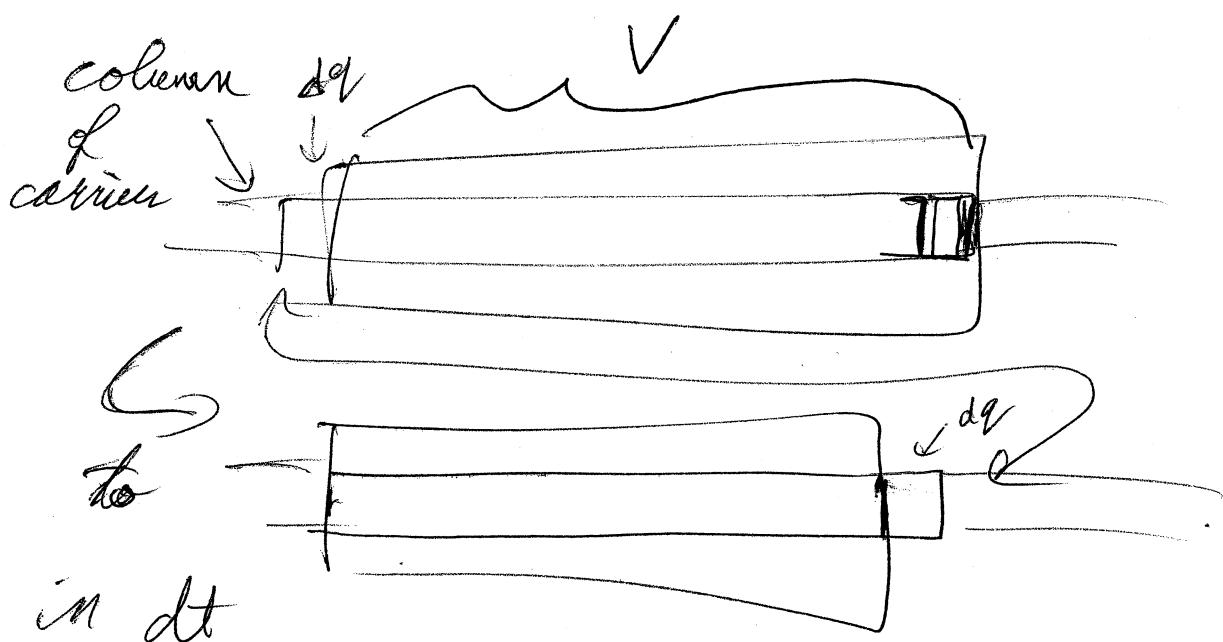

~~It's~~ It's the same ^{PE} energy change as if you moved the carriers from one end to another in Δt .

Now in Δt , V could change from V to $V + dV$

$$\text{But } \Delta E = dq(V + dV) \approx dqV \text{ to 1st order}$$

33-28]

in small changes
and in the derivative
limit all higher order
changes vanish.

So $P = IV$ is valid
for varying system.

say $V = V_0 \sin(\omega t)$

and $I = I_0 \sin(\omega t - \phi)$

$$P = I_0 V_0 \sin(\omega t) \sin(\omega t - \phi)$$

but it's usually time averaged
power that is of interest.

$$\text{So } P_{\text{ave}} = \frac{1}{T} \int_t^{t+T} I_0 V_0 \sin(\omega t') \sin(\omega t' - \phi) dt'$$

Trig identity

$$\sin(\omega t - \phi)$$

$$= \sin \omega t \cos \phi - \cos \omega t \sin \phi$$

This term
leads

to $\frac{1}{2}$ factor

as we've shown before

$$\frac{1}{T} \int_{t'}^{t+T} \left\{ \begin{matrix} \sin \omega t' \\ \cos \omega t' \end{matrix} \right\} dt'$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \left\{ \begin{matrix} \sin x \\ \cos x \end{matrix} \right\} dx = \frac{1}{2}$$

assuming $x = \omega(t - t')$

when $\omega T = 2\pi$

This term leads to zero

$$\frac{1}{T} \int_t^{t+T} \sin \omega t \cos \omega t dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \sin x \cos x dx = \frac{1}{2\pi} \cdot \frac{\sin^2 x}{2} \Big|_0^{2\pi} = 0$$

33 - 20)

$$\text{So } P_{\text{ave}} = I_0 V_0 \left(\frac{1}{2}\right) \cos \phi$$
$$= \frac{I_0}{\sqrt{2}} \frac{V_0}{\sqrt{2}} \cos \phi$$
$$= I_{\text{RMS}} V_{\text{RMS}} \cos \phi$$

Recall $V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^{+T} V_0^2 \sin^2 \omega t dt}$


Root mean square

$$= \frac{V_0}{\sqrt{2}}$$

$$\text{if } \phi = 0^\circ$$

$$P_{\text{ave}} = I_{\text{RMS}} V_{\text{RMS}}$$

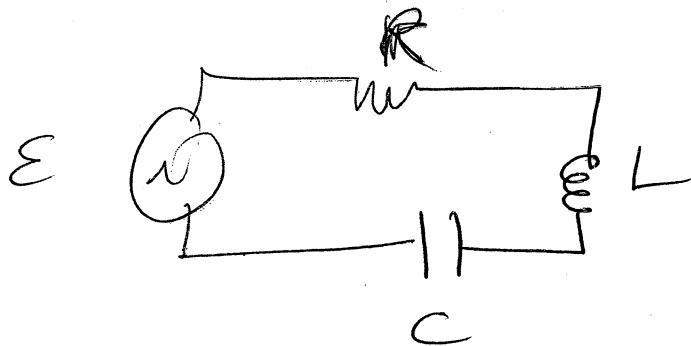Now to apply to our ^{driven} RLC circuit




33-30

$$P_{\text{out}} = I_{\text{RMS}} E_{\text{RMS}} \cos \phi$$

out
of emf

$$\approx - \frac{E_0^2}{Z} \frac{\cos \phi}{2}$$
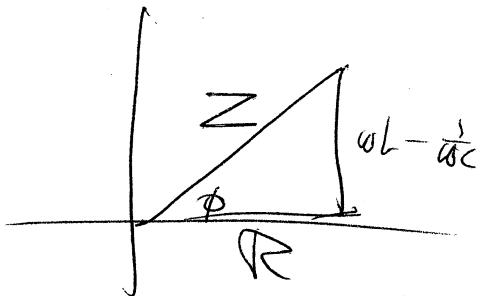
$$\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$



$$\cos \phi = \frac{R}{Z}$$

and $Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$

the impedance.

$$P_{\text{out}} = \frac{E_0^2}{2Z^2} R$$

Scrap
into circuit

~~P_{out}~~
of ~~emf~~
resistor
into heat

$$I_{\text{RMS}} V_{\text{RMS}} \cos \phi_{\text{resistor}}$$

↳ which is
fact is zero.

33-32

Now Ohm's law applies
at each instant.

$V = IR$ is the potential across the resistor

$$V_{\text{rms}} = I_{\text{rms}} R$$

$$= \frac{1}{\sqrt{2}} \frac{E_0}{Z} R$$

and $\phi_{\text{resistor}} = 0$

$$\therefore P_{\text{out}} = \frac{1}{\sqrt{2}} \frac{E_0}{Z} \frac{1}{\sqrt{2}} \frac{E_0}{Z} R$$

out
of
resistor

$$= \frac{E_0^2}{2Z^2} R = P_{\text{out}}$$

out of
emf.

and so we've verified

that energy is conserved. [33-33]

This was really built into system by Kirchhoff's laws and the ~~law~~ rules of PE and Ohm's laws.

What of the capacitor and inductor?

Well energy is being ~~constantly~~ put into them and taken out again in a period fashion.

— It goes into creating E-fields & B-fields recall.

Consider induction

$$V = L \frac{dI}{dt}$$

$$= L I_0 w \cos(\omega t - \phi)$$

33-34)

$$\text{So } P_{\text{ave}} = \frac{1}{T} \int_{t_0}^{t_0+T} I_0 \sin(\omega t - \phi) \\ * L \omega \cos(\omega t - \phi) dt \\ = 0$$

- no net power gain
or loss on average.

Capacitor.

$$\text{Well } V = \frac{q}{C}$$

$$\text{where } q = \int_{t_0}^t I_0 \sin(\omega t - \phi) dt$$

~~$\int_{t_0}^t \sin(\omega t) dt$~~

$$= -\frac{I_0}{\omega} \cos(\omega t - \phi) + C_0$$


So P_{ave} for capacitor

$$= \frac{1}{T} \int_{t_0}^{t_0+T} I_0 \sin(\omega t - \phi) [] dt$$

$$= 0$$

a time
zero
constant

33-35

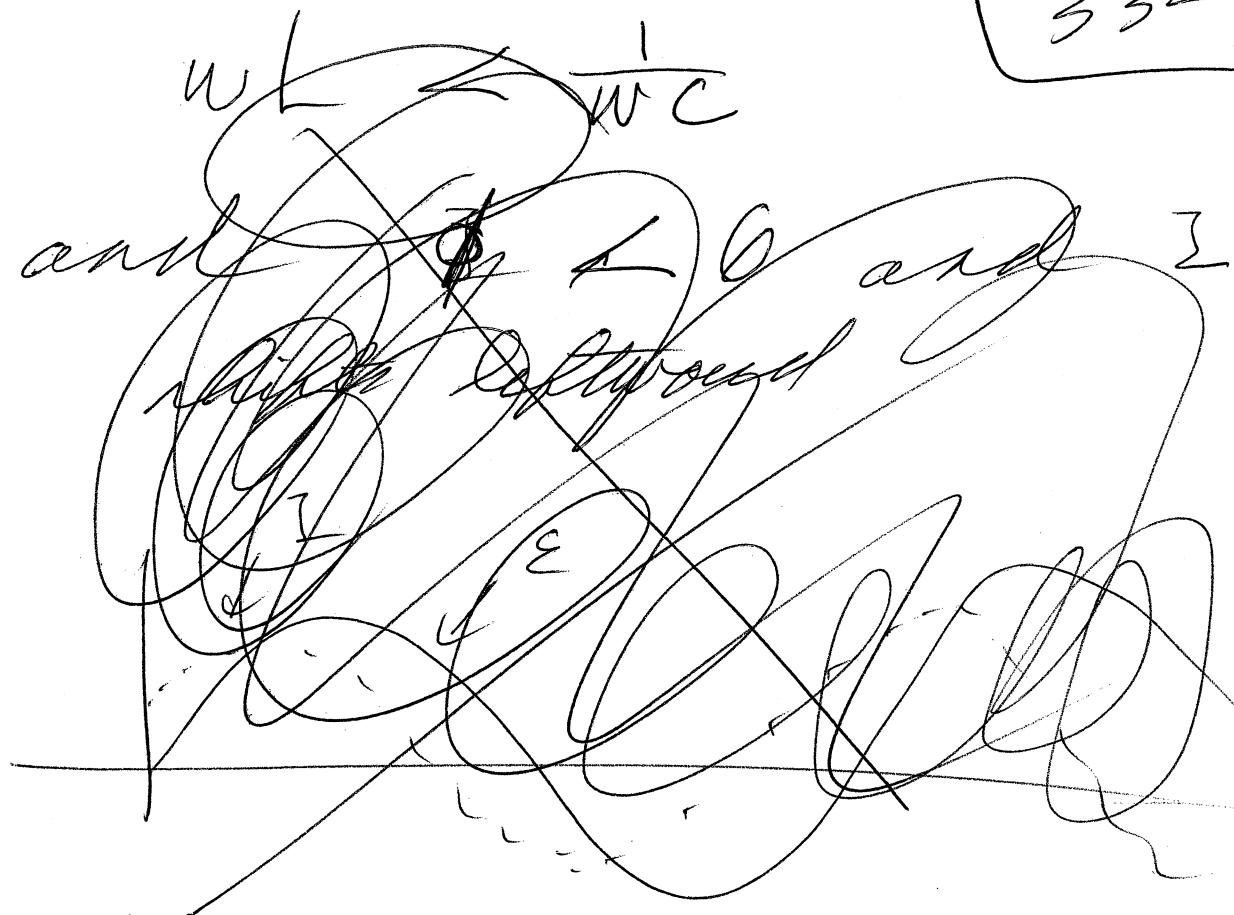

§ 33.7 Resonance

in Driven RLC circuit

The really interesting practical interest of RLC circuits — at least at our worm-like level is resonance.

33-2b


Many physical systems have oscillatory behavior and the frequency at which the oscillations grow large — sometimes very large are the resonance frequencies.

In fact everyone in the class knew how to drive an oscillator at a resonance before they knew the name of torque.

— the good old playground swing.


33-37

Resonance

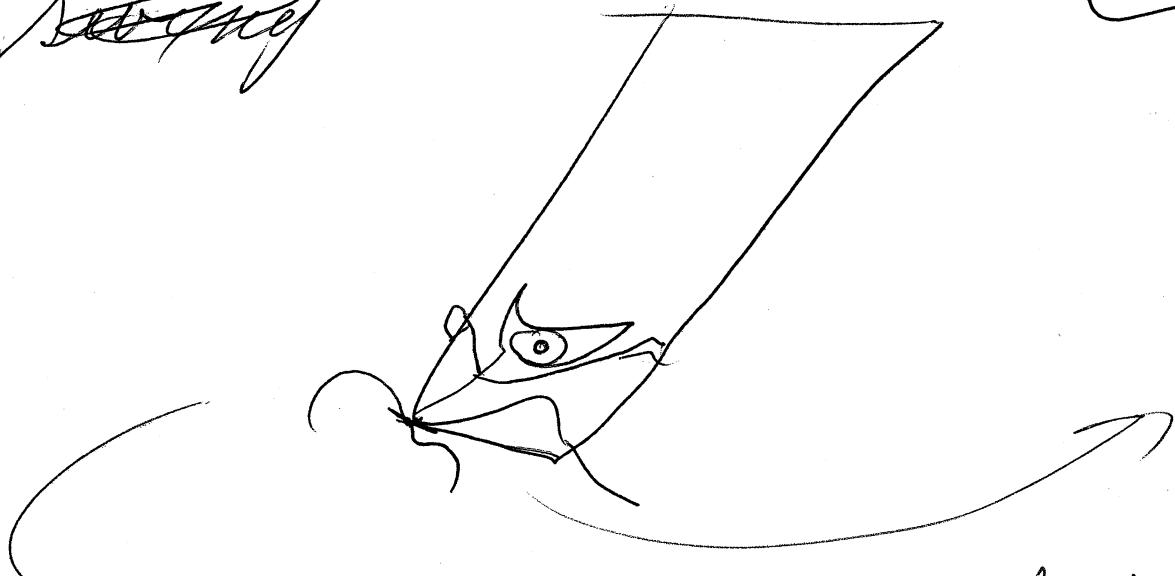

Really close to being
a simple pendulum with
resonance frequency
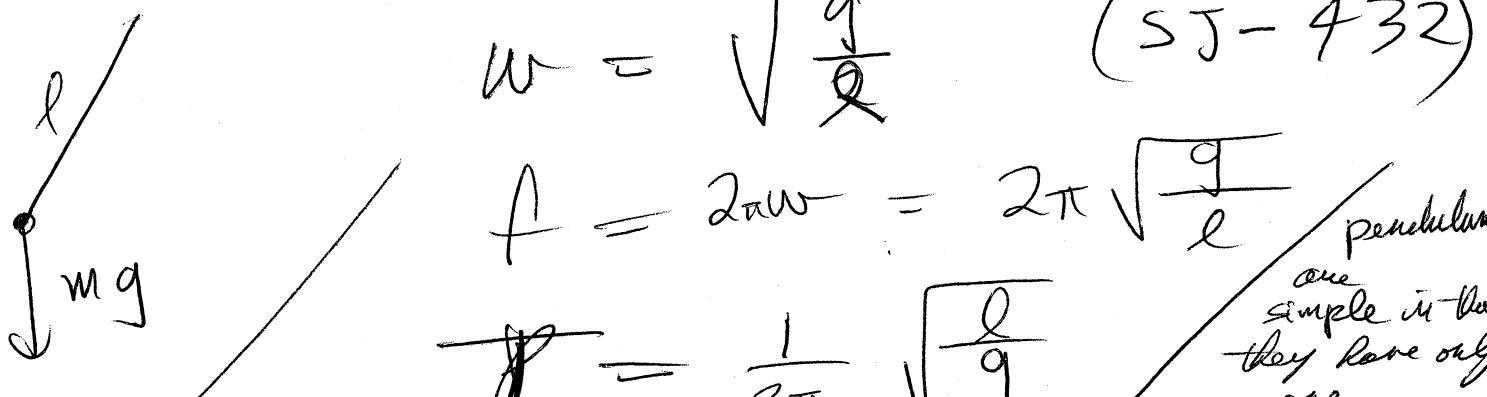
$$w = \sqrt{\frac{g}{l}} \quad (\text{SJ-432})$$



$$f = 2\pi w = 2\pi \sqrt{\frac{g}{l}}$$

$$\tau = \frac{1}{2\pi} \sqrt{\frac{l}{g}}$$

pendulum
one simple in that
they have only

one resonance

for a given
 l

the frequency of an unforced
pendulum — natural frequency

You can drive a pendulum
at any frequency; but

33-38]

then you constantly have to be adding & subtracting mechanical energy in a complex way to get big oscillations.

— If you drive it on resonance, you at little kicks of energy just at the resonance frequency — and the oscillations tend to grow without bound — of course, the ~~far~~ chain or ropes eventually lose tautness and that causes things and the ~~far~~ factor sets in too.

Foucault and owner react with frame frame background?
complex but still ultimately moves by pushing pulling off randomly

All traditional musical instruments rely on mechanical and/or sound resonance.

33-39

- atoms and molecules have QM resonances at which they absorb & emit electromagnetic radiation.

Our  ^{driven} RLC circuit solution exhibits a resonance.

$$I_o = \frac{E_o}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\phi = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

If $\omega L - \frac{1}{\omega C} = 0$,

or $\omega_{res} = \frac{1}{\sqrt{LC}}$

33-40]

$$\left. \begin{aligned} \text{also } \phi &= \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right) \\ &= 0 \text{ and so } E \text{ and } I \\ &\text{are in phase.} \end{aligned} \right\}$$

I_0 is largest for a given ϵ_0

Similarly the power dissipated in the resistor (See r. 33-32.)

$$P_{\text{ave}} = I^2 R = \frac{1}{2} \frac{\epsilon_0^2 R}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

Maximizes for $\omega_{\text{res}} = \frac{1}{\sqrt{LC}}$

From SJ-909

we recall $\omega = \frac{1}{\sqrt{LC}}$

is the frequency


of pure LC circuit

- it's the "natural"
frequency of the ~~the~~
RLC circuit.

This shape is quasi-Lorentzian

$$f(x) = \frac{1}{\pi} \frac{T/2}{(x^2 + x_0^2)} \text{ is } \cancel{\text{quasi}} \text{ Lorentzian (BeV - 53)}$$

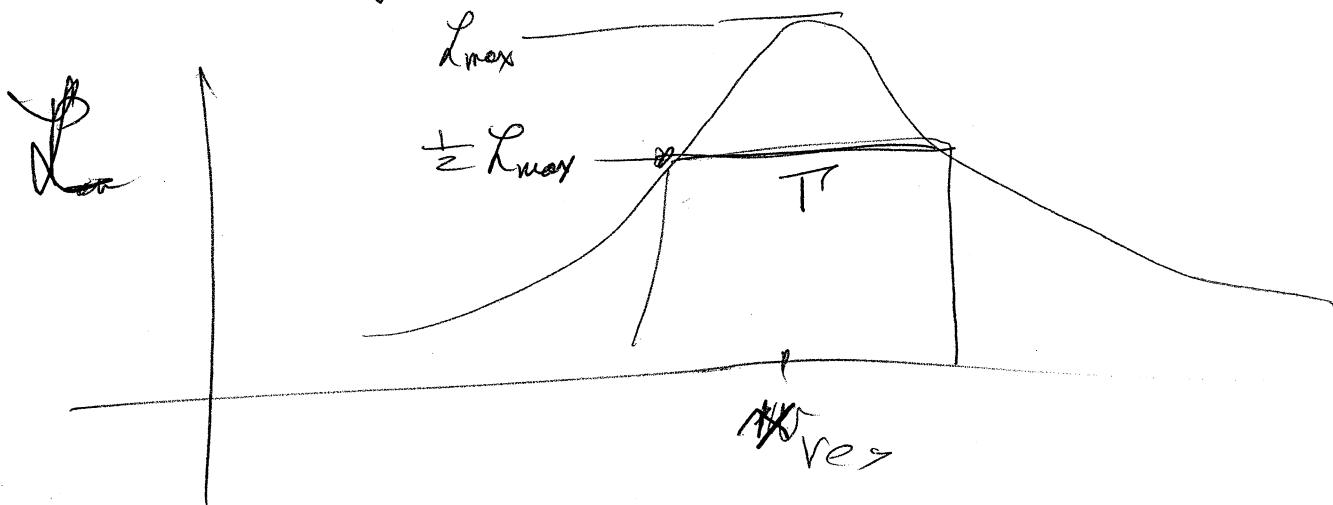— Just the name 33-41
 for this kind of
 function which often turns
~~up~~ up in resonance
 phenomena.



T is the full-width half maximum
 FWHM (Bev-51)

So $\frac{T}{2} = R$

or ~~T~~ $R = 2R$

— So R is half of FWHM

But our function is only
 an exact Lorentzian for $x = wL - wc$
 (not w)

33-42)

Driven RLC circuits
are used in tuning.

- e.g., radio, at least it can be.
- a radio antenna responds to all frequencies of radio emission.
- How does one select one's favorite country western station ("She done me wrong")
- all signals are run through an RLC ~~series~~ circuit.
- they are superimposed drivers.

— a variable capacitor 33-43
C

allows one to tune
for the radio frequency
one wants.

— So all other frequencies
are relatively suppressed
and the selected frequency
is used to drive amplifier
& speakers. (SJ-939)

There are probably trickier
ways of selecting frequencies
with modern electronics, but
the RLC circuit is the
conventional method.

33-44)

§ 33.8 Transformer

& Power Transmission

→ High voltage is better for transmission.

Say you had an E and some ~~intentional~~ load R .
— but also wires R_{wire} .

Say you had a circuit where you had an emf source of E

that output power $P = E I$

and you used that source to power a load

$$\text{with power } P_e = V_e I$$

but

there was also a resistance in the transmission ^{wire} R ,


and so a loss of energy

to waste heat that

$$\text{is } P_{\text{wire}} = V_{\text{wire}} I$$

$$= I^2 R \text{ using Ohm's law}$$

Schematically
the
circuit
is

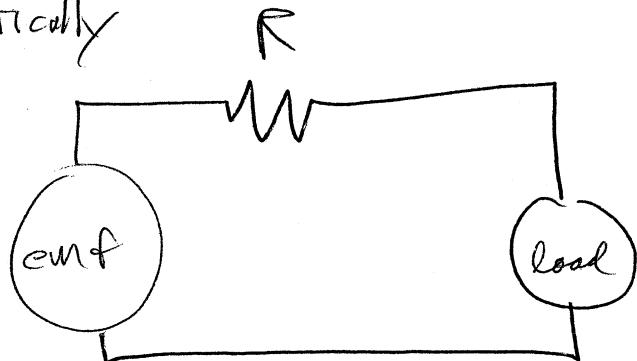

Our variables are

$$P, \epsilon, I, P_{\text{wire}}, R$$

$$\text{and } P_e, V_e$$

33-46]

and we have some relationships.

Say we take P, ϵ, R

as our independent
parameters.

→ These things are
can control
and adjust.

$$I = P/\epsilon$$

$$P_{\text{wire}} = I^2 R = \left(\frac{P}{\epsilon}\right)^2 R$$

$$\begin{aligned} P_e &= P - P_{\text{wire}} \\ &= P - \left(\frac{P}{\epsilon}\right)^2 R \end{aligned}$$

Note $\frac{dP_e}{dP} = 1 - 2\frac{P}{\epsilon^2}R \stackrel{?}{>} 0$

$P < \frac{1}{2} \frac{\epsilon^2}{R}$

So P_e increases with P up to $P = \frac{1}{2} \frac{\epsilon^2}{R}$

and

$$V_e = \frac{P_e}{I} = \frac{P_e}{\rho} \varepsilon$$

$$= \varepsilon - \left(\frac{\rho}{\varepsilon}\right) R$$

Say we don't care
what ε or V_e

we use. We can adjust
those (using transformers
to be exact).

If you fixed, P we want
smaller wire (wasted
energy)

larger P_e (useful energy)

33-48

then we can do
two things:

1) make R smaller
(obvious)

2) make E bigger
(less obvious)

— and, of course,
people try to do both
but there are practical
limits somehow.

— But high potential transmission
(is advantageous).

→ true for AC & DC.

(33-49)

So what ~~can~~ can
be done is step up potential
from ~~high~~ practical creation
potential to high potential
transmission

then step down potential
for practical potential use.

Historically the first
practical way to do this
was with AC and transformers,
and so AC won the
War of currents in the 1880s

Westinghouse & Tesla
General Edison.

33-50)

- But as I mentioned before,
it was never a complete
Victory

and HVDC

(High voltage DC)

has been used advantageously
for very long transmission
and might be the way of
the future for new advanced
grid.


Transformers

The essence is simple

Primary
coil

B-field. Secondary
coil

33-51

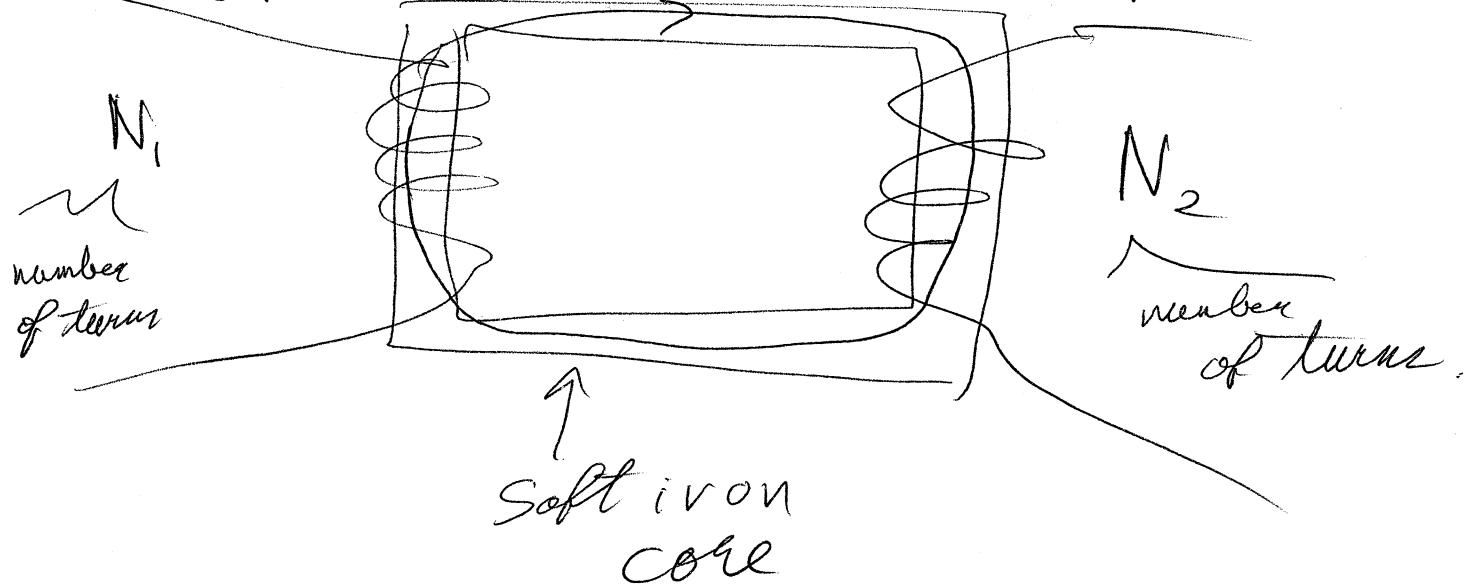

Ideally all the magnetic flux linked by one coil is linked by the other.

The soft iron core greatly enhances the magnetic flux and channels it from the primary to the secondary.

But modern transformer can transfer energy with $\geq 98\%$ efficiency (TM - 1004)

Both effects are actually important to transformer operation.

The field generated by a coil causes the air gap in the core greatly increases the field. But the channeling is the key point.

~~33 - 52~~

Potential drop across primary

$$V_1 = E_1 = N_1 \frac{d\Phi_1}{dt}$$

induced
emf
in 1

↑ ↑
number
of turns
in 1 ↓
↓
Φ, magnetic
flux in
1 turn.

drop
any
resky
negative
signs.

For secondary, the same

$$V_2 = E_2 = N_2 \frac{d\Phi_2}{dt}$$

Assuming ideal flux linkage
between two coils

$$\bar{\Phi}_1 = \bar{\Phi}_2 = \bar{\Phi}$$

$$\therefore \frac{E_1}{N_1} = \frac{d\bar{\Phi}}{dt} = \frac{E_2}{N_2}$$

$$\frac{E_1}{N_1} = \frac{E_2}{N_2}$$

$$\text{or } E_2 = \frac{N_1}{N_2} E_1$$

This one applies
at each instant

but one can take
an RMS ^{average} of it and
get the RMS form

$$\frac{E_1 \text{ RMS}}{N_1} = \frac{E_2 \text{ RMS}}{N_2}$$

~~These~~
But these are induced
emfs.

With no primary current
they are both zero.


33-54]

This is why transformers work with AC
where the current is changing all the time.

Let's assume I_1 is

~~sinusoidal~~
since $E_1 = \frac{d\Phi}{dt} \propto \frac{dI_1}{dt}$

E_1 ~~must be sinusoidal~~
as well

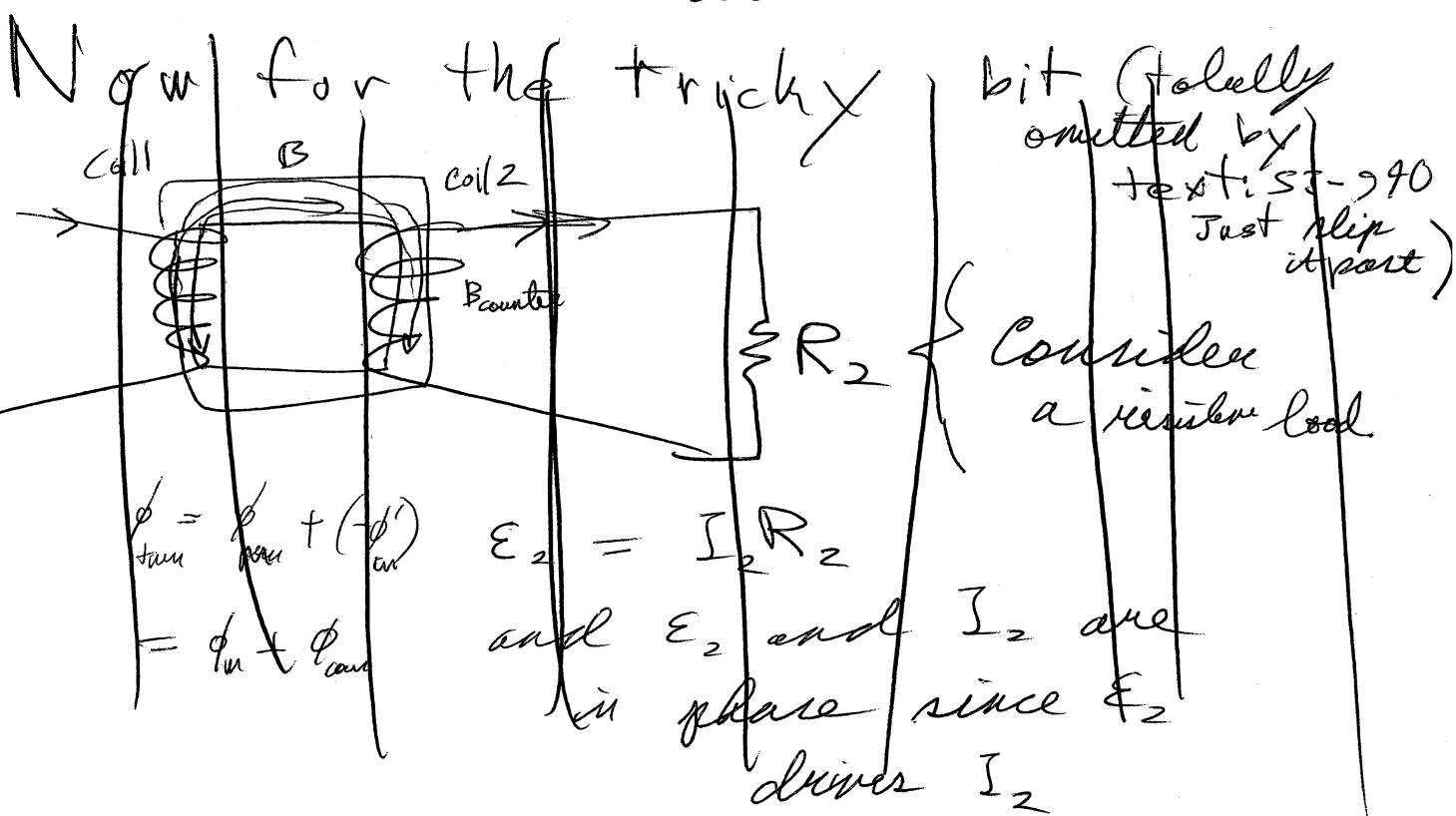

Now for a bit I can't prove — (TM-1005 gives an explanation but either it's defective or I am)

$$N_1 I_1 = N_2 I_2$$

at least ideally for sinusoidal currents & emfs.

→ The two currents are in phase — or 180° out of phase depending on how you look at the system — since the currents are in different circuits, it's a matter of perspective.

and these currents are in phase with their coils' emfs (ideally)

33-96

Do we have the ideal transformer equations

$$\textcircled{1} \quad \frac{E_1}{N_1} = \frac{E_2}{N_2}$$

$$\text{and } \textcircled{2} \quad N_1 I_1 = N_2 I_2$$

~~① + ② gives~~ ~~energy eq~~

$$\textcircled{3} \quad P_1 = E_1 I_1 = E_2 I_2 = P_2$$

consistent
with
energy
conservation

Power
out of coil 1

power
into coil 2

which
hold
ideally
at every
instant
for
~~AC~~
sinusoidal
 E_1 which
is the
driven.
with all
 E_1, E_2, I_1, I_2
in phase.

One can time average for in phase
sinusoids to get

$$P_{\text{avg}} = E_{1\text{rms}} I_{1\text{rms}} = E_{2\text{rms}} I_{2\text{rms}} = P_{\text{avg}}$$

— One can drop the RMS subscripts

if one knows what
one is talking about

33-57

(I generally like to drop
cluttering subscripts if one
knows what is meant from
context.)

Do we have three ideal transformer
equations.

→ real transformers aren't
quite ideal, but as mentioned
above $\approx 98\%$ energy transfer
is achievable with good ones (TM-1004).

One source of loss is eddy currents
in the iron core (W_{ik})

I assume
the metal
laminated
somehow to
make it a
poor conductor
~~-~~

→ but the core can be made of laminated soft iron
... & make it less conductive (TM-11114 note)

33-58]

Because of

$$\frac{E_1}{N_1} = \frac{E_2}{N_2}$$

or $E_2 = \frac{N_2}{N_1} E_1$

the ratio $\frac{N_2}{N_1}$ ~~can~~ allows
step-up $\frac{N_2}{N_1} > 1$

or
step-down $\frac{N_2}{N_1} < 1$

transformers

(on even step-level $\frac{N_2}{N_1} = 1$ transformer)

which may have no practical use)

33-59

Example 33.7

Power station needs to deliver 20 MW to a city

1.0 km

its generators create

$$\mathcal{E}_1 = 22 \text{ kV}$$

I have no idea how realistic these values are.

$$\frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{N_2}{N_1}$$

$$= \frac{230}{22}$$

$$\approx 10.5$$

step-up

and

then this is stepped-up to 230 kV for transmission.

The wire resistance is 2Ω .

$$P_1 = \mathcal{E}_1 I_1 = \mathcal{E}_2 I_2 = P_2$$

$$P_{\text{lost}} = I^2 R = \left(\frac{P_1}{\mathcal{E}_2}\right)^2 R$$

33-60]

$$= \left(\frac{20 \times 10^6}{230 \times 10^3} \right)^2 \cdot 2$$
$$\approx (10^2)^2 \cdot 2$$
$$= 2 \times 10^4 \text{ W}$$

So compared to 20 MW
= $2 \times 10^7 \text{ W}$
this is pretty small.

But what if there were no step-up.

$$P_{loss} = \left(\frac{P_i}{\epsilon_i} \right)^2 R$$
$$= \left(\frac{20 \times 10^6}{22 \times 10^3} \right)^2 \times 2$$
$$= 2 \times 10^6 = 2 \text{ MW}$$

which is a significant loss

about 10% of
the total transmission.

33-61

So high-voltage transmission
is good