
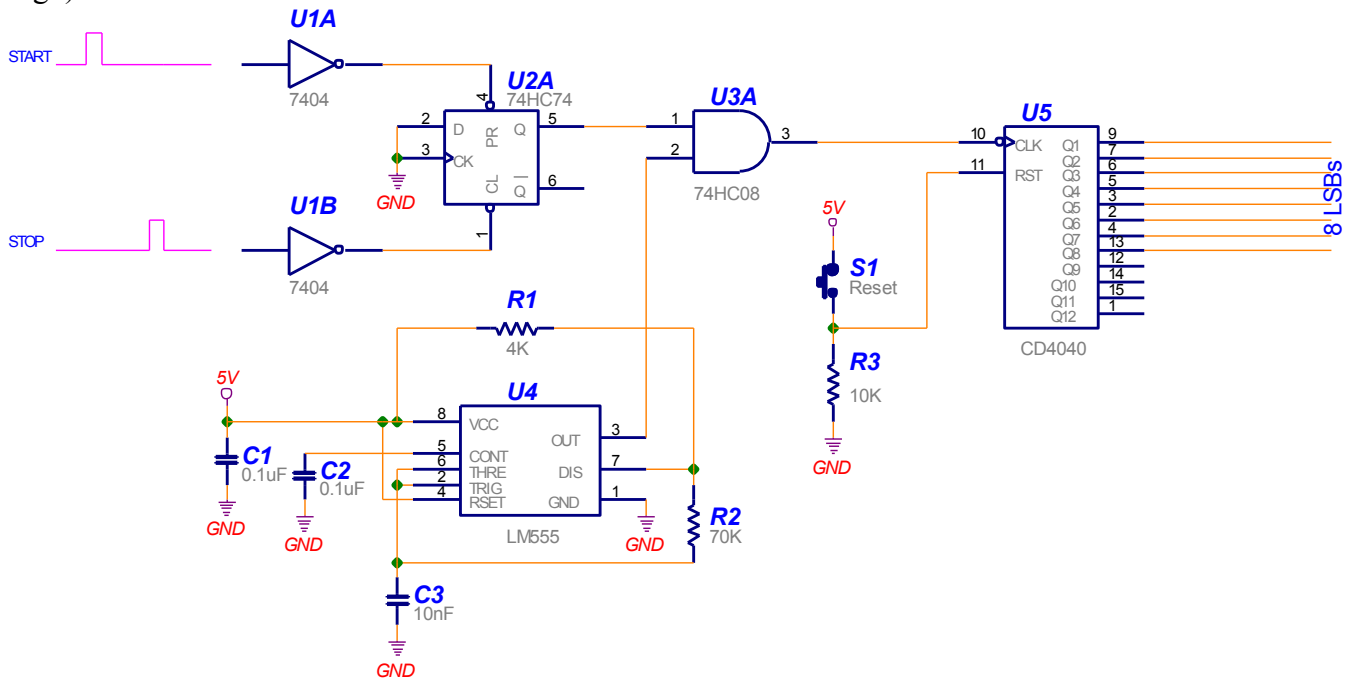


Homework #10 Solution

Since the preset and clear lines on the flip-flop are active low you need to invert the start and stop pulses since they're active high. In class we used a resistor to tie these lines high and brought them low by grounding the inputs. The Q output of the flip-flop will go high when the start pulse comes in and go low when the stop pulse comes in. The flip flop output is used to gate the clock to the counter on and off with an AND gate. The 555 timer is configured as an oscillator and the resistors and capacitor are chosen to oscillates at 1Khz. The counter is reset when the switch is pressed (the reset on the 4040 counter is active high).

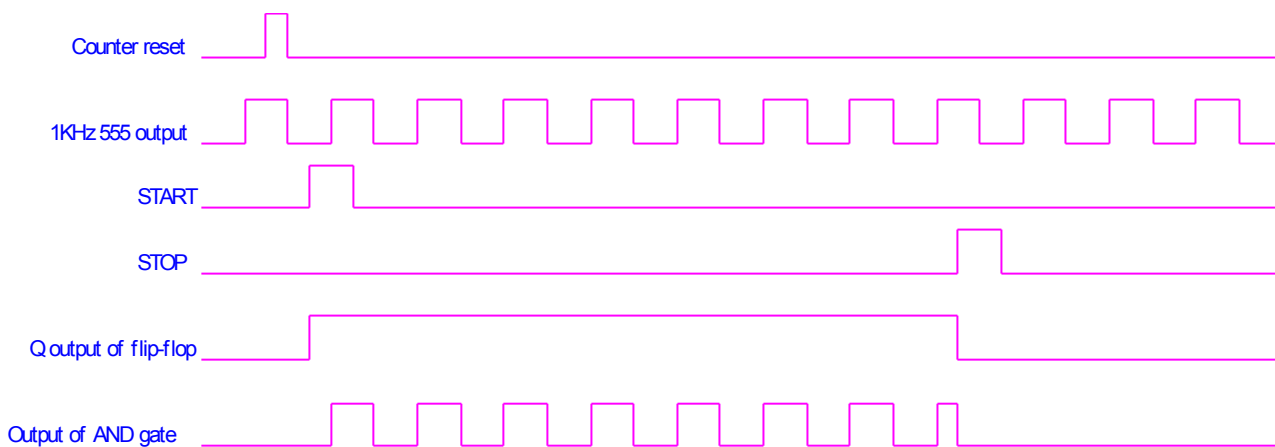

The timing diagram is shown below. The counter is reset, the start pulse comes in, the Q output of the flip-flop goes high, the counter starts counting, the stop pulse comes in, the Q output of the flip-flop goes low and the counter stops counting. The counter now has a count (1ms per count) representing the time between the start and stop pulses.



Binary output would be 00001000 (a count of 8, counts on falling edge)

