

## **HWK #2          FET Relay Driver**

**(Due 9/?/07)**

**Repeat HWK #1 but use a FET instead of a transistor.**

Again, make sure to label your parts so I can check the datasheet to make sure that the FET turns on enough (i.e.  $V_{DS}$  is small at the given  $V_{GS}$  and coil current).