
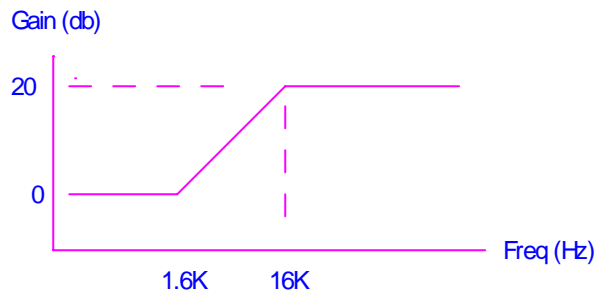
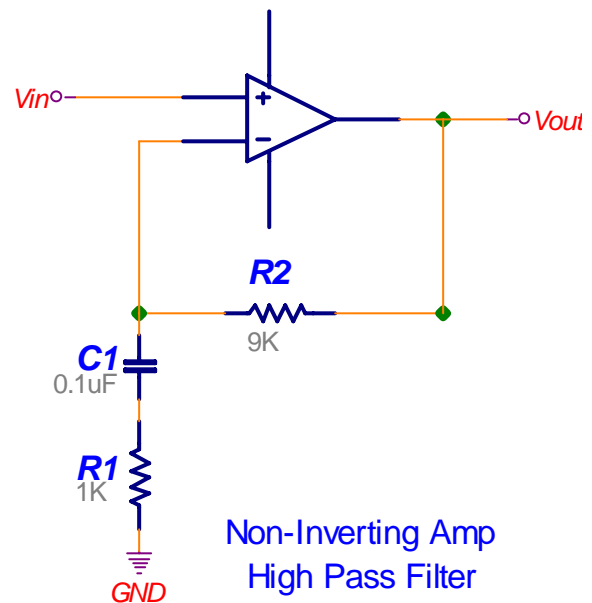
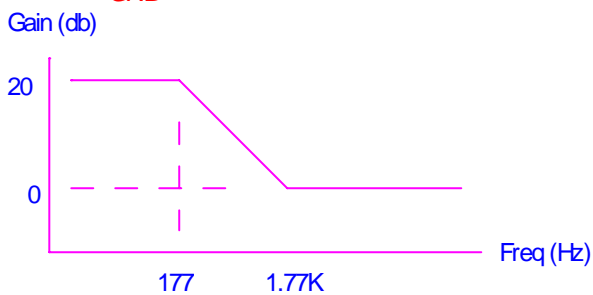


OP-AMP Filter Examples:

The two examples below show how adding a capacitor can change a non-inverting amplifier's frequency response. If the capacitor is removed you're left with a standard non-inverting amplifier with a gain of 10 ($1 + R2/R1$). Recall that the capacitor's impedance depends on frequency ($X_c = 1/(2\pi fC)$) and the corner frequency of an RC filter is $f_c = 1/(2\pi RC)$.

In the first circuit the capacitor is placed in parallel with the feedback resistor ($R2$). At low frequencies ($f \ll f_c$) the capacitor's impedance (X_c) is much greater than $R2$ and therefore the parallel combination of $R2$ & X_c is about $R2$ (i.e. $R2 \parallel X_c = R2$ when $f \ll f_c$). As frequency increases towards the corner frequency the impedance of the capacitor decreases and becomes comparable to that of the resistor. This lowers the impedance of the parallel combination of $R2$ & X_c and therefore the gain begins decreasing. When $f \gg f_c$, $R2 \parallel X_c = X_c$ causing the gain to drop. In this case the gain bottoms out at one since the gain equation is $1 + R2/R1$.




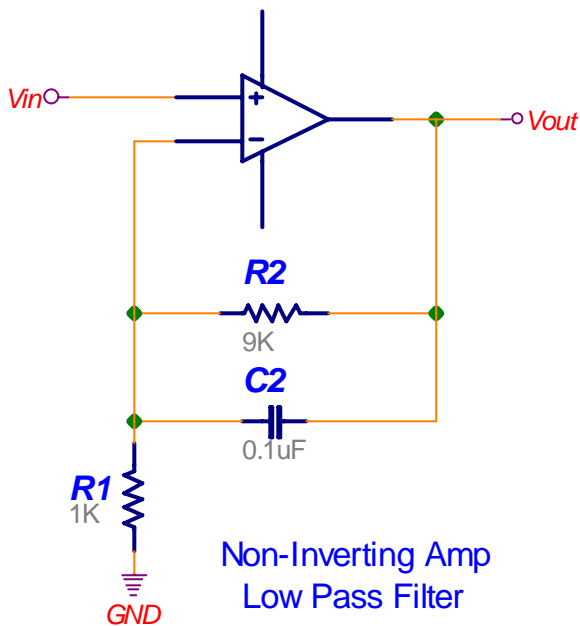
The second circuit has the capacitor in series with $R1$. When $f \ll f_c$ the capacitor's reactance is large and $R1 + X_c = X_c$. Therefore the gain is $1 + R2/X_c$ which = 1 when $X_c \gg R1$. When $f \gg f_c$ the capacitor's reactance is small and $R1 + X_c = R1$. Therefore the gain is $1 + R2/R1$ which = 10 when $X_c \ll R1$.







High and low pass filters can be made by adding capacitors to inverting amplifiers as well.

The first circuit is a low pass filter. At low frequencies the capacitors impedance is high, much higher than R_2 , and therefore doesn't affect the circuit ($X_C \parallel R_2 = R_2$). At high frequencies the capacitors impedance is low, much lower than R_2 , and therefore limits the impedance of the parallel combination ($X_C \parallel R_2 = X_C$). Since the gain equation for a non-inverting amp is $-R_2/R_1$ the gain doesn't bottom out at one. The gain continues to decrease as frequency increases beyond the cutoff frequency.

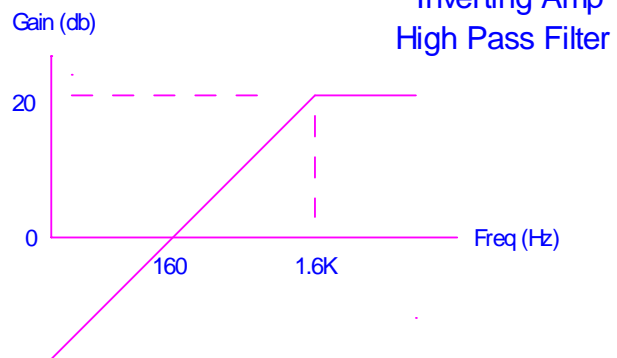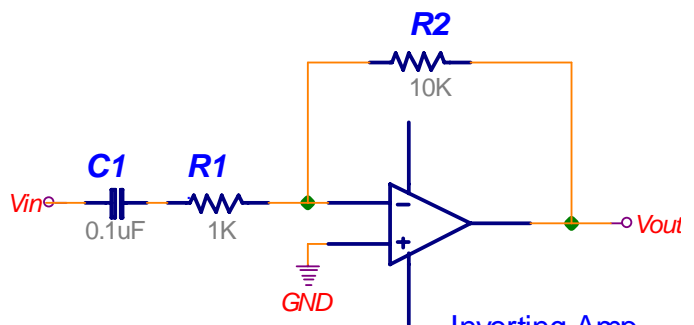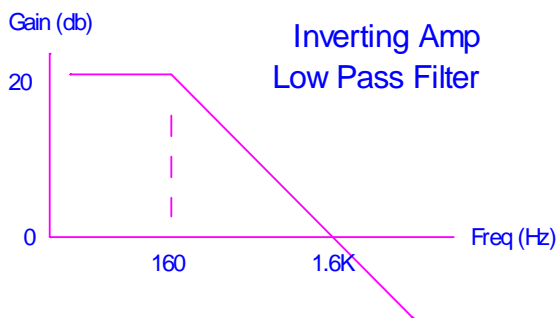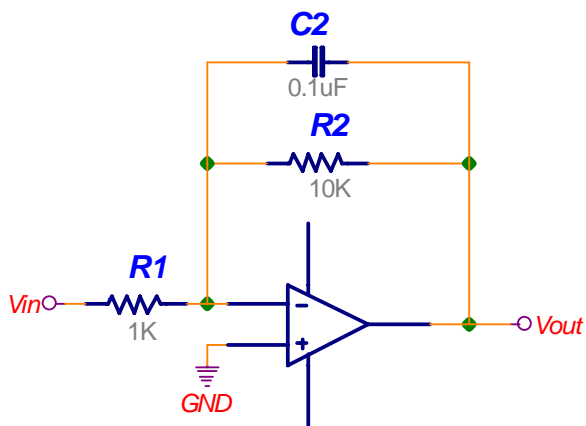The second circuit is a high pass filter. At low frequencies (below the cutoff frequency) the capacitors impedance is high, much higher than R_1 , and therefore $R_1 + X_C = X_C$. The gain is therefore R_2/X_C . At high frequencies the capacitors impedance is low, much lower than R_1 , and therefore $R_1 + X_C = R_1$. The gain is therefore R_2/R_1 .



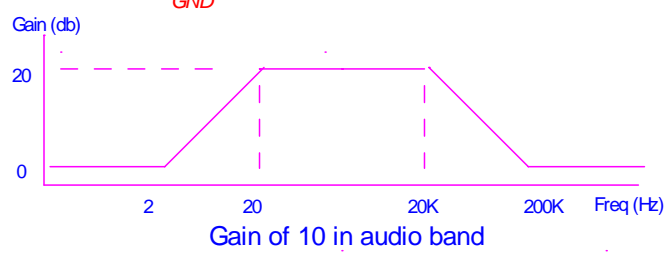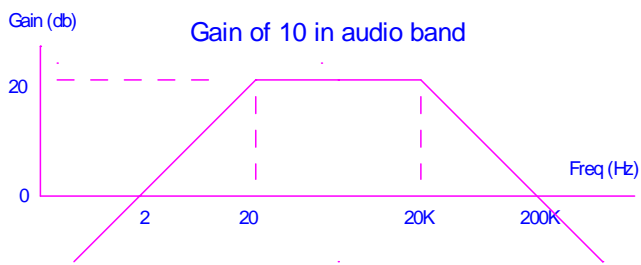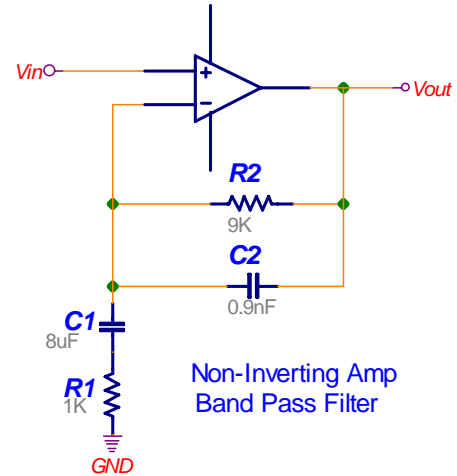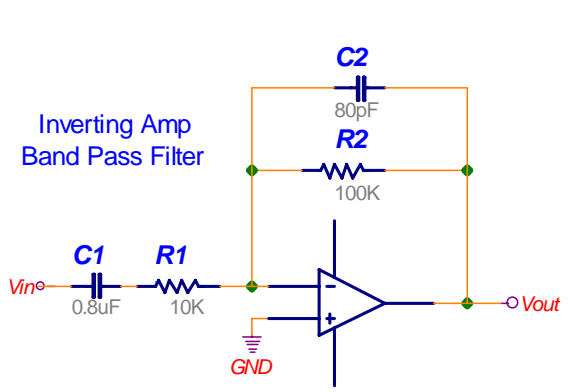The low pass and high pass filter can be combined into a band pass filter. In the examples below the corner frequencies were chosen to be the audio band (20Hz – 20KHz). Notice the difference in the gain outside of the pass band. The gain of the inverting amplifier continues to drop as you get farther away from the pass band. The gain of the non-inverting amplifier only drops to 1 (0db).



Each gain stage can be combined with another for a larger gain and a steeper roll-off of the frequency.

