

# Intro to Circuits

1

## 1) Intro

In a circuit, you have a closed system of flowing charge,





— Charge flows around about in the circuit, but never gets in or out.

In DC circuits (direct current circuits) the flow in most common modes <sup>of operation</sup> is everywhere steady-state.

In AC (alternating current) circuits, the flow in most common modes of operation is periodic or steady-state on average.

2

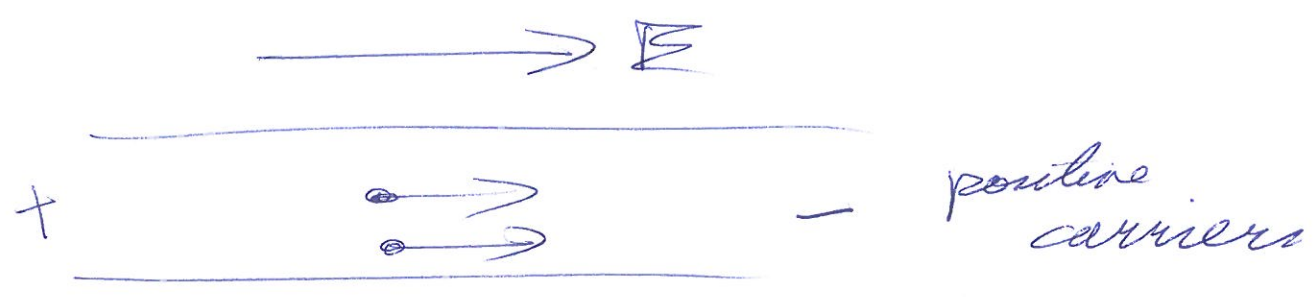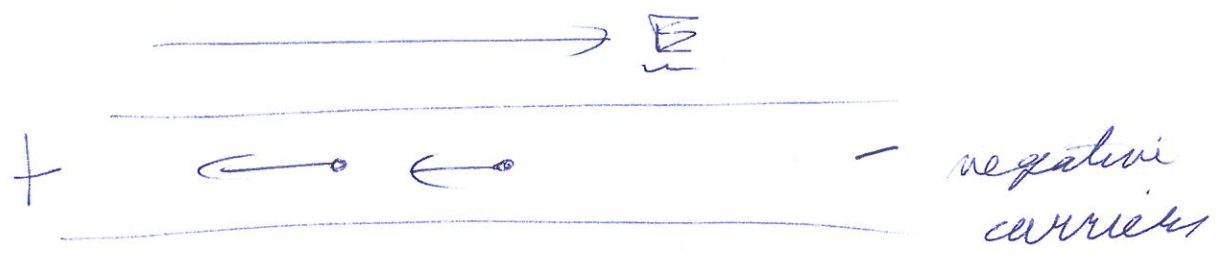In most parts of most circuits, the conductors are metals and the ~~carriers~~ charge carriers are electrons, which are negative.



In fact, in ~~most~~ for most effects, one can NOT tell if we have -ve carriers going to the left or +ve carriers going to the right.


It was NOT known 3  
~~or~~ before 1879, that metal  
carriers were negative  
(discovery then of magnetic  
Hall effect distinguished  
the sign of the carriers)

By then the convention  
had been long established  
to assume +ve carriers  
going from +ve to -ve  
and  
that convention has held.

So conventional current  
flows from +ve to -ve

4) Ben Franklin actually named positive and negative and he guessed wrong since it would have been convenient to call the most mobile carriers electrons as positive.

## 2) Definition of Current

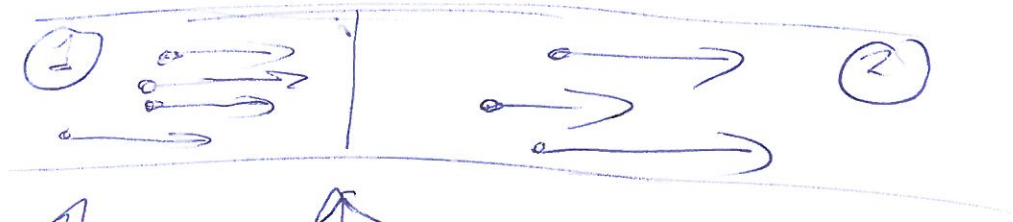

↑  
conducting path

↑ some imagined boundary

See  $\Delta q$  goes past  
someplace in time  $\Delta t$   
 ~~$I = \frac{\Delta q}{\Delta t}$~~  to the right.

Say  $\Delta q$  goes to the right across the boundary in time  $\Delta t$ .

$$I_{\text{Ave}} = \frac{\Delta q}{\Delta t}$$

$$I = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$

MKS  
unit of current  
C/s  
= 1 A

ampere  
often shortened to  
amp.

$\Delta q > 0$ , flows right,  $I > 0$

$\Delta q < 0$ , flows left,  $I < 0$

$\Delta q < 0$ , flows left,  $I > 0$

$\Delta q < 0$ , flow right,  $I < 0$

These sign conventions make sense.

Say  $Q$  is the net charge in section (2)

$I > 0$  means  $Q$  is increasing

$I < 0$  means  $Q$  is decreasing

6)

In simple DC circuits  
without ~~capacitors~~ capacitors  
or inductors,

we think of current  
in every branch as  
steady-state usually.

→ i.e.,  $I$  in each branch  
is not changing.

But of course, it must  
change when the circuit  
is changed.

— eg, (1) closing an open circuit

to allow flow in an ~~open~~ circuit

(2) opening a closed circuit  
— to stop flow in  
an ~~open~~ circuit.

These changes seem to happen instantaneously.

Question Why when you turn on a light, does the light come on instantaneously ~~seemingly~~ seemingly? Doesn't it take time for the electrons to get from switch to light.

ANS. The electrons are already in the wire and light.

Analogous to water in a pipe. Open a tap and water flows "instantly". The signal to go into motion propagates at about speed of sound in water.

— an electric field signal starts them in motion and that signal

8

travels at roughly  
the speed of light

$$c = 3 \times 10^8 \text{ m/s}$$

$$= 1 \text{ ft/ns}$$

### 3) Kirchoff's Laws

Kirchoff's laws are essential to understanding circuit behavior.

They are NOT fundamental laws, they are derived from more basic principles,

but historical reasons they are usually called "laws" rather than "rules".



There are two of them.


9

a) Kirchhoff's current law

AKA the node law or the junction law.

$$\sum_i I_i = 0$$

sum of currents into a node

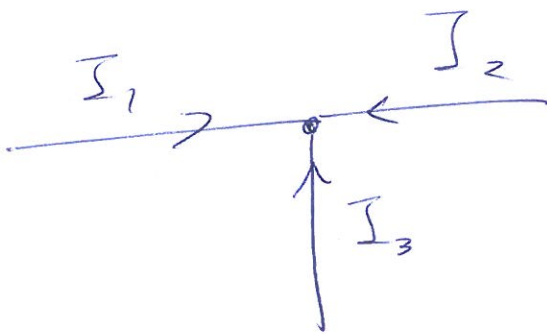

or junction equals zero

or  $\sum_i I_{i \text{ inflow}} = \sum_i I_{i \text{ outflow}}$

Given a no-charge build-up condition

~~Given steady state~~

~~conditions (no charge build up)~~

Not necessarily steady-state.

10

and conservation of  
charge

the current law must  
hold.

What if you have charge  
build ups?

Net charge build-ups  
are strongly resisted  
by the Coulomb force.

~~—~~ so small fluctuating ones  
happen all the time,  
but usually too small  
to notice.


— e.g., the end of a line  
wire will have a small  
build up.

At the highest level of accuracy, you might need to worry about them.

But for most circuit work, they are insignificant.

### Examples

a)

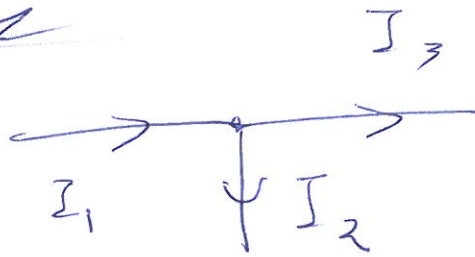

$$I_1 = 1 \text{ A}$$

$$I_2 = 2 \text{ A}$$


$$I_1 = I_2 + I_3$$

$$\begin{aligned} I_3 &= I_1 - I_2 \\ &= 1 - 2 = -1 \text{ A} \end{aligned}$$

In fact,  
the current,

12

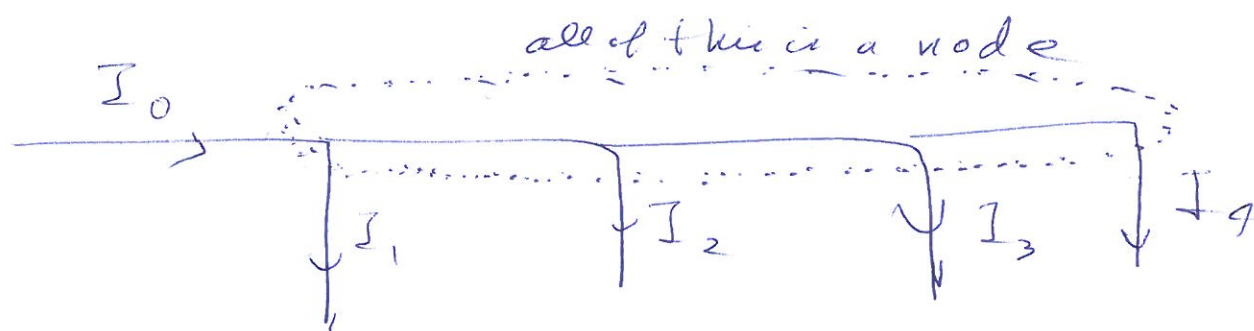If you choose the wrong direction for a current, you just get a negative answer which is fine.



$$I_1 = I_2 = I_3 = I_4 = 1A$$

$$I_0 = I_1 + I_2 + I_3 + I_4 \\ = 4A$$

# b) Kirchhoff's Voltage Law

Units of potential and emf are Volts (symbol V roman)

(AKA the loop law)

$$V = J/C$$

$$\sum_i \Delta V_i = 0$$



The changes in potential going around a closed loop sum to zero

riser and drops, but around a closed loop one always returns to the same elevation. Very analogous to potential!

$$\sum_i \Delta V_{\text{rises}} = \sum_i \Delta V_{\text{drops}}$$


It's more general to say "sum of emf's" rather than "sum of potentials" since the law works when

14

potentials strictly speaking don't exist as in a current loop caused by a Faraday law induced E-field.

But it's common to say potential and emfs take a bit of discussion that comes later.

Example

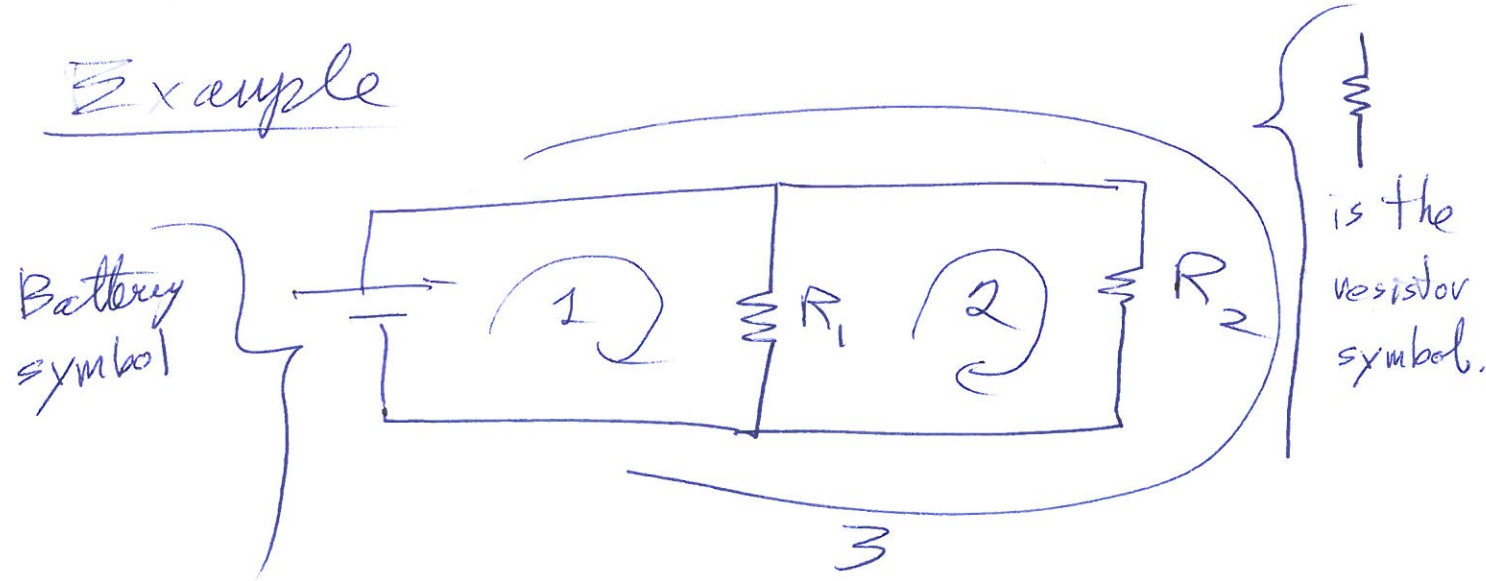

loop 1  $V_{Ba} = V_1$   
 rise across battery = drop across resistor 1

loop 2  $V_1 = V_2$   
 rise across resistor 1 = drop across resistor 2

loop 3  $V_{Ba} = V_2$   
 rise across battery = drop across resistor 2

Proof of Kirchoff's Voltage Law

Assume steady state.

Recall the work-kinetic-energy theorem


a classical proof and electrons in circuits are quantum objects  
 — but I think it can be made valid with some argument  
 — but eludes me.

16

$$\Delta KE = W$$

Change in  
Kinetic energy

work  
done on  
object.

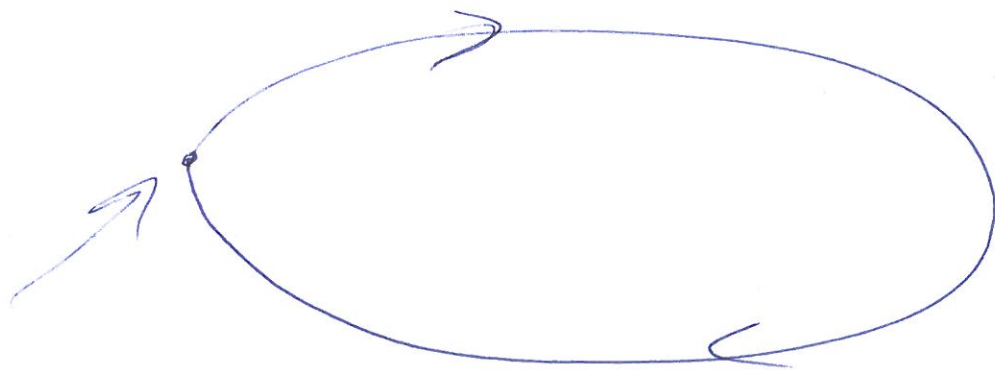

Now take a charge (conventional positive charge for simplicity) ~~an electron~~ around a closed loop.

You can imagine doing this in an instant in time.

Since the flow is steady state

$\Delta KE = 0$  for a closed loop.

and 
$$W = \sum_i q_i \mathcal{E}_i$$



$\mathcal{E}_i$  are the emfs

work done per unit charge by what ever set of ~~charges~~ forces encountered by charge.

formally emfs  
(electromotive forces  
although they  
are NOT forces)  
are defined at an instant  
in time

$$\mathcal{E} = \int_a^b \vec{f} \cdot d\vec{s}$$

force per unit charge

18

Since  $\Delta KE = 0$

$$0 = W = \sum_i q_i \mathcal{E}_i$$

$$\therefore \sum_i \mathcal{E}_i = 0$$

Usually (but not always)

$$\mathcal{E}_i = -V_i$$

$$\therefore \sum \mathcal{E}_i = 0$$

implies  $\sum_i V_i = 0$

What if there is no steady-state?

Well  $\Delta KE \neq 0$  then.

But in most circuit cases,

Again one can think of going around in an instant in time.

the nature of the system is

Flows of energy into electrons and outflows balance.

The electrons are in a sense glued to each other by ~~the~~ the need to constraint of near neutrality.

such that  $\Delta KE$  is very, very tiny compared to significant emfs.

Their density stays pretty constant.

$$\rho \approx 0$$

$$\sum_i \epsilon_i \approx 0 \text{ to excellent approximation}$$

There can't be any rapid speed-up and slow-downs.

$$\text{and then } \sum_i \Delta v_i = 0$$

in a single branch

Lots of KE will just not get into the electrons actually.

The situation is again like water under pressure, in a pipe.

There are exceptions of course like charged particles in a cyclotron, but those are NOT ordinary circuits.

The water is forced to respond collectively all over. Similarly with charge carriers where ~~speed of~~ near speed of light signaling keeps them in lockstep.

20

## 4) Using Kirchoff's laws


Given Kirchoff's laws and some formulae for the behavior of circuit devices you can solve for circuit unknowns (e.g., currents, potential drops, etc.) given sufficient knowns.

### Devices

#### a) Battery

The ideal battery maintains the same potential between its terminals no matter what current flows through the battery.

So if  $V_{Ba}$

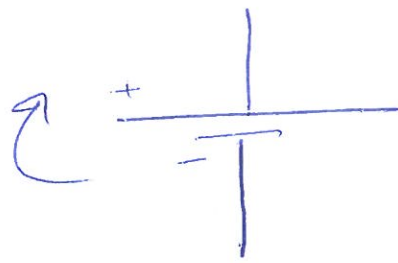

21

is the  
rise in  
potential  
across the

battery, it is constant.

Real batteries actually

have  $V_{Ba}$  decrease a little  
as current ~~flow~~  
increases.

b) IV devices

Such devices have

$$I = I(V)$$

current  
through


current  
through is  
a function of  
potential drop  
across.

This can be inverted to  $V = V(I)$   
usually.

22

Many such devices have  
IV curves that look  
like so

e.g.,  
light  
bulbs.

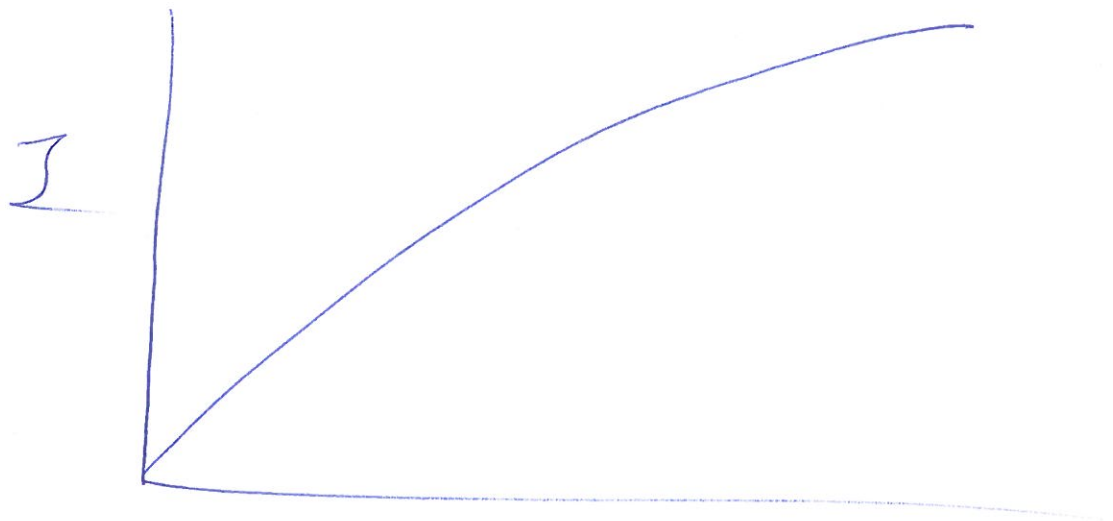

The resistance of an  $IV$  device  
is defined to be


$$R = \frac{V}{I} = \frac{V}{I(V)}$$

Not constant in general

Units of  $R$  are  $\text{V}/\text{Coulomb} = \text{V}/\text{C} = \Omega$   
special symbol capital Greek omega, the Ohm.
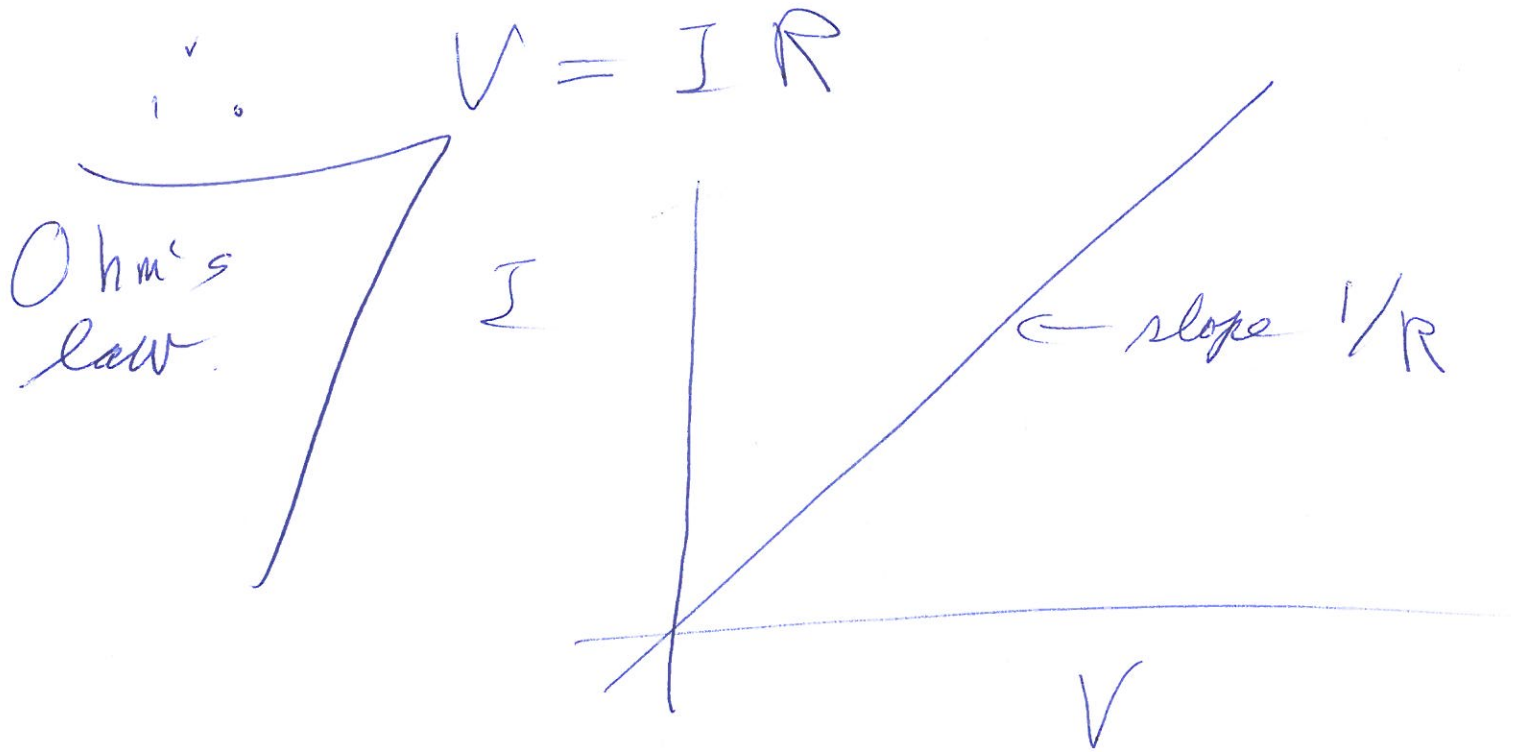
## c) Ohmic Devices

These are  $I$ - $V$  devices  
where  $R$  is a constant.



Usually such devices  
are resistors.

symbols




d) Others like capacitors  
and inductors

that will come up later  
(or earlier)

27

Examples

a)

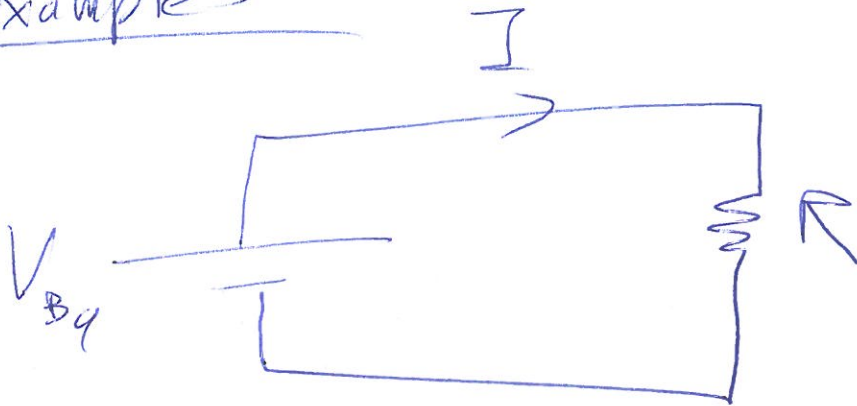Solve for current I.

$$V_{Ba} = V_R = IR$$

Kirchoff's  
Voltage  
law

drop  
across  
resistor

Ohm's law

$$I = V_{Ba} / R$$

b)






Solve for  $I_0, I_1, I_2$ . 25

$$V_{Ba} = I_1 R_1 = I_2 R_2$$

$$I_1 = \frac{V_{Ba}}{R_1}, \quad I_2 = \frac{V_{Ba}}{R_2}$$

$$I_0 = I_1 + I_2 = V_{Ba} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

c)

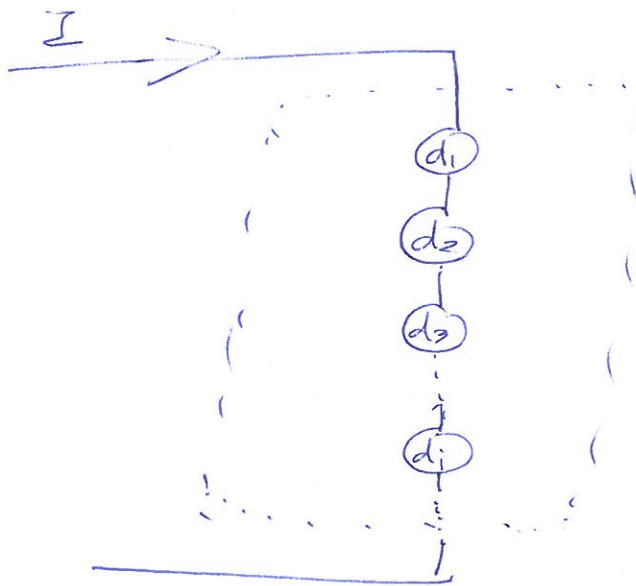

$d_i$  is an  
I-V device.

$$R_i = \frac{V_i}{I(V_i)}$$

What is  $R$  for the set of devices  
in series?

26

By definition

$$R = \frac{V_{\text{drop across all devices}}^{\text{the net}}}{I_{\text{current through the net}}}$$

$$= \frac{\sum_i V_i}{I} = \frac{\sum_i V_i(I)}{I}$$


which is the same for all devices.

If the devices are all ohmic

$$V_i = I R_i$$

and  $R = \sum_i R_i$

d)

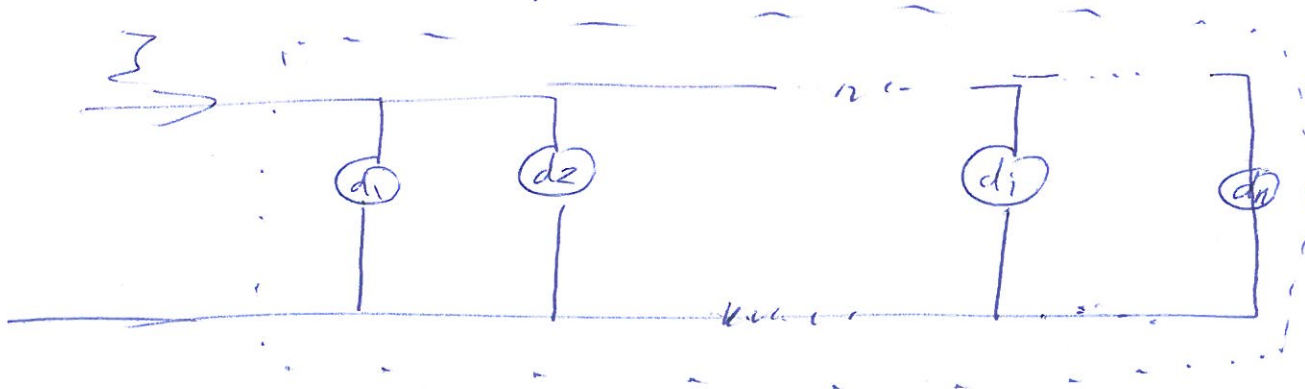

What is  $R$  for [ 27  
the set of IV devices  
in parallel?

$$R = \frac{V_{\text{drop across}}}{I_{\text{through}}} = \frac{V}{\sum_i I_i} = \frac{V}{\sum_i I_i(V)}$$

where  $V$  is any device.  
since all  $V_i$ 's are the same

If the devices are all ohmic,

$$I_i = V_i / R_i = V / R_i$$

$$\therefore R = \frac{V}{\sum_i V / R_i} = \frac{1}{\sum_i (1/R_i)}$$

$$\frac{1}{R} = \sum_i \frac{1}{R_i}$$


Note  $\frac{1}{R} \geq \text{Max}(\frac{1}{R_i})$

28

and no

$$R \leq \text{Min}(R_i)$$

e)

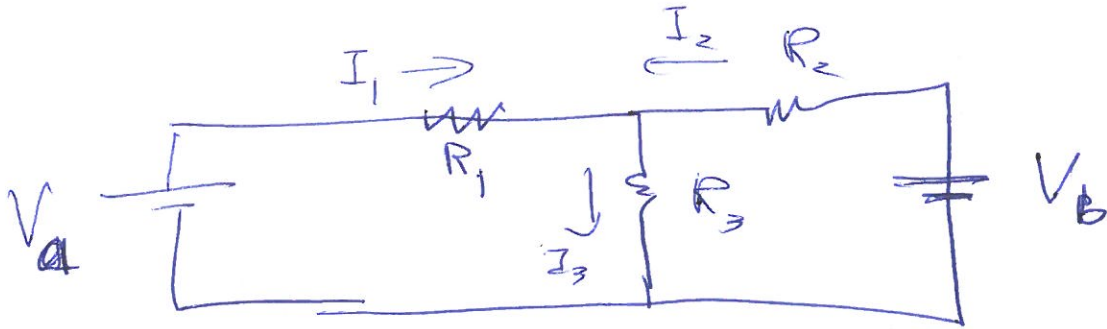Solve for  $I_1, I_2, I_3$ .

OK, it's very tough.

But exploiting symmetry makes it tractable.

Three equations and three unknowns. A solution can be found.

$$I_3 = I_1 + I_2$$

$$I_1 R_1 + I_3 R_3 = V_a$$

$$I_2 R_2 + I_3 R_3 = V_b$$

- eliminating  $I_2$  preserves symmetry

29

$$I_1 R_1 + (I_1 + I_2) R_3 = V_a$$

$$I_2 R_2 + (I_1 + I_2) R_3 = V_b$$

$$I_1 (R_1 + R_3) + I_2 R_3 = V_a$$

$$I_2 (R_2 + R_3) + I_1 R_3 = V_b$$

$$I_2 = \frac{V_b - I_1 R_3}{R_2 + R_3}$$

$$\therefore I_1 (R_1 + R_3) + \left( \frac{V_b - I_1 R_3}{R_2 + R_3} \right) R_3 = V_a$$

$$I_1 \left[ R_1 + R_3 - \frac{R_3^2}{R_2 + R_3} \right] = V_a - \frac{V_b R_3}{R_2 + R_3}$$

$$I_1 \left[ \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 + R_3} \right] = V_a - \frac{V_b R_3}{R_2 + R_3}$$

$$I_1 = \frac{V_a (R_2 + R_3) - V_b R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

30

$$I_1 = \frac{V_a(R_2 + R_3) - V_b R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

By symmetry ( $I_1$  and  $I_2$  are symmetrical in circuit and no just interchange 1 & 2 indexes)

$$I_2 = \frac{V_b(R_1 + R_3) - V_a R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

~~$$I_3 = \frac{(V_a + V_b) R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$~~

$$I_3 = \frac{(V_a + V_b) R_3 + V_a R_2 + V_b R_1 - (V_a + V_b) R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$= \frac{V_a R_2 + V_b R_1}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

Special Cases

$$R_3 \rightarrow \infty \quad I_1 = \frac{V_a - V_b}{R_1 + R_2}, \quad I_2 = \frac{V_b - V_a}{R_1 + R_2}, \quad I_3 = 0$$

$R_3 \rightarrow 0$ ,  $I_1 = V_a/R_1$ ,  $I_2 = V_b/R_2$ ,  $I_3 = \frac{V_a}{R_1} + \frac{V_b}{R_2}$   
which are all what one would expect,

# 5) Power

(3)

In general power is energy transferred per unit time.

$$P = \lim_{\Delta t \rightarrow 0} \frac{\Delta E}{\Delta t} = \frac{dE}{dt}$$

$$\text{If } \Delta E = \Delta q V,$$

$$P = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} V = \frac{dq}{dt} V$$

$$P = IV$$

a very general formula

The power transferred is the current through a device times the

the potential rise/drop  
across it.

What are the sign conventions?

Well whatever you like  
as long as you know  
what is happening.

Example

In a battery

$$P = I V_{\text{rise}}$$

is the power into  
circuit

and also the power  
out of battery  
chemical  
store.



# Power in resistors

33

$$P = I_{\text{current through}} V_{\text{drop across}}$$

or  $P = IV$

but using Ohm's law  $V = IR$

$$P = IV = I^2 R = \frac{V^2}{R}$$

only for resistors

— well actually they will be valid for any  $IV$  device, but since  $R$  is NOT constant, they are NOT too useful in those cases.

34)

## Energy conservation

$$P_{in} = P_{out}$$

for whole circuit                      for whole circuit

assuming negligible  
KE for electrons.

— We built this in with  
Kirchhoff's laws actually

and there seems no  
simple alternative  
proof.

### 6) Practicalities

In this lab one  
assumes the ~~the~~  
bulbs are OHMIC  
(even though they  
are NOT).

The  
Voltage  
law  
nearly  
builds  
in energy  
conservation  
for  
quasi-steady  
state.