

Electrical Resistance

1

1) I V Devices

An I V device is one where

$$I = I(V)$$

↑
current through it

↑
~~V~~
potential drop across.

Thus I is a function of V and often the function can be inverted to

give $V = V(I)$

(i.e., V is a function of I)

2) Recall power transferred
in many devices is

$$P = I V$$

current through ~~Potential~~ potential change across

∴ For an $I V$ device

$$P = I(V) V$$


or

$$P = I V(I)$$

2) Non- $I V$ device

Here we just give 3 important examples.

a) Ideal Battery

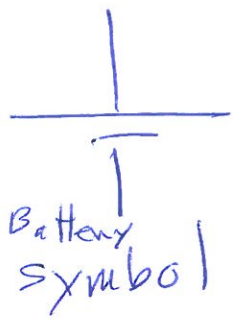

$$V_{\text{Battery}} = \text{Constant}$$


3

no matter what
current flows through.

h) Capacitor

$$V = \frac{Q}{C}$$

Potential
drop across

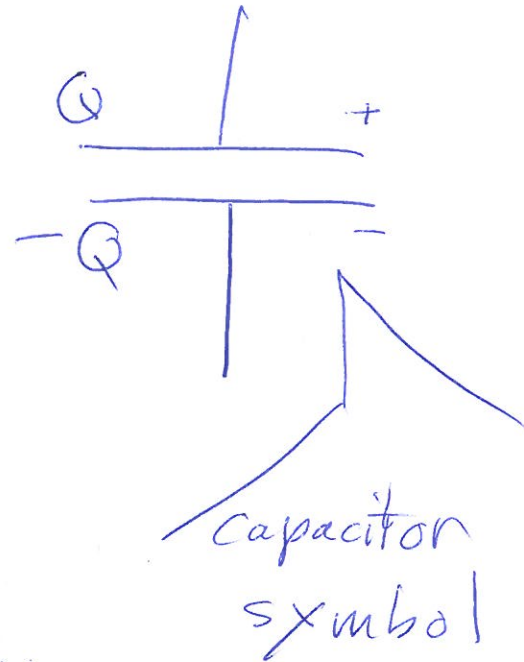

Q is the capacitor
charge

(i.e., the charge on the
positive plate)


There is $-Q$ on the
negative plate in
ordinary operation.

4

C is the capacitance which ideally depends only on geometry of plates and the dielectric in which the capacitor is embedded.

— Capacitor potential depends on charge on not current through.

c) Inductor

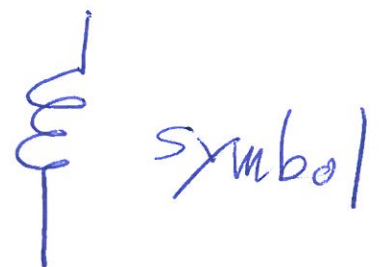


$$V = L \frac{dI}{dt}$$



potential drop across

~~per~~
~~probability~~

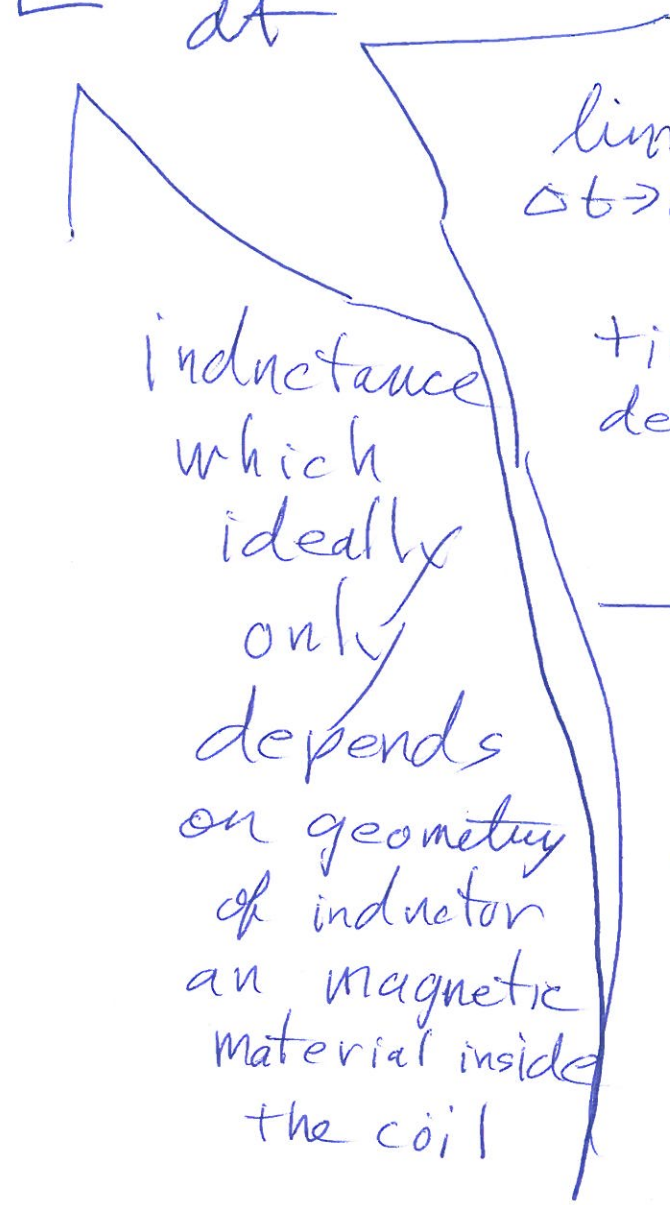

inductance which ideally only depends on geometry of inductor and magnetic material inside the coil

$$\lim_{\Delta t \rightarrow 0} \frac{\Delta I}{\Delta t}$$

time derivative of current.

— rate of change of current with time.

So Potential change across depends on derivative of current, not current,


6

3) IV curves

(AKA current-voltage characteristic)

For IV devices,

one can plot IV curves

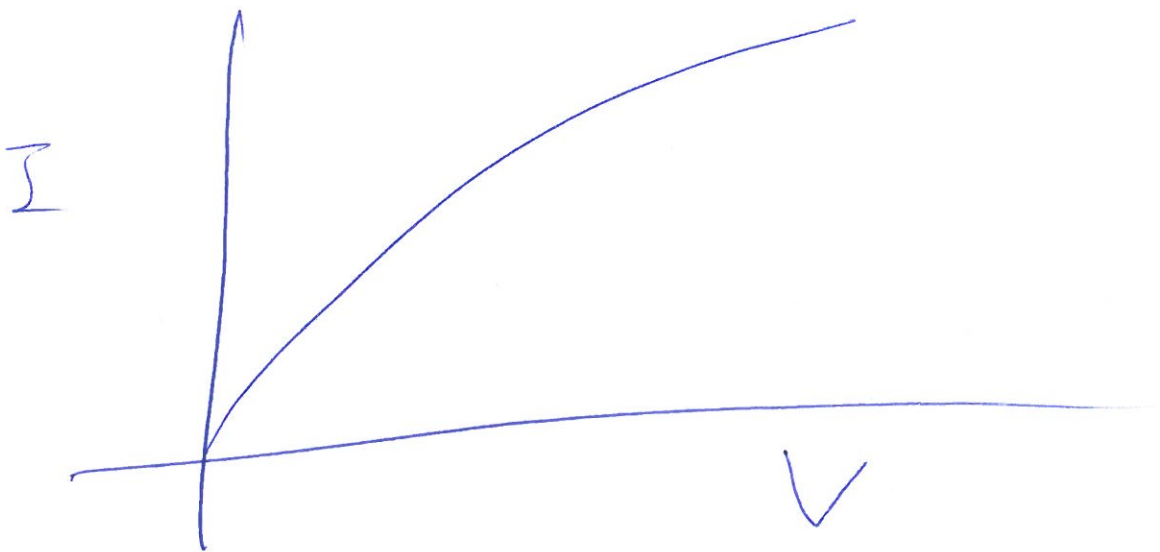


~~— a light bulb~~

— an incandescent light bulb

~~might~~ can have curve something like this.

⊙
symbol

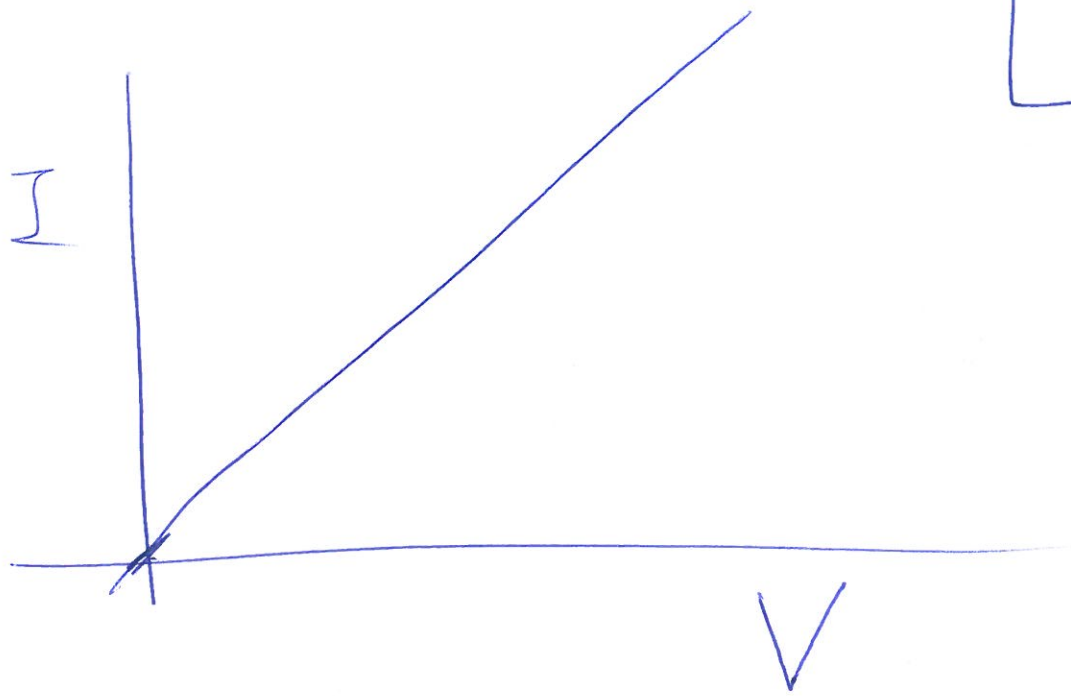

— a resistor has an I V like this.



symbol

A) Resistance

— Resistance can be defined for I V devices

8

$$R = \frac{V}{I} = \frac{V}{I(V)}$$

$$\text{unit of } R = \frac{\text{Volt}}{\text{Ampere}}$$

$$= \frac{V}{C/s}$$





$$= \frac{J \cdot s}{C^2}$$

$$= \Omega, \text{ the ohm}$$

It has its own
name and symbol



then

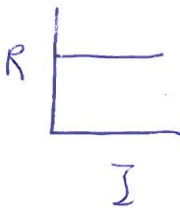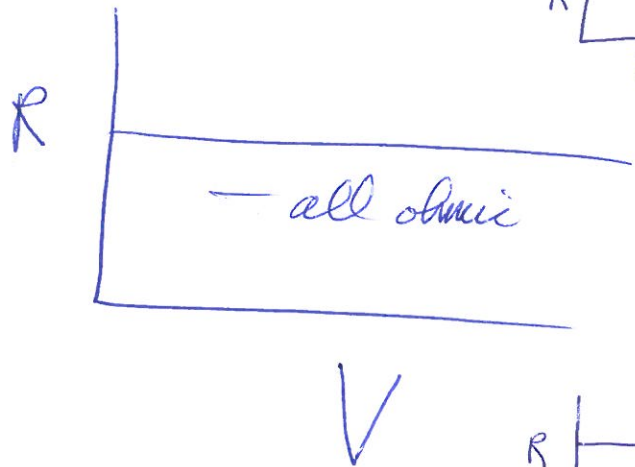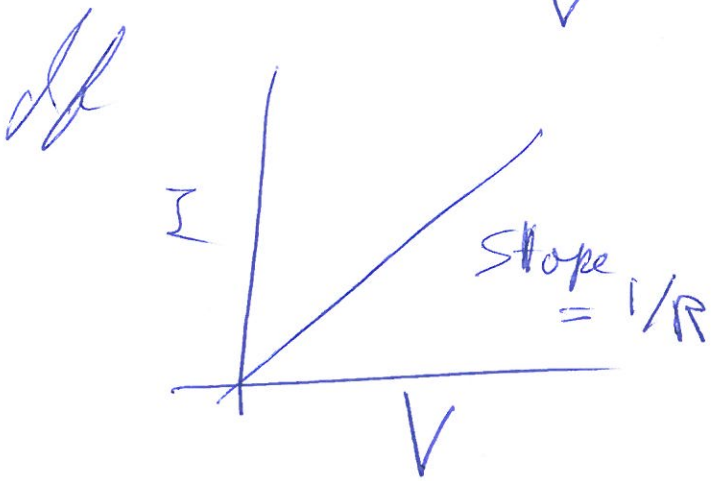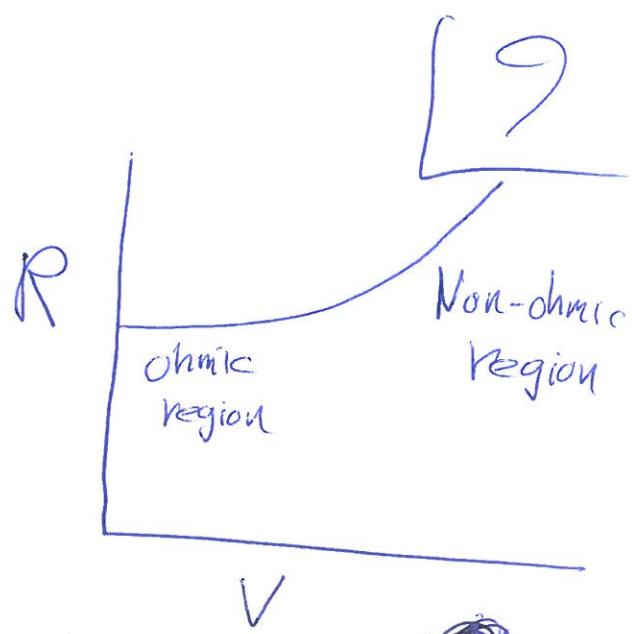

Ohmic devices have constant R .

- a resistor is an ohmic device
- a light bulb is NOT.

10

But the distinction is
NOT hard in reality

— Non-ohmic devices are
often ohmic over
some range ~~usually~~
usually at very
low ~~pot~~ potential

— Ohmic devices will
behave non-ohmically
at high enough potential.

5) Resistances in Series & Parallel

— Note resistances, and

So these results



are NOT just

for resistors

or other ohmic devices.


They apply to all IV devices.

Series

$$V = \sum_i V_i$$

drop
across
all

drop
across
device I

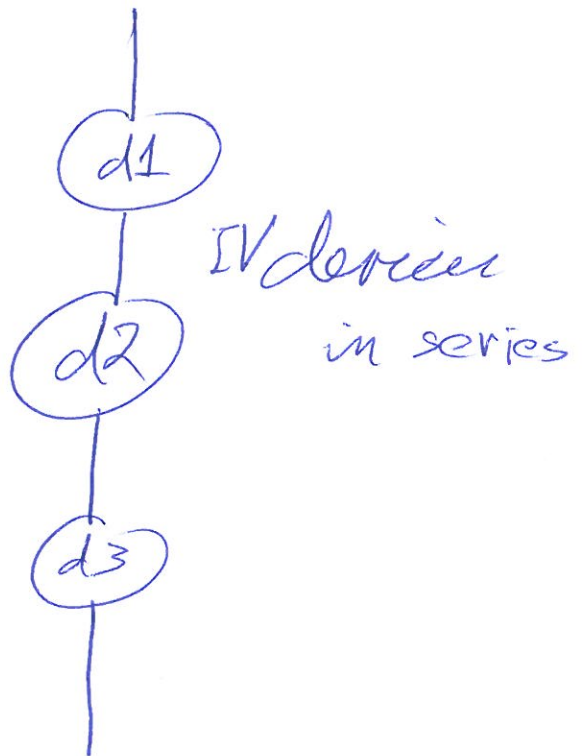

The current I is the
same through all

$$\therefore IR = \sum_i IR_i$$

by Kirchhoff's
current
law.

12) and so

$$R = \sum R_i$$


resistance
across
net device

resistance of
individual devices

If N
identical
~~resistors~~
resistors
 $R = NR_i$

Parallel

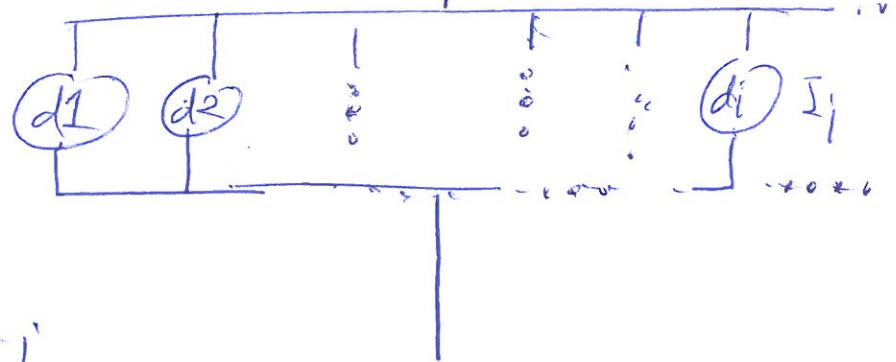Kirchhoff's
voltage law
applies to
each loop.



$$I = \sum I_i$$

current
through
net device

current
through device i

Potential drop V is the same
across all devices.

by Kirchhoff's Voltage
law applied to each loop of the
~~device~~ array.

$$\frac{I}{V} = \sum_i \frac{I_i}{V}$$

13

$$\frac{1}{R} = \sum_i \frac{1}{R_i}$$

Note $\frac{1}{R} \geq \max\left(\frac{1}{R_i}\right)$

$$\therefore R \leq \min(R_i)$$

Case of only 2 resistors

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

Case of N identical resistors


$$\frac{1}{R} = \sum \frac{1}{R_i} = \frac{N}{R_i}$$

$$\text{or } R = \frac{R_i}{N}$$

14

6) Current through a light bulb
like I V device

Say

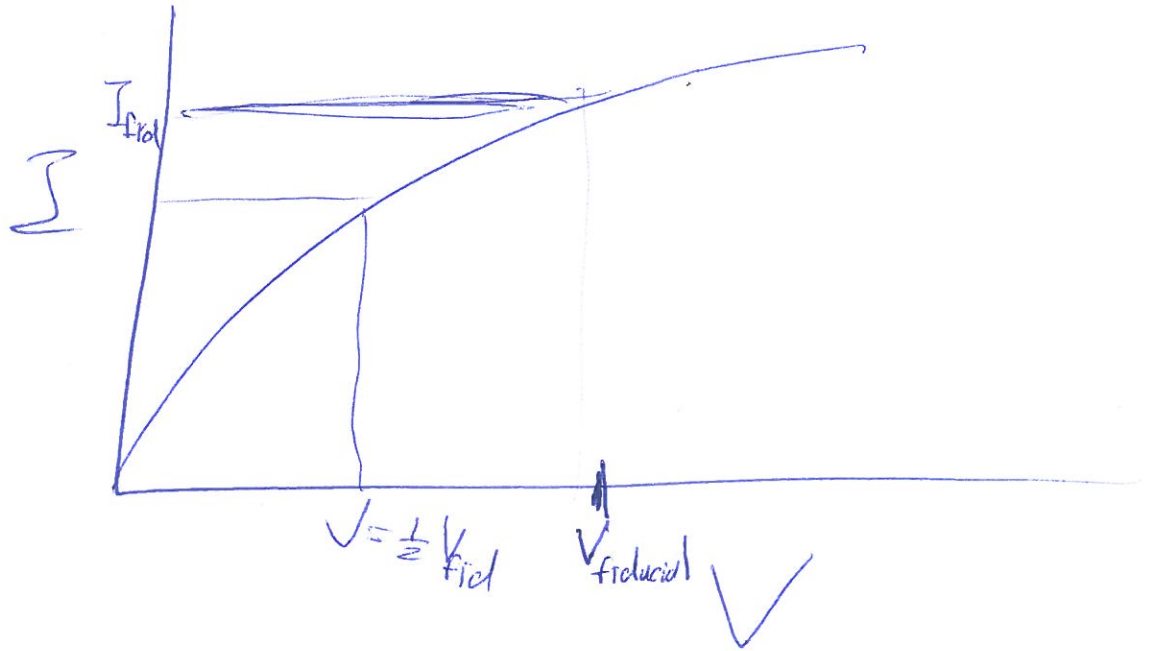

$$I_{\text{fiducial}} = I(V_{\text{fiducial}})$$

Examples


$$V = \frac{1}{2} V_{\text{fid}} , \quad I > \frac{1}{2} I_{\text{fid}}$$

$$V = \frac{2}{3} V_{\text{fid}} , \quad I > \frac{2}{3} I_{\text{fid}}$$


$$V = \frac{1}{n} V_{\text{fid}} , \quad I > \frac{1}{n} I_{\text{fid}}$$

$$V = n V_{fid} \quad , \quad I = n I_{fid} \quad \boxed{15}$$

Question

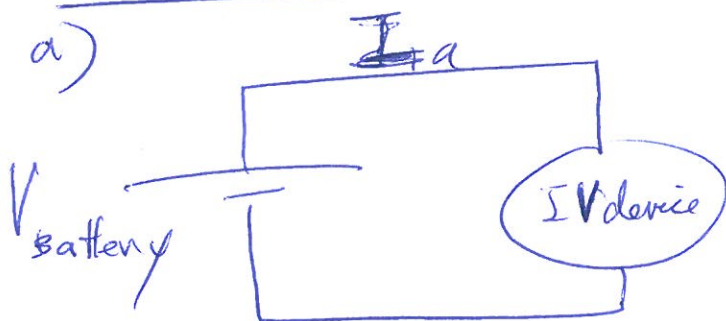

$$V_{device} = ?$$

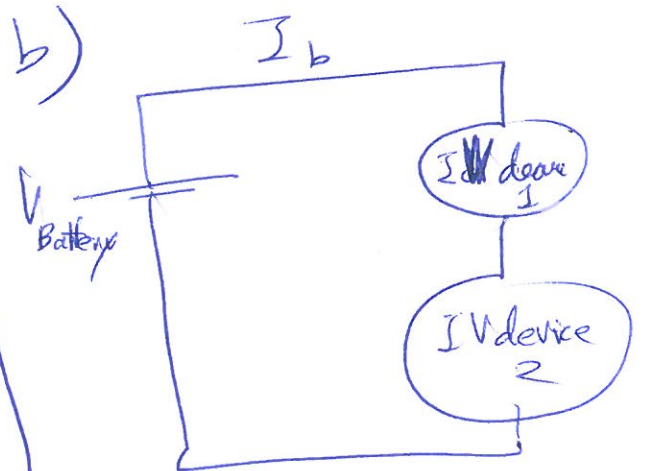

The devices are identical

$$V_{device 1} = ?$$

~~IV device 1~~

$$I_b = x I_a$$

What is x ?

16


7) Nichrome Wire Resistance

Measurement

Nichrome

alloy of nickel
and chromium
— typically 80% Ni
20% Cr
by mass

setup

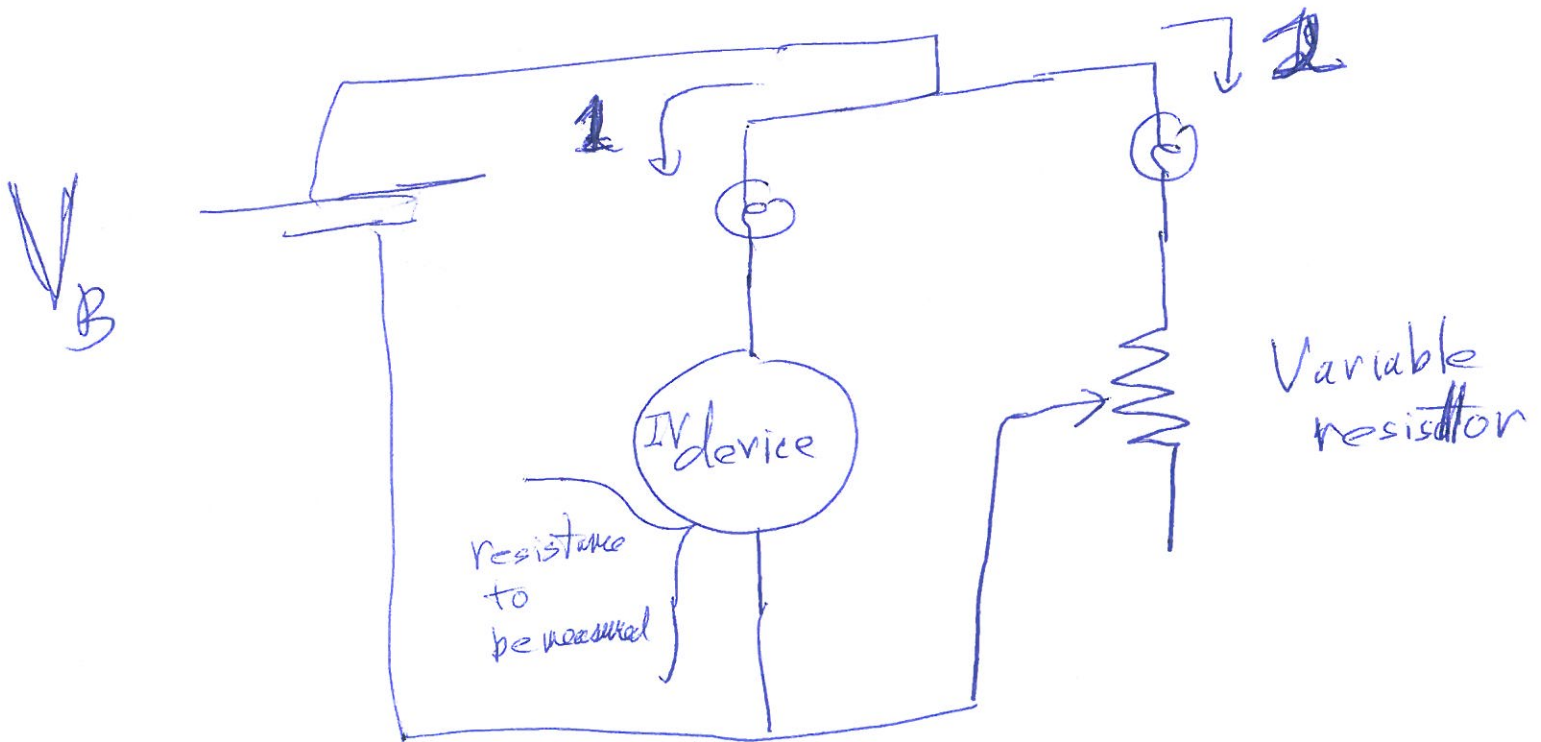

— the two bulbs are identical.

— The variable ~~resistor~~ resistor is a length of NiCr wire with a contact ~~on~~ that slides along the wire

↳ the length of wire is proportional to the resistance.

When brightness of bulbs are equal

$$R_{\text{device}} = R_{\text{wire}}$$

18

Proof~~Given~~

$$B_1 = B_2$$

~~power~~

$$B = \text{brightness} \\ = B(P)$$

$$\therefore P_1 = P_2 \quad \text{power in bulbs}$$

$$I_1 V_1 = I_2 V_2$$

$$I(V_1) V_1 = I(V_2) V_2$$

$$\therefore I_1 = I_2$$

$$\therefore V_1 = V_2$$

Also from Kirchhoff's ~~voltage~~ law

$$V_B = V_1 + V_{\text{device}}$$

$$V_B = V_2 + V_{\text{wire}}$$

When equal brightness $V_1 = V_2$ (19)

and therefore $V_{\text{device}} = V_{\text{wire}}$

$$\text{Now } R_{\text{device}} = \frac{V_{\text{device}}}{I_1} = \frac{V_{\text{wire}}}{I_2} = R_{\text{wire}}$$


$$\therefore R_{\text{device}} = R_{\text{wire}}$$

Judging Equal Brightness

is hard

— slide the contact on
the wire between
locations of clearly
unequal brightness
and take difference

20

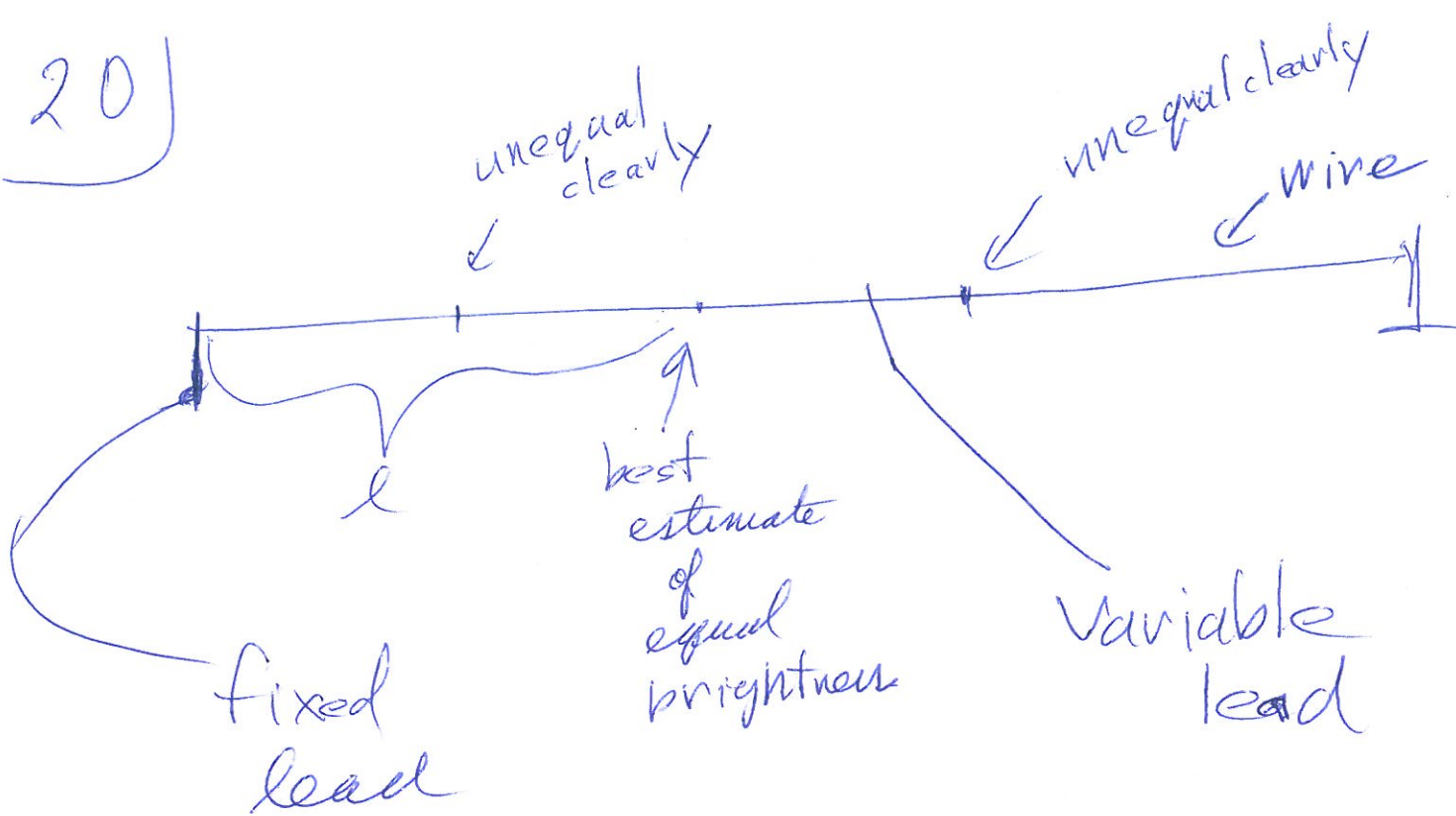

$$R_{\text{wire}} = l * \underbrace{r}_{\text{resistance per unit length}}$$

8) Practicalities of Lab


- a) Dim overhead lights so that judging brightness is better.

b) Do NOT alligator 21
clip the wire.

It can snap.

Just touch with the
variable lead.

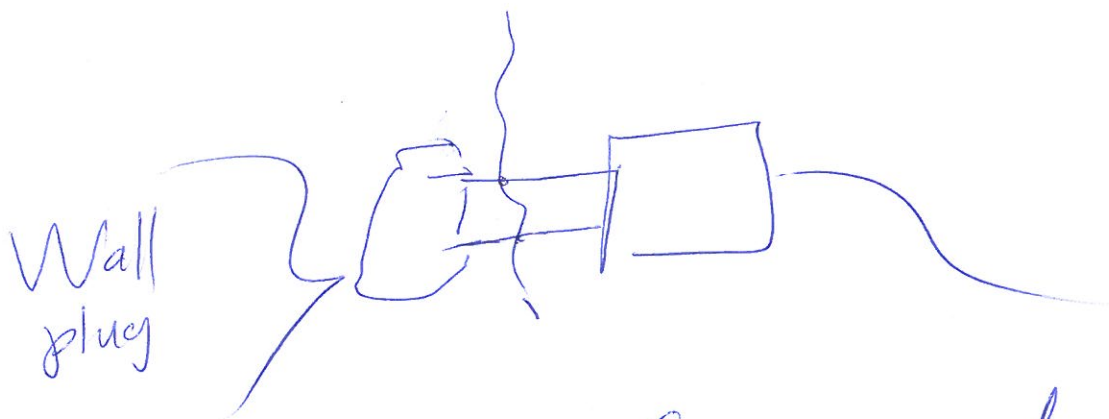
c) Don't let a
dangling NiCr wire
contact plug prongs



— a large and
slightly dangerous
current can flow.
between prongs

22)

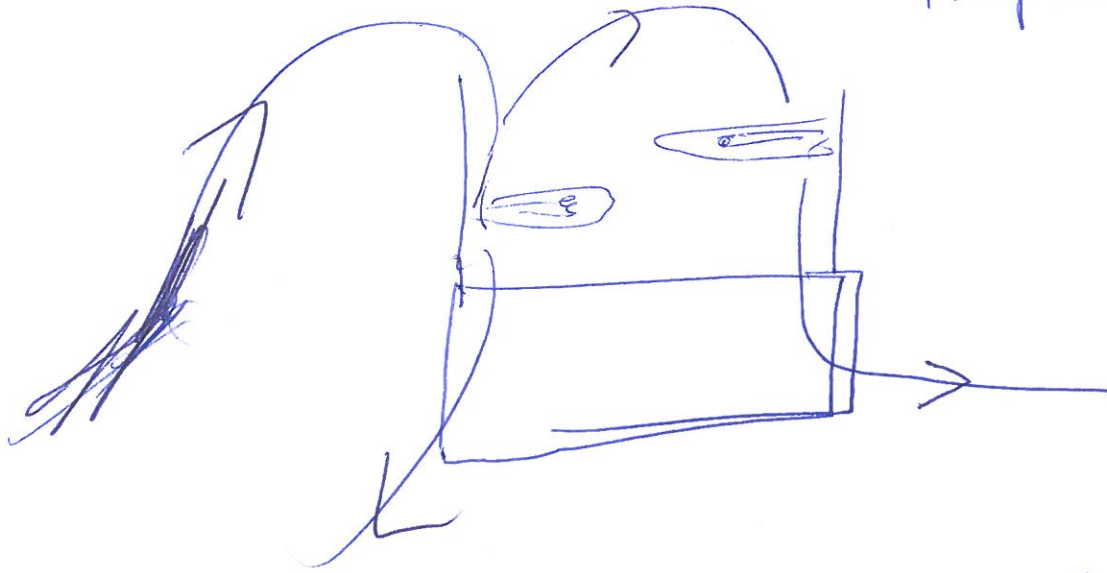d) Use bulb holders
for parallel bulbs
(if they arn't
impossible)



e) Constructed Circuits

wires
curling
all
over,
etc,

often do not look
much like
schematic diagrams,

— You should try to
make your circuit

look as transparent 23
as reasonably
possible.

In any case make the
right connections

∥ The battery's connected to the node
The node's connected to the bulbs

The bulb 1 is connected
to the device

The bulb 2 is connected to
the wire

The ...


and that's how the
circuit is made."

24)

9) Ohmmeters

Our Ohmmeters (a function of the multimeter) read resistance for a device

NOT in ~~the~~ circuit.

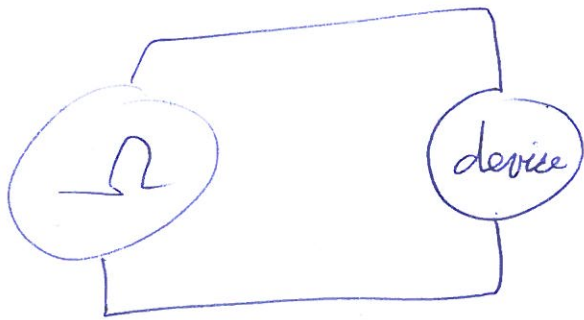

The ohmmeter itself sets a circuit and passes a fixed ~~or~~ small current I through the device and reads the potential drop across the device.

$$R_{\text{ohmmeter}} = \frac{V}{I_{\text{fixed}}}$$

The ohmmeter
assumes I_{fixed} .

If another current I_{other}
is running through
the device, then V
does NOT correspond
to I_{fixed} but ~~not~~
to $I_{\text{fixed}} + I_{\text{other}}$

$$R_{\text{ohmmeter}} = \frac{V}{I_{\text{fixed}}} \neq \frac{V}{I_{\text{fixed}} + I_{\text{other}}} = R_{\text{actual}}$$

So the ohmmeter
gives the
wrong Resistance
in this case.

26)

Ohmmeters only read
small current, small
potential drop
resistance R_{small} .

If the device is Ohmic

$$R_{\text{actual}} = R_{\text{small}} \text{ for all cases}$$

(where the
device
behaves
ohmically)

If the device is
non-ohmic,

$$R_{\text{actual}} \neq R_{\text{small}} \text{ only for } I_{\text{fixed}}$$

and

$R_{\text{actual}} \neq R_{\text{small}}$ usually and
usually for $I \gg I_{\text{fixed}}$.