

About Batteries




① What is a basic property of batteries?

Well what is marked on every commercial battery?

A voltage, e.g. 1.5V, 9V, etc.

~~VV~~

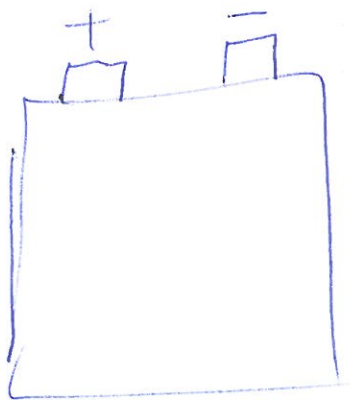Voltage is actually the potential difference between the terminals.



Ideally, it is a constant no matter what current

2) is drawn from the battery

$$P = I V_{Ba} \quad \text{is the power}$$

- Ideally it only depends on I since V_{Ba} is constant. (output of a battery.)

② In Reality Batteries

do have an internal resistance R_{Ba} that can be approximated as ohmic for currents NOT too large.

- R_{Ba} is usually pretty small in a circuit with

a good battery

and can be neglected
to 1st order




If one needs

to ~~do~~, one can model
a real battery as
an ideal battery in series
with ~~but~~ an ohmic battery
resistance R_{Ba}


We don't need to that
in our lab.

4

i) What would this circuit be called?

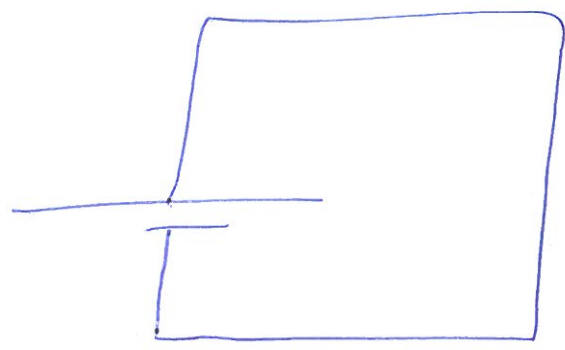

ANS. a short circuit of the battery.

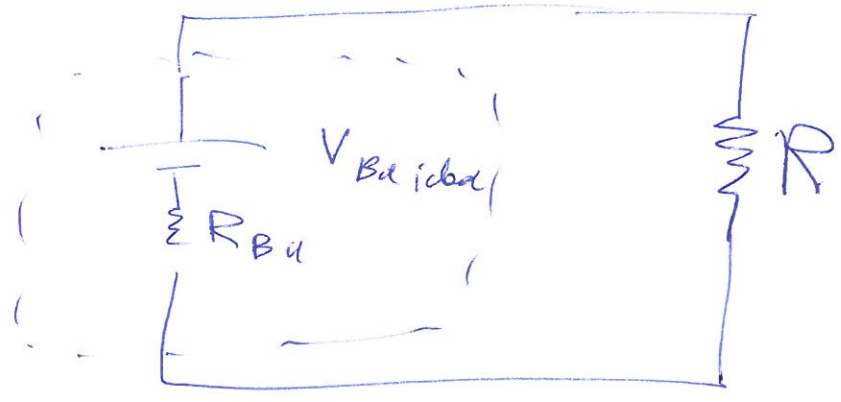

ii) Solve for current I

$$I = \frac{V_{Ba}}{R_{Ba} + R}$$

Solve $P_{\text{output of battery}}$ in terms of V_{Ba}, R_{Ba}, R

ANS. $P = I V_{Ba} = \frac{V_{Ba}^2}{R_{Ba} + R}$

As $R \rightarrow 0$ (i.e., one goes to [∞] short circuit) 5


What happens to P ?

Where does this power end up?

Is this safe?


③ In this lab (see Task 1)

This circuit defines

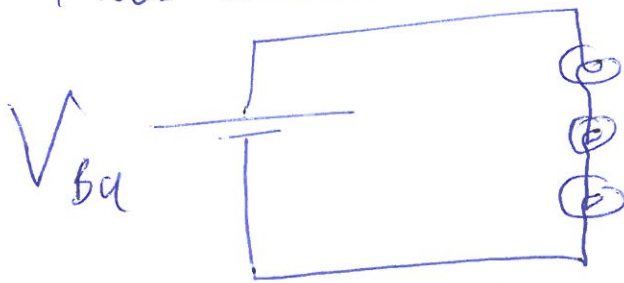

I_u unit current
 V_u unit potential
 R_u unit resistance

— The battery is assumed ideal

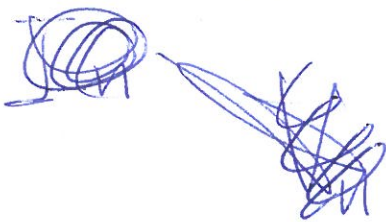

as always in this lab
 (a good assumption)
 and the bulbs
 identical (a so-so
 assumption)

V_u is the potential drop
 across a
 single bulb.

6)


What is V_u
in terms of V_{Ba} ?

You actually need
to measure I_u .

What is R_u in terms
of V_u and I_u ?

④ In Task 2

In task 2, you
build circuits of form

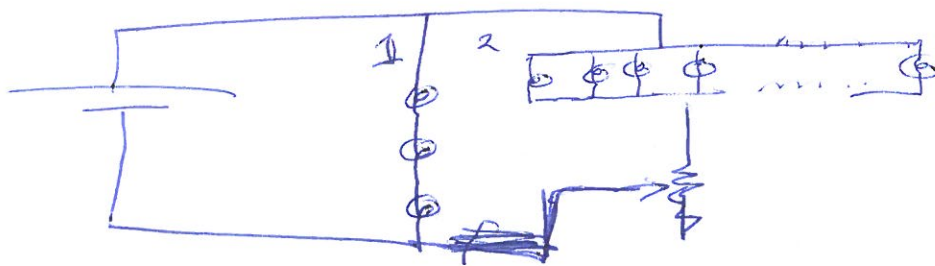

N
bulbs in parallel
are
identical

You adjust

the wire so that
all the bulbs
are equally bright.

What is the resistance
of the N bulbs in
parallel?

$$I = \sum_i I_i$$

and $R \equiv \frac{V}{I}$ for any IV device

$$\therefore \frac{V}{R} = \sum_i \frac{V}{R_i}$$

$$\frac{1}{R} = \sum_i \frac{1}{R_i}$$

$$\frac{1}{R} \geq \text{Max}(\frac{1}{R_i})$$

$$R \leq \text{Min}(R_i)$$

The
resistances
are NOT
ohmic
in general

8

If all R_i are
equal

$$R = ?$$

~~If all bulbs are
equally bright,
what current
flows through each
bulb?~~

~~What potential drop
occurs across each bulb?~~


~~Remember the bulbs are I-V devices~~

$$I = I(V) \text{ or } V = V(I)$$

If all bulbs are
 equally bright,
~~what is power output~~
 how do their power outputs
 compare?
 their currents?
 their potential drops
 across?

What is the current
 in branch 1?
 in branch 2?

Example

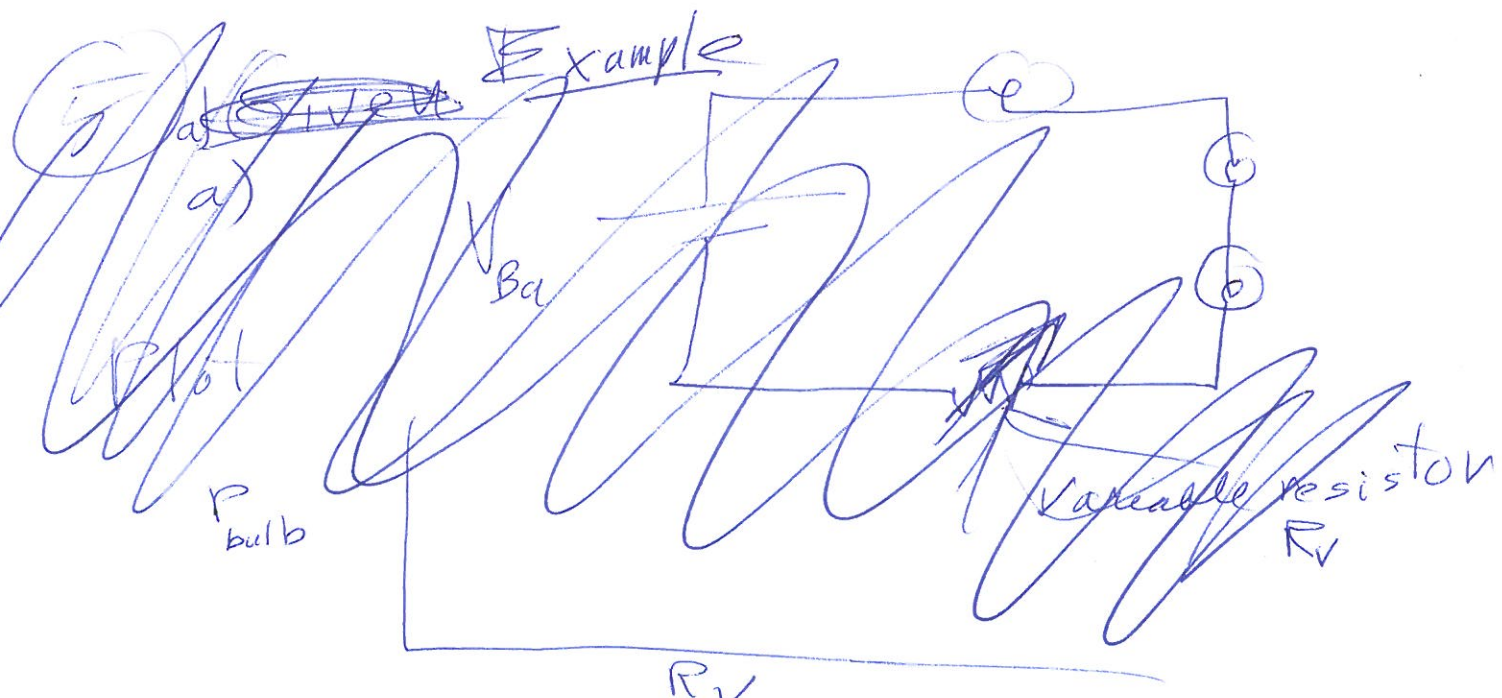


10


5

Example Circuits to test Your know how


a)

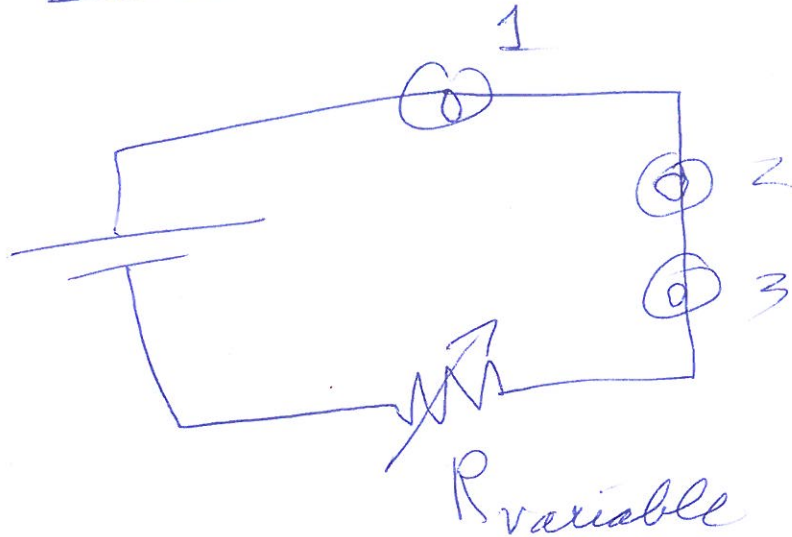

Plot schematically a variable resistor.

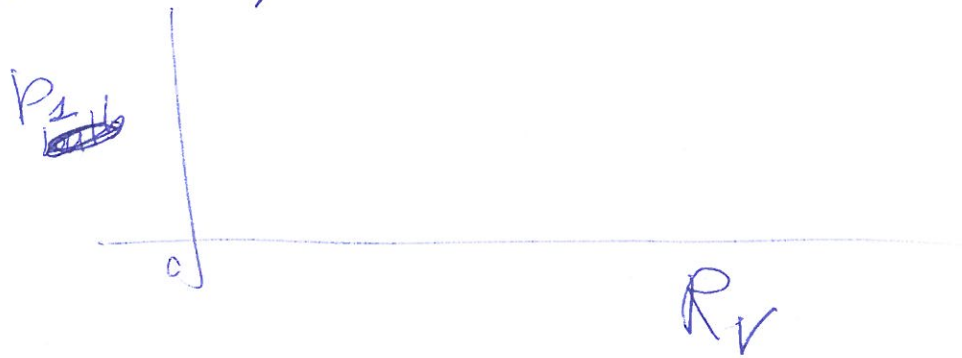

b)

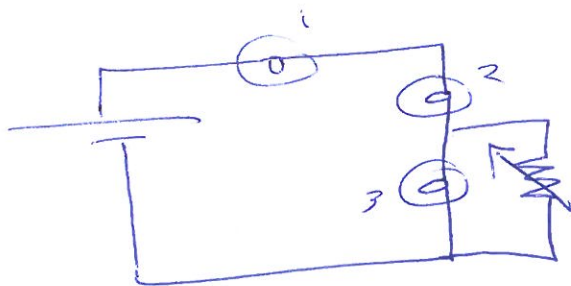


Plot



Plot




c)

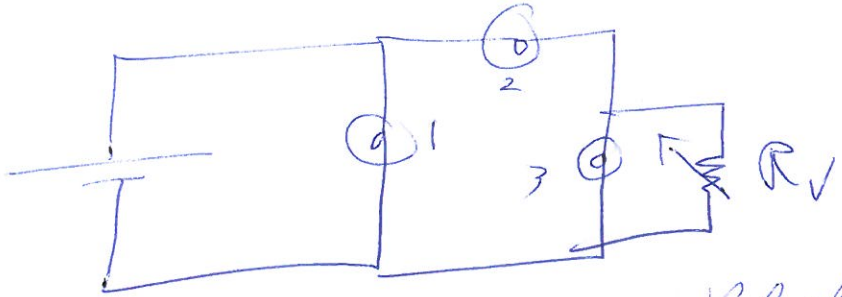


Plot





Plot

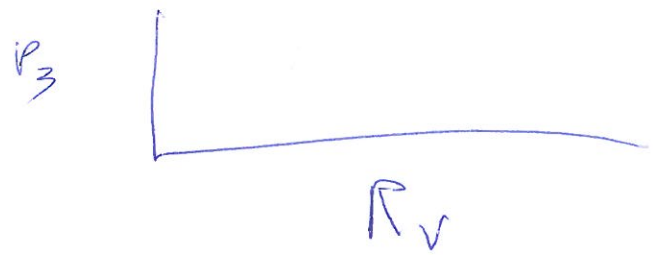

d)

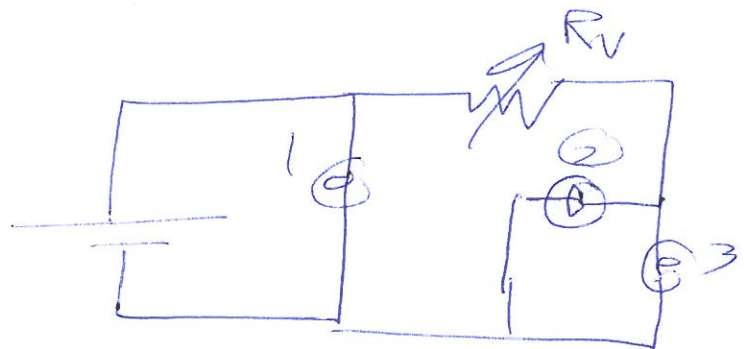

Plot

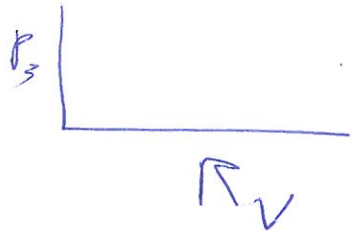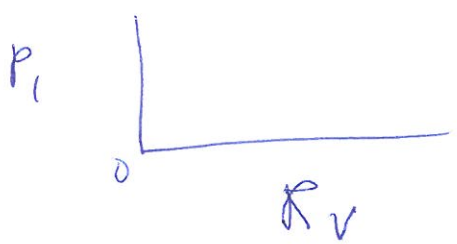


You may be asked in the lab to build one of these circuits and test its behavior.


6) Practicalities

i) Use two batteries in a holder to get $V_{Ba} = 3V$.

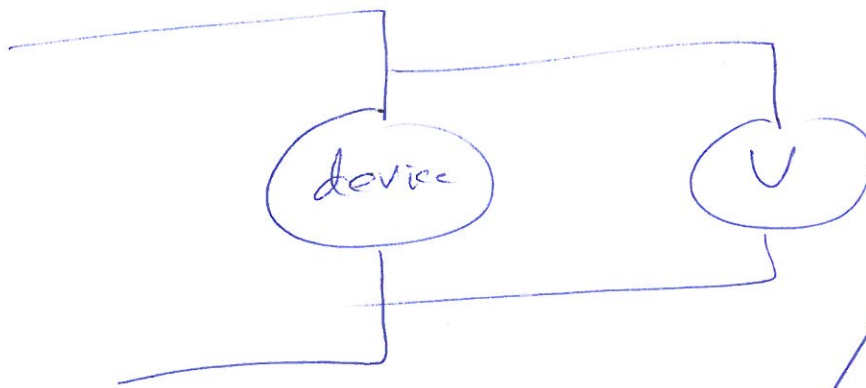ii) Voltage is measured across a component.



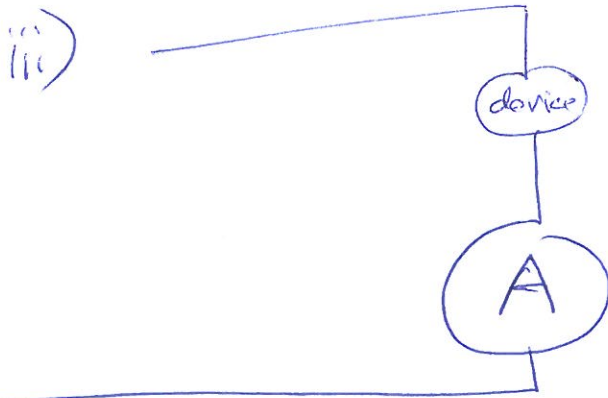Voltmeter measure V across device.
The voltmeter has a very high resistance so as to minimally perturb the circuit.



An ammeter must be in current path to measure current.

An ammeter has small resistance so as to minimally perturb the circuit.

In this lab we will


use galvanometers

as ~~ammeters~~ ammeters

NOT multimeter ~~ammeters~~
ammeters

These blow their fuses if $I \geq .7A$ and the fuses are tedious to replace.

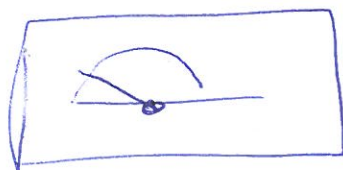There's too much chance of blowing fuses in this lab.



- analog devices,
not digital
nor electronic.

