

Discharging Capacitors

1) Capacitors

— Capacitors are simple circuit devices

for storing charge and energy.

— They are extremely important and have many uses.

- frequency tuning
- energy for fast release
- maybe one day powering your car.

— The equation describing their behavior is

2

$$V = \frac{Q}{C}$$

$$\frac{Q}{C}$$


Charge
on the
positive
plate

potential
drop across
the capacitor
plates.

capacitance
— a property
that ideally
depends
only on the
geometry of
the capacitor
and the
dielectric
it is embedded
in.

Circuit


Symbol

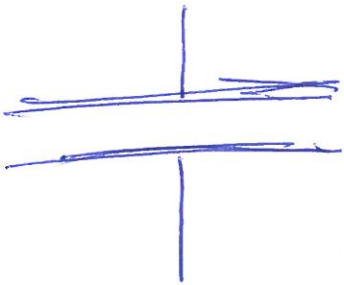

$$\text{or } C = \frac{Q}{V}$$

which gives the interpretation of C as
how much charge can be stored per volt.

Physically one has two metal plates

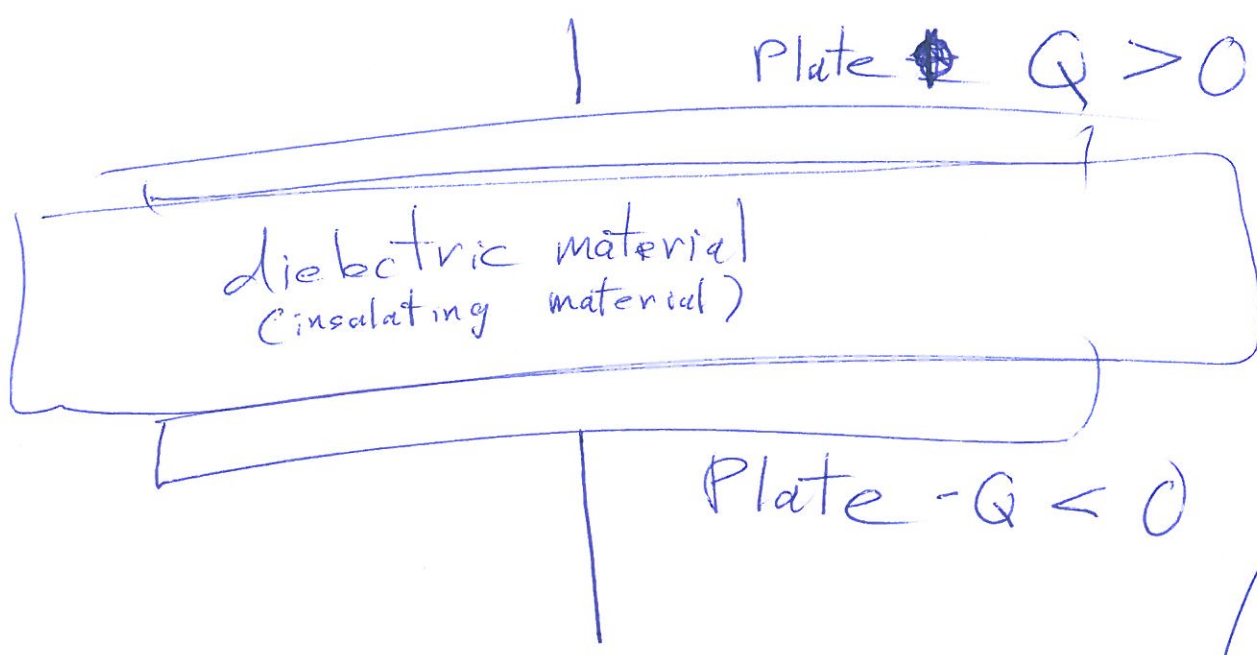

Don't have to be planar
 - They can be rolled up in a cylinder or other configurations

A charge Q is put on the positive plate and a negative $-Q < 0$ is put on the negative plate.

4

The potential energy stored in a capacitor is easily found

$$dPE = Vdq$$

Change in PE
by moving
 dq from
-ve plate
to +ve plate

$$V = \frac{q}{C}$$

is the potential
difference at
the time
of transferring dq

$$\begin{aligned} PE &= \int_0^Q Vdq = \int_0^Q \frac{q}{C} dq \\ &= \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2 \\ &= \frac{1}{2} QV \end{aligned}$$


$$PE = \frac{1}{2} QV = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2 \quad \boxed{5}$$

2) RC Circuit

A simple RC circuit has a resistor and capacitor in series.

— One also includes a battery for charging.

a) Charging RC Circuit

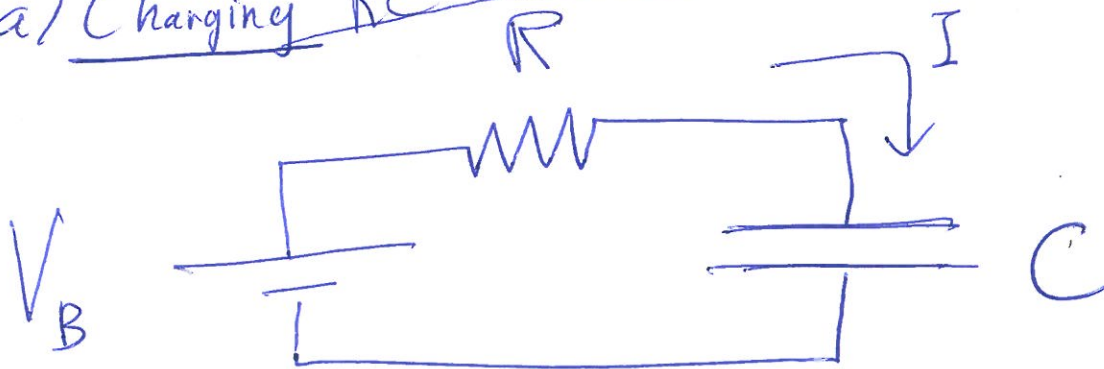

6

We apply
Kirchhoff's Voltage Law

$$V_B = I R + \frac{Q}{C}$$

from
Ohm's law

from
capacitor
law

Now we assume
the capacitor ~~potential~~
change was ~~entirely~~
is due to current
flowing into the
capacitor:

$$Q = \int_0^t I(t') dt' + Q_0$$

time zero charge

We assume at time $t = 0$, 7

$$Q = 0$$

i.e., the capacitor starts uncharged.

$$\therefore \text{at } t = 0, \quad V_B = I_0 R$$

$$I_0 = \frac{V_B}{R} \text{ is the}$$

time zero current.

We note that the current builds up the charge Q .

$$\therefore Q = \int_0^t I(t') dt'$$

$$\therefore \frac{dQ}{dt} = I$$

We can solve for I .

Experience tells me the easiest way is to differentiate the

8

Kirchhoff's law equation
to

$$0 = \frac{dI}{dt} R + \frac{I}{C}$$

A differential equation for I ,
not an algebraic equation.

which rearranges to

$$\frac{1}{I} \frac{dI}{dt} = -\frac{1}{RC}$$

unit $[RC]$

$$= \frac{\text{Volt}}{\text{Coulomb/s}} \frac{\text{Coulomb}}{\text{Volt}}$$

= second
and this
RC does
have units
of time.

We define $\tau = RC$,

where τ is the time constant
or e-folding time. (for
reasons that soon become
evident).

Now

$$\frac{dI}{I} = -\frac{dt}{\tau}$$

We integrate both sides
to get

$$\ln(I') \Big|_{I_0}^I = -\frac{t}{\tau}$$

9

$$I/I_0 = e^{-t/\tau}$$

$$I = I_0 e^{-t/\tau}$$

Recall $Q = \int_0^t I(t') dt'$

$$Q = I_0 (-\tau) e^{-t'/\tau} \Big|_0^t$$

$$= I_0 \tau (1 - e^{-t/\tau})$$

$$= \frac{V_B}{R} RC (1 - e^{-t/\tau})$$

$$= CV_B (1 - e^{-t/\tau})$$

$$= Q_{\infty} (1 - e^{-t/\tau})$$



where we define $Q_{\infty} = CV_B$

Now $V = \frac{Q}{C} = V_B (1 - e^{-t/\tau})$

$$V = V_B (1 - e^{-t/\tau})$$

10)

Our solutions graphically are

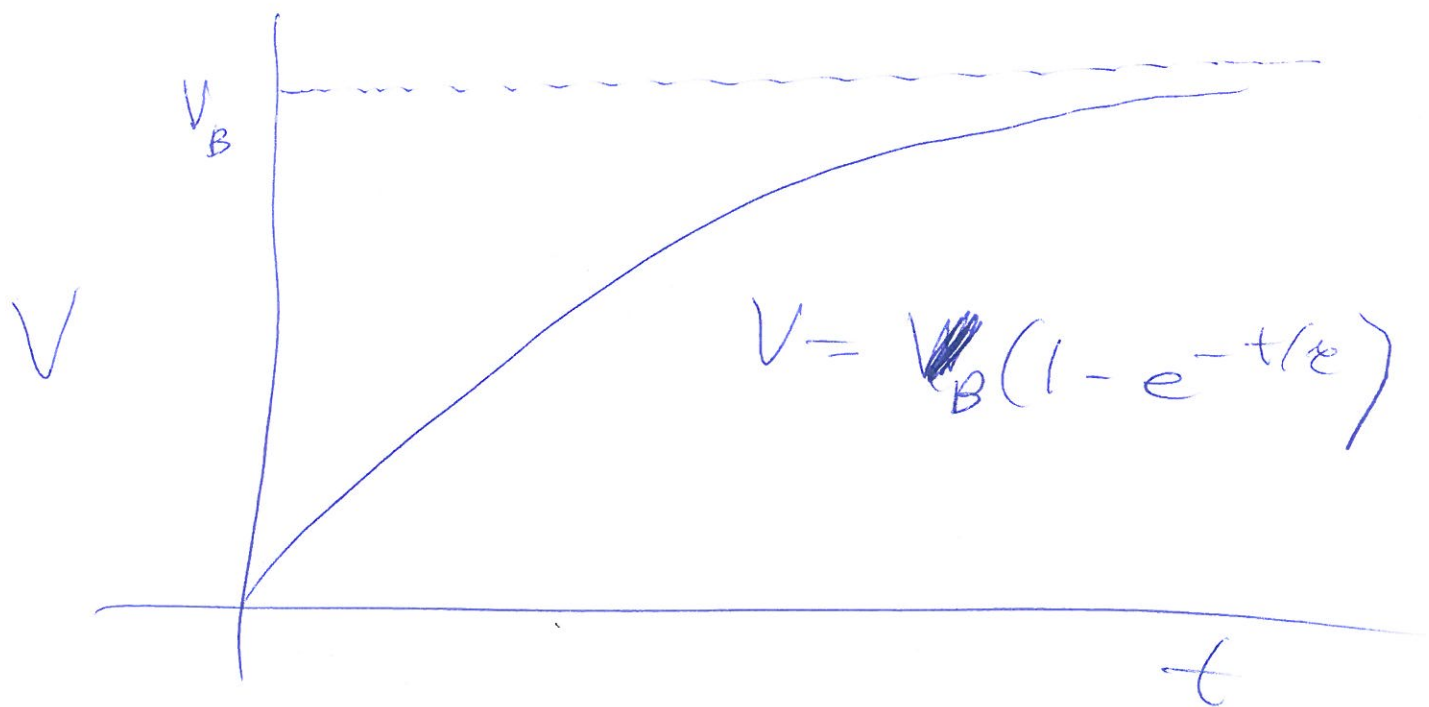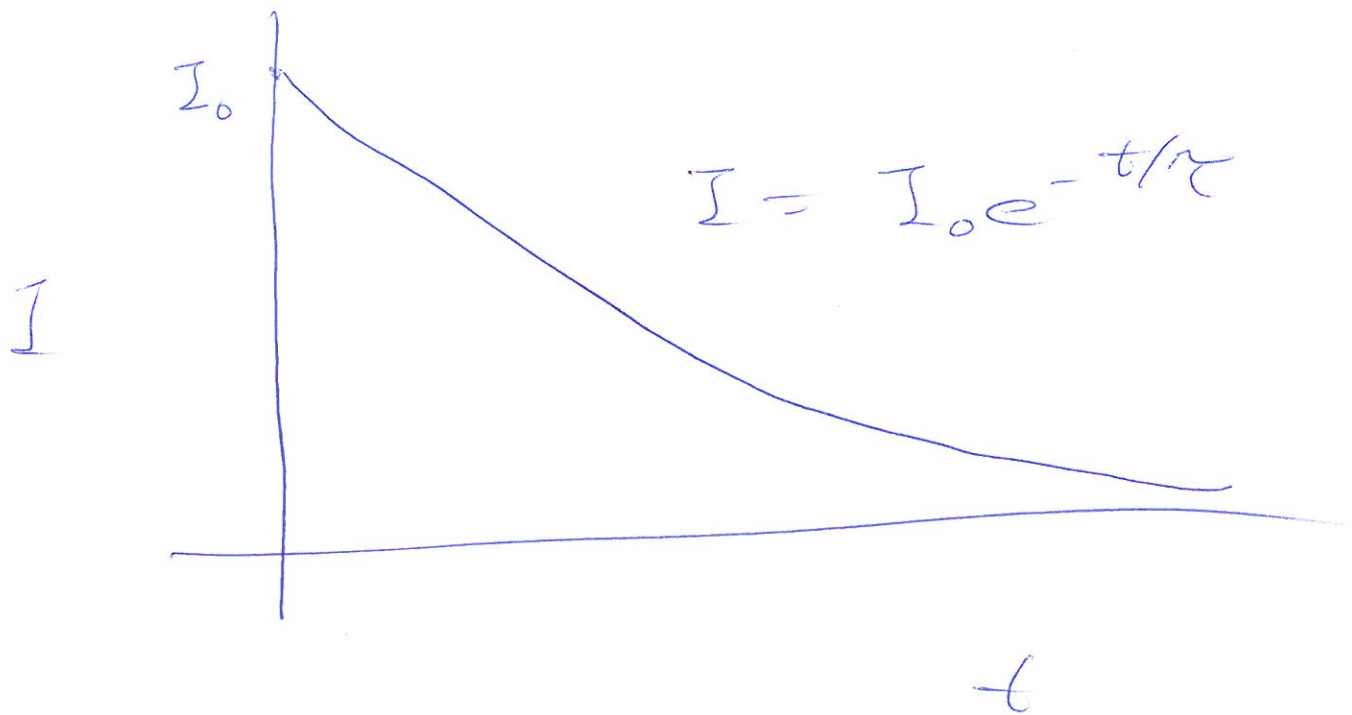

Formally I goes to zero and V goes to V_B only at $t = \infty$.

But practically after
a few τ 's typically

I is so close to zero

and V to V_B that

the differences are
smaller than

error in the measurements

and/or

fluctuations in the system.

So for practical purposes

$$I \rightarrow 0$$

$$\text{and } V \rightarrow V_B$$

in a finite time.

12)

b) Discharging the RC circuit

We remove the battery of the RC circuit when the capacitor is fully charged.


For the new calculation

$$Q_{\text{new}} = Q_{\text{old}}$$

Kirchhoff's Voltage law applied gives after one has closed the circuit,

$$0 = IR + \frac{Q}{C}$$

No driven term this time.

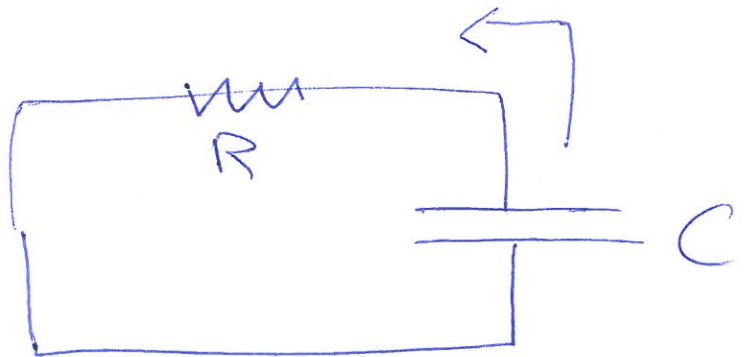

$$I_0 = - \frac{Q_0}{RC} = - \frac{Q_0}{\tau}$$

We can still use

13

$$\frac{dQ}{dt} = I$$

as long as we understand a negative current as flowing clockwise and discharging the capacitor.

Differentiating ~~again~~ the Kirchhoff Voltage law, we get

$$0 = \frac{dI}{dt} R + \frac{I}{C} \quad \text{just as on p. 8}$$

Thus the solutions for I is the same

$$I = I_0 e^{-t/\tau}$$

$$I = -\frac{Q_0}{\tau} e^{-t/\tau}$$

14

We integrate to get Q

Q

$$\int_0^t I dt = -\frac{Q_0}{\tau} e^{-t/\tau} \Big|_0^t$$

$$Q - Q_0 = -Q_0 (1 - e^{-t/\tau})$$

$$Q = Q_0 e^{-t/\tau}$$

$$V = \frac{Q}{C} = \frac{Q_0}{C} e^{-t/\tau} = V_0 e^{-t/\tau}$$



Changing our sign convention
on I ($I_{\text{new}} = -I_{\text{old}}$),
our solutions become

$$\bar{I} = \bar{I}_0 e^{-t/\tau}$$

$$V = V_0 e^{-t/\tau}$$

$= V_B$ if we charged up with a battery.

Graphically

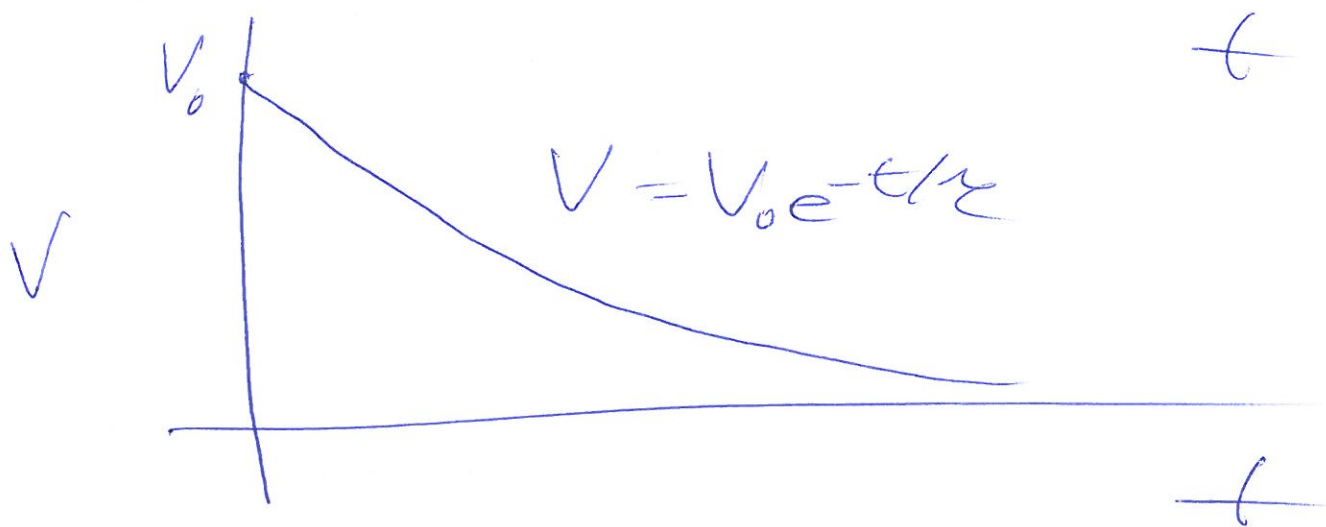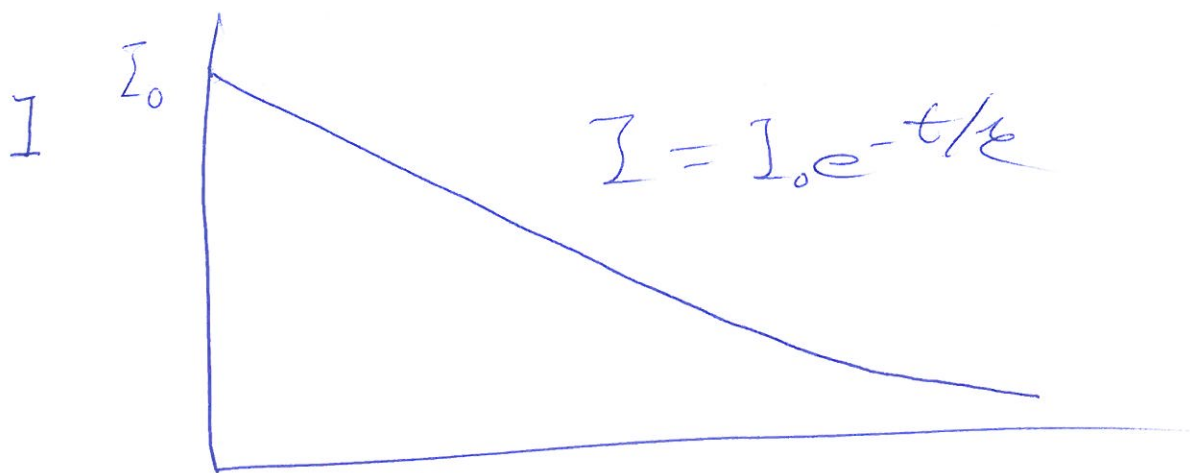


Formally $I \rightarrow 0, V \rightarrow 0$
only at $t = \infty$.

But, in fact, their differences from ~~either~~ zero becomes less than error and/or fluctuations within a few τ 's typically.

16

c) Charging a bulb-C circuit

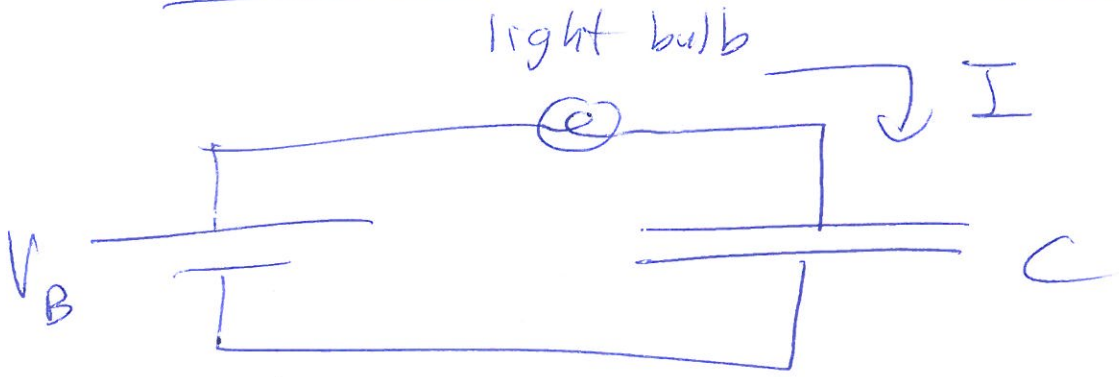

What if we change the capacitor using a light bulb rather than a resistor?

Well Kirchoff's law gives

$$V_B = V_{\text{bulb}}(I) + \frac{Q}{C}$$

Final state
I=0
Q=CV_B


The bulb is not ohmic, so $V_{\text{bulb}} \neq IR$

We cannot solve the differential equation without specifying $V_{\text{bulb}}(I)$

18

and even if we did
an analytic solution
may not be possible
— Maybe only
a numerical solution
could be obtained.

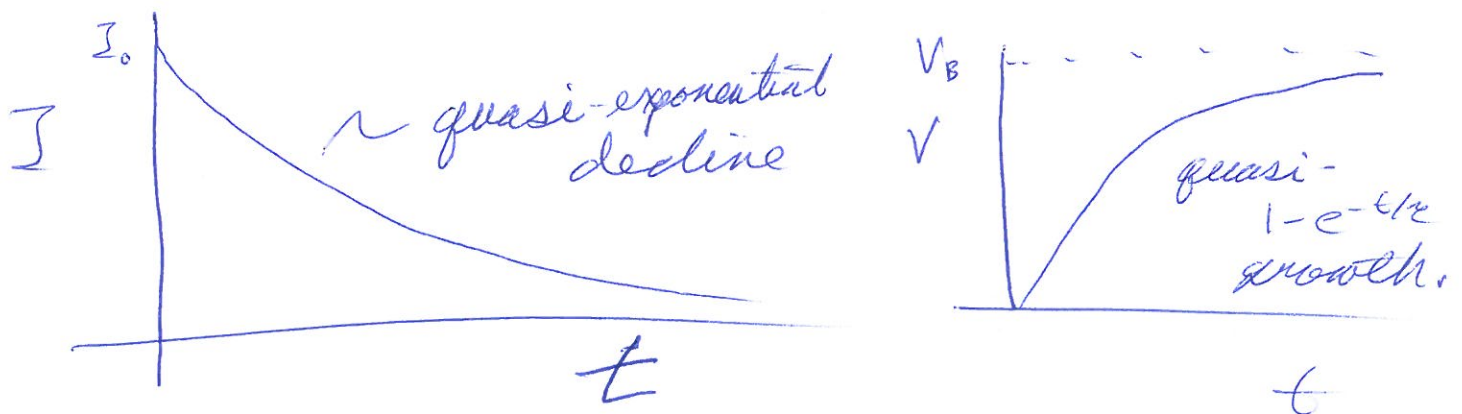But qualitatively we
expect the behavior to
be much like charging
an RC circuit




3) Testing Our
Discharge Theory

$$V = V_0 e^{-t/\tau}$$

$$\tau = RC$$

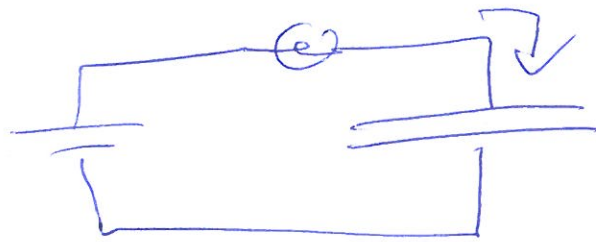We charge up our capacitor
using a bulb-C circuit



The bulb is ~~just~~ for
display. The capacitor
would charge very quickly
with no bulb.

20a

Maybe too quickly

Initial current $I_0 = \frac{V_B}{R}$ (see p. 7)

If R is very ^{small}, I_0
can become very large
for a short time
— time scale for changing
is $\tau = RC$ recall.

Our capacitors are

modern tantalum
electrolytic
capacitors

of $C = 1.0 \text{ Farad}$


$$1 \text{ Farad} = \frac{1 \text{ Coulomb}}{1 \text{ volt}}$$

Unlike standard

capacitors

the electrolytic capacitors

have a definite polarity

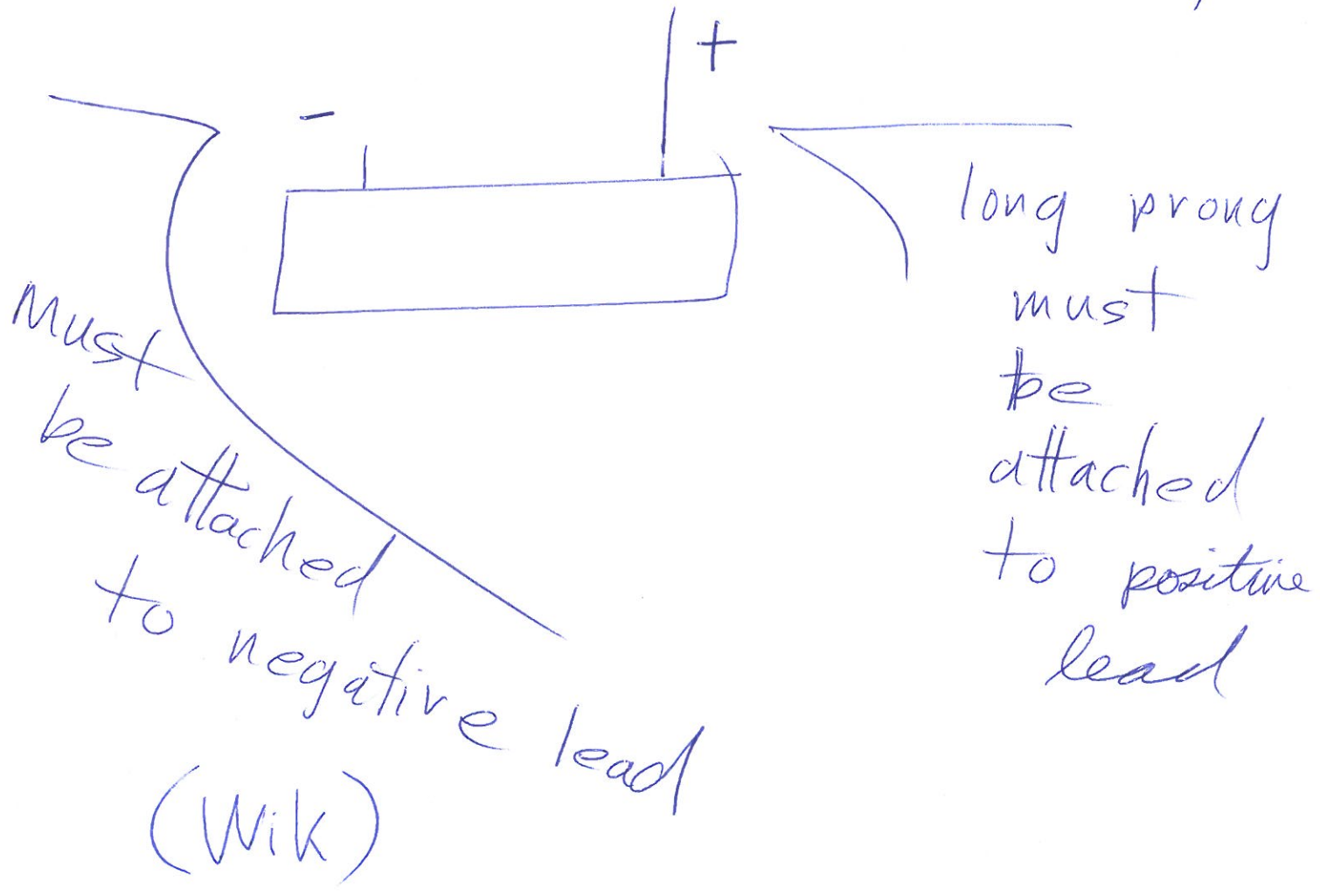

20c

~~They actually~~

Curs actually seem
to work in reverse
mode — But
that is NOT
recommended.

Actually 1 Farad is 21
a huge capacitance
for a small ~~lab/capa~~
lab/circuit capacitances

- typical lab capacitors
are of order

picofarads
 $= 10^{-12} \text{ F}$

or nanofarads
 $= 10^{-9} \text{ F}$

or microfarads
 $= 10^{-6} \text{ F}$

1 Farad means the
capacitor holds a
Coulomb with 1 Volt.


- A net charge of a coulomb

22) is actually an ^{enormous} dangerous charge, but of course the capacitor is overall neutral $+1\text{ C}$ on +ve plate
 -1 C on the -ve plate

Measurements

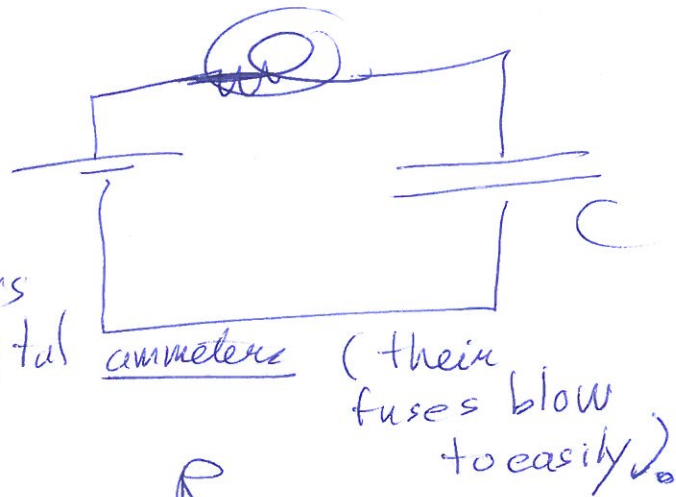
a) Charge up capacitor

Use Galvanometers ~~as~~ ammeters to check current, NOT digital ammeters



b) Discharge

— we don't use resistor

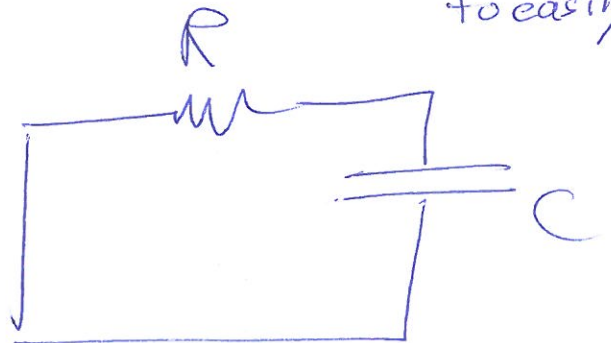


boxes any more

(they kept getting overheated) and ~~breaking~~ burning out

Use two resistors
of $150\ \Omega$

in parallel

23

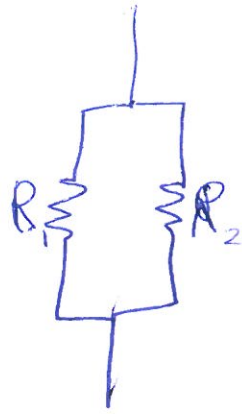

What is their net
resistance?

Measure V_0 at time zero

Table

t (s)	V (V)	$\ln(V)$
$0 \pm ?$	$V_0 \pm ?$	$\ln V_0$
10	⋮	⋮
20	⋮	⋮
30	⋮	⋮

24)

Use 10 second

18 data
points
altogether.

intervals

and read ~~as~~

~~long~~ for 3 minutes

(Redundant data
is good. Bad data
points due to misreading
etc., can be spotted
and left out of consideration)

You must estimate
a time error Δt
and a potential error
 ΔV .


These should be the same for whole set.

Or Use Graphical Analysis

to tabulated data

and plot V versus t

mark errors by hand on table of data

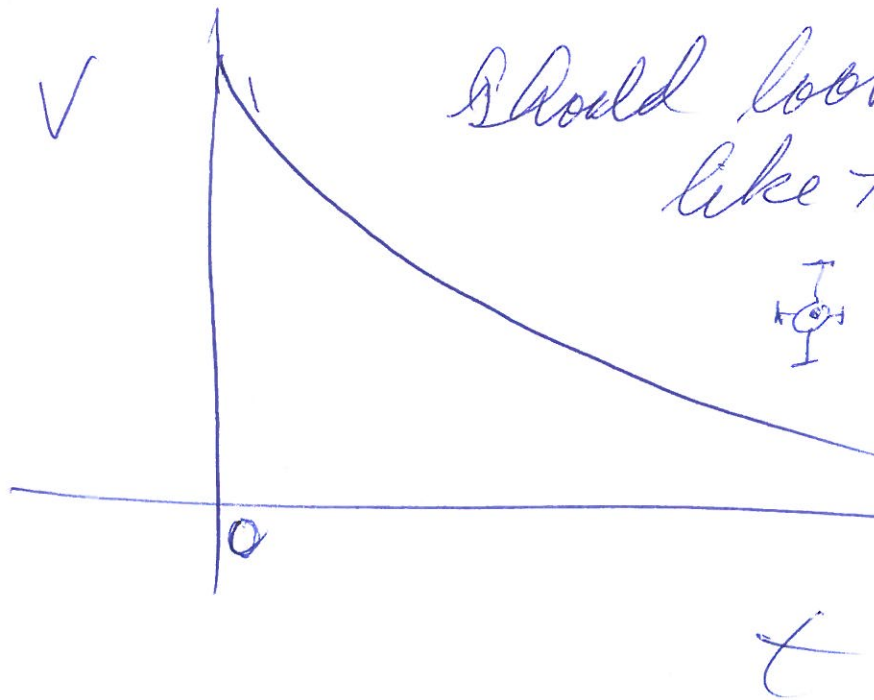

Should look like this.

Representative data point with error bars

26)

But a curve
can only be
judged to be
qualitatively consistent
with theory by eye.

We want a quantitative
check.

So we need a
linearized theoretical
equation

Our equation is
$$V = V_0 e^{-t/\tau}$$

a) So what is the
linearized version?

(27)

Hint You need
natural logarithms.

Answer on your lab.

~~b) What is the~~

b) So what do you
plot against what
to test the

linearized version?

This is graph 2

— Some points should have
error bars if they are large
enough.

28

c) You will need
to do best
and worst fit

Is the data
linear
within
error?

Answer
on
your
lab.

lines on Graph 2
to get
slope and

error in slope
Enter on your lab report.

d) From the slope
you should
get a value

for the capacitance 29

$$C \pm \Delta C$$

error
in value.

How does this compare
to the manufacturer
value of 1.0 F.

Do you get
agreement within
error?

Answer on your lab

30]

e) You will need errors for $\ln V$.

How you find those?

Old trick for small error propagation

Expand $f(x + \Delta x)$ in a Taylor's series about x .

$$f(x + \Delta x) = f(x) + \Delta x f'(x) + \frac{\Delta x^2}{2!} f''(x) + \dots$$

If terms of order $\mathcal{O}(\Delta x^2)$ are negligible

$$\Delta f = f(x + \Delta x) - f(x)$$

$$\approx \Delta x f'(x)$$

Recall
error
is always
positive.

$\therefore \Delta f = |f'(x)| \Delta x$ is the
1st order error
propagation formula

Examples.

a) $y = x^{\frac{1}{2}}$

$$\Delta y = \frac{1}{2} |x^{-\frac{1}{2}}| \Delta x$$

b) $y = x^n$

$$\Delta y = n |x^{n-1}| \Delta x$$

c) $y = e^{kx}$

$$\Delta y = k e^{kx} \Delta x$$

32

d) $y = \ln|x|$

$$\Delta y = \frac{\Delta x}{|x|}$$

The error in a
natural logarithm of x
is relative error
of x

(which is quite cute.)