

| 2026 Aug 01 really |

(D2-14001)

Chapter 19

Inductance

02-14002 }

14.1 Recapitulation Faraday's Law of induction and The Inductance of a Solenoid

a) Faraday's Law
of Induction


$$\mathcal{E} = \oint \vec{E} \cdot d\vec{\ell} = -\frac{d\Phi_B}{dt} = -\frac{d}{dt} \int_{\text{Linked}} \vec{B} \cdot d\vec{A}$$

Can be
called out
even there
is no free charge
to move

Faraday Law
Induced $\vec{E}$ -field
NOT due
+

The line integral
can also be called
the circulation
of the induced
 $\vec{E}$ -field around
closed loop

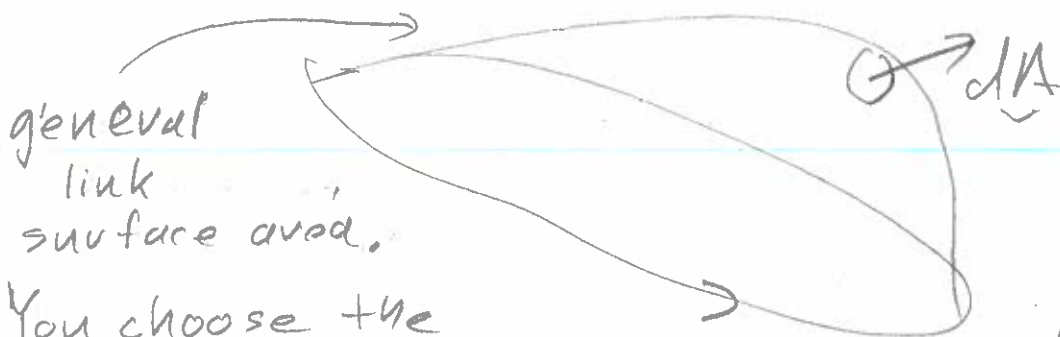Φ_B is the magnetic flux through a linked area



You choose the
convenient one
for a calculation.

They all give the same answer by "Flux conservation."

the sense
of the
differential
area vector
is determined
by curling
right-hand fingers
in fiducial current
direction and the
thumb gives the
sense.

02-14004

The minus sign tells us that the induced emf $\mathcal{E}$ opposes the change in B-field that caused the emf $\mathcal{E}$.

Corollary: The B-field is caused by a current I , then the emf $\mathcal{E}$ opposes changing current: the sense of the emf is

$$\mathcal{E} < 0 \quad \text{if} \quad \frac{dI}{dt} > 0$$

$$\mathcal{E} > 0 \quad \text{if} \quad \frac{dI}{dt} < 0$$

b) Say the B-field is due to a current confined to a thin wire (ideally an infinitely thin wire), then

$$\oint \mathbf{B} \cdot d\mathbf{A} = L I$$

Where L is the inductance

and depends on geometry and, in general, material properties of any medium containing the B-field.

μ_0 is the vacuum permeability.

In general, permeability of magnetization of the medium. We leave this topic sinadie.

2026 aug 01


02-1400-5

For the inductance case

$$\mathcal{E} = -L \frac{dI}{dt}$$

General rule
for devices
called inductors

d) For ideal infinite Solenoid

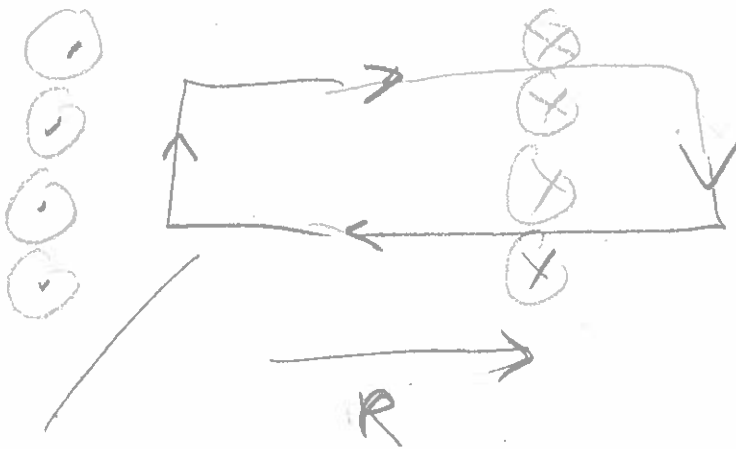

Given that
symmetries
and other
arguments
tell us

$$\vec{B} = \begin{cases} B(r) \hat{z} & \\ & > 0, r < R \\ & = 0, r > R \end{cases}$$

Amperian loop

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{total}}$$

$$B l = \mu_0 N I$$

current in an
individual wire

turns

inside Amperian loop

length
of z-direction
side of
the Amperian
loop

$$\therefore \vec{B}(r) = \begin{cases} \mu_0 n I \hat{z} & \text{inside with } n = \frac{N}{L} \\ 0 & \text{outside} \end{cases}$$

From p. WB2-13008 $\mathcal{E} = -\mu_0 n^2 \pi r^2 \frac{dI}{dt} = -L \frac{dI}{dt}$
for solenoid, and so $L = \mu_0 n^2 \pi r^2 \ell$ where ℓ = volume

14.2 The R.C Circuit without a Driven

A warm-up for the LC circuit

A pure RC circuit is i.e.,
a power source



Recall

$$U = \frac{1}{2} \frac{Q^2}{C}$$

$$= \frac{1}{2} C V^2$$

for
a capacitor

Initial and Final Condition

i) For the capacitor, $Q(t=0) = Q_0$

Since we assume it is
charge to Q .

And $Q(t \rightarrow \infty) = 0$ since the
capacitor is fully discharge
and its energy is dissipated to heat
in the resistor.

ii) For the resistor, we apply
Kirchhoff's voltage law $\frac{Q}{C} = IR$
to time zero and get

$$I_0 = \frac{Q_0}{RC} = \frac{Q_0}{\tau}$$

where τ is the time constant

or e-folding time as before
on p. 02-09050 ff.

(2026aug01)

(02-14007)

Note, also as before, there is an instantaneous start to current in the quasi-steady approximation.

The time-varying E-field establishing the guiding charge is just so fast.

And $I(t \rightarrow \infty) = 0$ when all capacitor charge is discharged and we have neutrality everywhere.

Solution of

$$\frac{Q}{C} = IR$$

which is an integro-differential equation.

To solve take the derivative

which gives

$$\frac{1}{C} \frac{dQ}{dt} = \frac{dI}{dt} R$$

but there is a difference from p. 02-09050

Here $-\frac{dQ}{dt} = I$ since $\frac{dQ}{dt}$ is

decreasing

$$\therefore \frac{dI}{dt} = -\frac{1}{RC} I = -\frac{1}{\tau} I$$


where $\tau = RC$ is again the time constant or e-folding time.

02-19008

$$\frac{dI}{I} = -\frac{1}{\tau} dt$$

$$\ln[I/I_0] = -\frac{t}{\tau}$$

$$I = I_0 e^{-t/\tau}$$

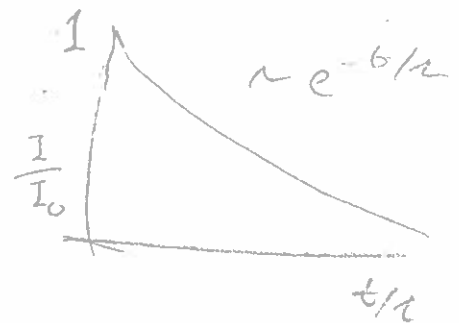

which is NOT surprising

since it just to p. 02-09051,

However $Q = \int_0^t (-I) dt + Q_0$

$$Q = -\tau I_0 (1 - e^{-t/\tau}) + Q_0$$


$$Q = -Q_0 (1 - e^{-t/\tau}) + Q_0$$

$$Q = Q_0 e^{-t/\tau}$$

and so Q declines, NOT increases
as on p 02-09053.

4.3 The LC circuit without a Driver

Here the circuit is

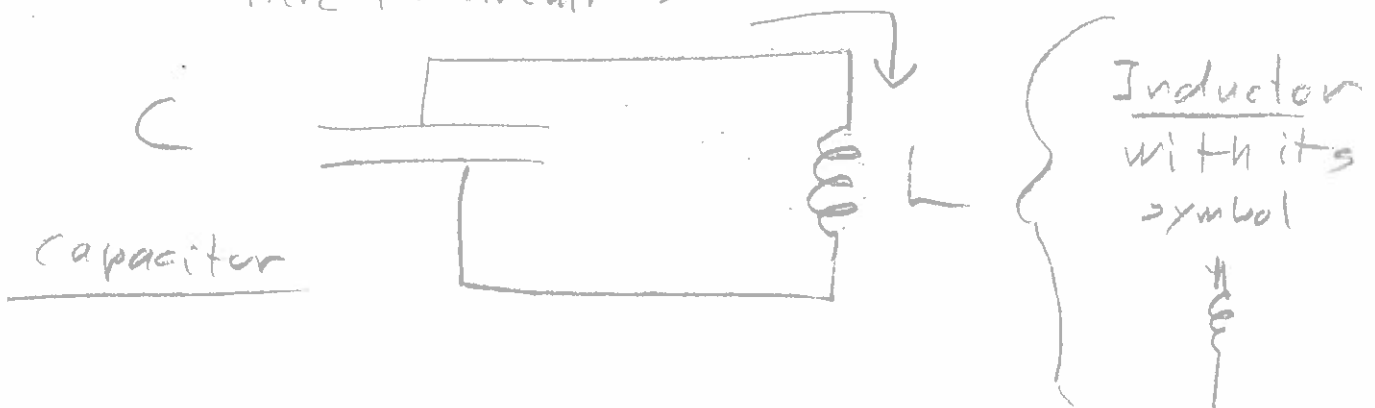

2026aug01

02_14009

Initial and Final conditions

For Q -capacitor, $Q(t=0) = Q_0$


and $Q(t \rightarrow \infty) = ?$

For the current, $I(t=0) = I_0 = ?$

In fact, $I_0 = 0$. In this case, the inductor prevents an instantaneous jump from zero to finite current.

What of final conditions? There is no way to dissipate energy. So one could expect some perpetual oscillation is a potential energy landscape

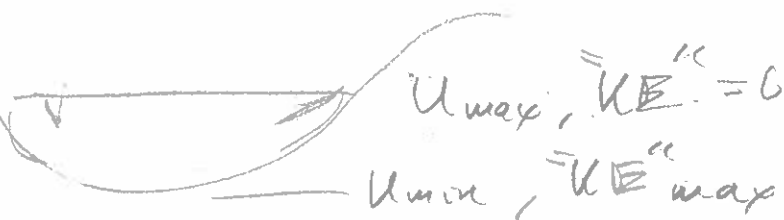Capacitor stores energy in potential of charge
and inductor stores energy as magnetic field energy



$E_B = \frac{1}{2\mu_0} B^2$
energy density

Kirchhoff's voltage law

$$\frac{Q}{C} = L I'$$

$$\frac{1}{C} \frac{dQ}{dt} = L I''$$

and again differentiate to turn into a differential eqn.

and as on p.02-14007

$$-\frac{dQ}{dt} = I$$

$$L I'' = -\frac{1}{C} I$$

A 2nd order ordinary linear DE.
Since 2nd order there are 2 independent solutions

02-14010

$$I'' = -\frac{1}{LC} I$$

which is the simple harmonic oscillator DE

and the resonance (angular) frequency

$$\omega = \frac{1}{\sqrt{LC}}, \quad \left\{ \begin{array}{l} \text{Relabeled } \omega_0 \\ \text{on p. 02-14013} \end{array} \right.$$

A resonance frequency because it is the natural frequency and NOT a frequency

from a driver: i.e., an AC source

$$I'' = -\omega^2 I \quad \left\{ \begin{array}{l} \text{A 2nd order} \\ \text{ordinary} \\ \text{linear DE} \end{array} \right.$$

With general solution

$$I = A \cos \omega t + B \sin \omega t$$

where A and B are constants to be set by the initial conditions

Recall $I(t=0) = 0$, and so $A = 0$

Q must oscillate back and forth between $Q_0(2\pi n)$ and $-Q_0(2\pi n + \pi)$

and so $-Q_0 = \frac{I_a}{\omega} [-1 - 1] + Q_0$

$$\frac{I_a}{\omega} = (Q_0)$$

$$I_a = \omega Q_0$$

$$I = I_a \sin \omega t,$$

where I_a is the amplitude of the oscillation

$$Q = \int (-I) dt + Q_0 = \frac{I_a}{\omega} \cos \omega t \Big|_0^t + Q_0$$

$$Q = \frac{I_a}{\omega} [\cos \omega t - 1] + Q_0 = Q_0 \cos \omega t$$



$$Q = (Q_0 \cos(\omega t))$$

∴]

2026 aug 01

02-14011
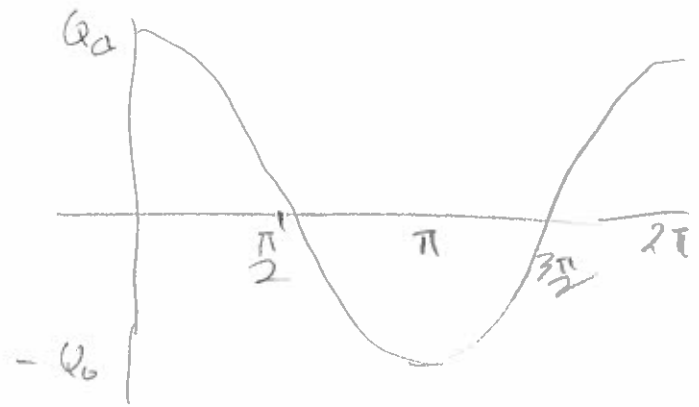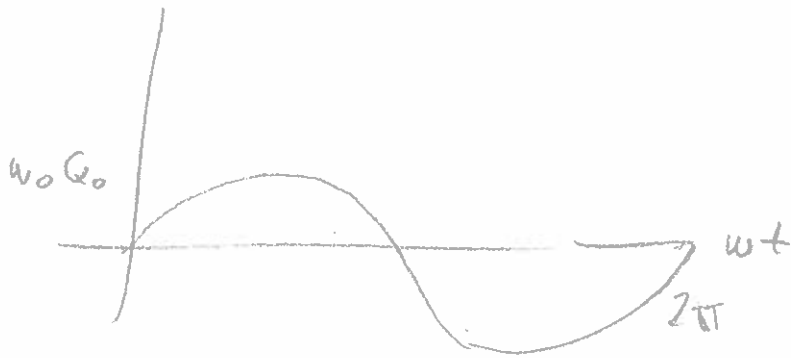
$$I = w Q_0 \sin(wt) , \quad Q = Q_0 \cos(wt)$$



14.4 The LRC circuit without a Driven

a) In fact, the case of real interest is with an AC driven

and the solution of this case

is trickier than I recall

and the Text-611 has a wrong answer which

I learnt when I gave up trying to reproduce and I just asked Google AI,

if even saw it or did it which may be never,

Zen Kōans for Our Time

AI is the answer that is not the answer.

A discovery is well known.

Kōans come in threes.


2026 aug 02 (The most useful product of my weekend, alas)

02-14012

R

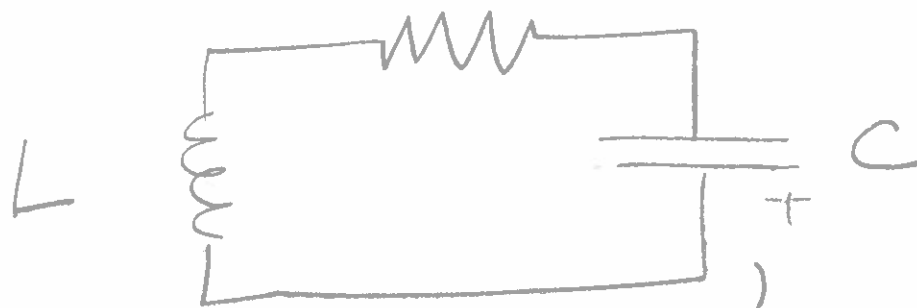b) An LRC circuit without a driver

(which is a AC power source usually and which we consider in Chapter 15 probably)



Applying Kirchhoff Voltage law

$$\frac{Q}{C} = LI' + IR$$

and differentiating the Integro-DE

with $\frac{dQ}{dt} = -I$ gives

$$0 = LI'' + I'R + \frac{I}{C}$$

A 2nd order linear ordinary DE

This DE is an exact analog

of the damped harmonic oscillator DE,

where R acts as a damping force to dissipate energy to heat,Ansatz the solution $I = e^{-\gamma t}$

(because we know this the path)

Reduced the differential eqn. to an algebraic equation.

$$0 = L\gamma^2 - R\gamma + \frac{1}{C}$$

which is quadratic eqn: Recall

$$0 = ax^2 + bx + c$$

$$\text{gives } x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

[2026 aug 01]

[02-14015]

$$\therefore I = -\frac{\omega_0^2 Q_0}{2\beta} \left[e^{-(\alpha+\beta)t} - e^{-(\alpha-\beta)t} \right]$$

$$I = \frac{\omega_0^2 Q_0}{2\beta} \left[e^{-(\alpha-\beta)t} - e^{-(\alpha+\beta)t} \right]$$


Google AI agrees, except it had an overall minus for a different fiducial current direction

$\alpha - \beta > 0$
and this gives slow exponential decline

$\alpha + \beta > \alpha - \beta$
and this gives fast exponential decline

also $I = \frac{\omega_0^2 Q_0}{2\beta} e^{-\alpha t} \sinh(\beta t)$ which doesn't show the behavior so well, but is more numerically

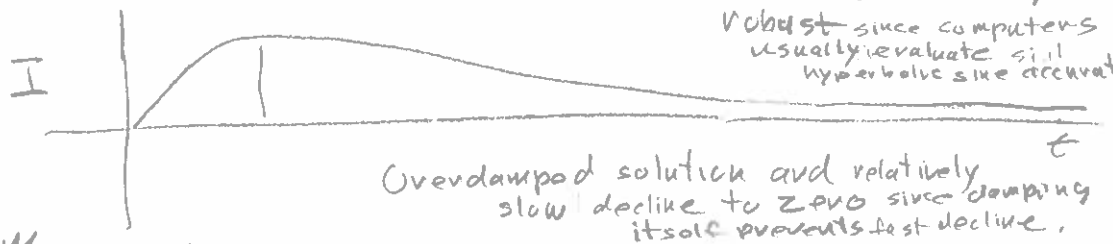robust since computers usually evaluate $\sinh$ hyperbolic sine accurately.



Overdamped solution and relatively slow decline to zero since damping itself prevents fast decline.

For maximum

$$\frac{dI}{dt} = 0 = -(\alpha - \beta) e^{-(\alpha-\beta)t} + (\alpha + \beta) e^{-(\alpha+\beta)t}$$

$$0 = -(\alpha - \beta) e^{\beta t} + (\alpha + \beta) e^{-\beta t}$$

$$0 = -(\alpha - \beta) e^{2\beta t} + (\alpha + \beta)$$

$$\therefore (\alpha - \beta) e^{2\beta t} = (\alpha + \beta)$$

$$2\beta t = \ln\left(\frac{\alpha + \beta}{\alpha - \beta}\right) > 0$$

$$t_{\max} = \frac{1}{2\beta} \ln\left(\frac{\alpha + \beta}{\alpha - \beta}\right)$$

$$I_{\max} = \frac{\omega_0^2 Q_0}{2\beta} \left[\left(\frac{\alpha + \beta}{\alpha - \beta}\right)^{-(\alpha-\beta)/(2\beta)} - \left(\frac{\alpha + \beta}{\alpha - \beta}\right)^{-(\alpha+\beta)/(2\beta)} \right]$$

02-14016

Critical damping

Fastest decline to zero

What one wants
2-way swinging
restaurant doors, but
oscillating doors
are
tacky

e) Case 2 From p. 02-14014

$$\gamma = \alpha \quad \text{since } \alpha^2 - \omega_0^2 = 0$$

Our
Ansatz
solution
does NOT
conform
to 2nd
solution
in
this case

and seems only one solution

$$I \propto e^{-\alpha t} \quad \text{which cannot match initial condition } I(t=0) = 0.$$

But 2nd order ordinary linear DE
always has a 2nd solution (Arken-469,

There is, of course, a general procedure
for finding a 2nd solution, but is
there something simpler?

$$\text{Try } I = f(t) e^{-\alpha t}$$

This is a
correction factor

This is the main damping behavior

$$0 = L I'' + I' R + I / C \quad \text{from p. 02-14012}$$

$$0 = L [f'' - 2\alpha f' + \alpha^2 f] + [f' - \alpha f] R + f / C$$

using Leibniz rule

Arken-667, 989

a generalization
of the product rule

$$0 = L [f'' - 2\alpha f'] + f' R + \{ L [\alpha^2 f] - \alpha f R + f / C \} = 0$$

$$0 = L [f'' - 2\alpha f'] + f' R$$

$$[L \alpha^2 - \alpha R + 1/C] f = 0 \quad \text{since } \alpha \text{ satisfies}$$

original
quadratic
eqn.
p. 02-14012

2026aug01

02-14017

At this point we guess $f = t$

$$\therefore f'' = 0$$

$$f' = 1$$

$$\text{and } U = L[-2\alpha] + R$$

$$\text{leads to } \alpha = \frac{R}{2L}$$

which is consistent
with the p. 02-14013
definition of α .

$$\therefore I = A t e^{-\alpha t}$$

and we need to determine
coefficient A .

$$t_{\max} = \frac{1}{\alpha}$$

and

$$I_{\max} = \alpha Q_0 e^{-1}$$


$$I' = [A e^{-\alpha t} - \alpha A t e^{-\alpha t}] \Big|_{t=0}$$

$$= \omega_0^2 Q_0 \text{ from p. 02-14017}$$

$$A = \omega_0^2 Q_0$$

$$I = \omega_0^2 Q_0 t e^{-\alpha t} \text{ where } \omega_0 = \frac{1}{\sqrt{LC}} = \alpha$$
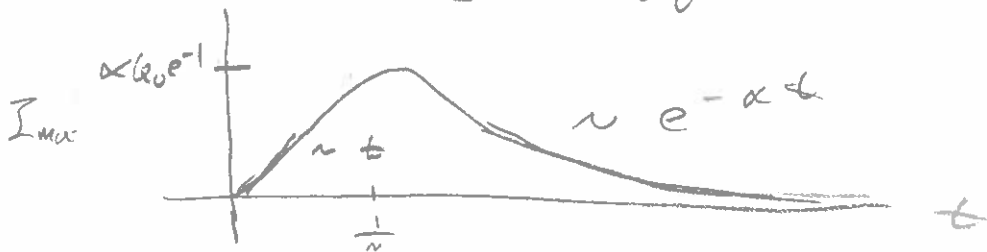
$$= \alpha^2 Q_0 t e^{-\alpha t} \text{ since } \omega_0^2 = \alpha^2 \text{ for critical damping.}$$



0214018

Which is very need for
two-way swing restaurant doors,
Great for slopstruck comedy

f) Case 3 Underdamping which gives
oscillatory behavior.
 $\gamma = \alpha \pm i\omega_d$

$$\alpha^2 - \omega_0^2 < 0$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\text{So } I = I_0 e^{(\alpha + i\omega_d)t} + I_0 e^{-(\alpha - i\omega_d)t}$$

Now the complex number solutions
are valid solutions of
the DE, but don't
match the requirement
that $I(t)$ be a pure real.

But with some complex number trickery
we can find the real solutions

Show of hands: How many
of you-all have covered
complex number math to some degree?

Some? All?

Especially electrical engineers will need
complex number math because
it is used for alternating currents.

It is a very useful tool for avoiding
endless trigonometric identity use.
And I intend to cover a bit of it for Chapter 15.

2026aug01

02_19019

Turkey: Recall from p. 12-19019

$$I = \frac{\omega_0^2 G_0}{2\beta} \left[e^{-(\alpha - \beta)t} - e^{-(\alpha + \beta)t} \right]$$

was a solution

Now $\beta \rightarrow i\omega_d$

and $\frac{1}{1} = \frac{1}{1/2} = -i$

$i = \sqrt{-1}$ is the
imaginary unit

$$I = \frac{\omega_0^2 G_0}{2\omega_d} e^{-\alpha t} \left[-i e^{i\omega_d t} + i e^{-i\omega_d t} \right]$$

Now we need Euler's formula

$$e^{\pm i x} = \cos x \pm i \sin x \quad (\text{W.k: Euler's formula})$$

and so

$$I = \frac{\omega_0^2 G_0}{\omega_d} e^{-\alpha t} \left[\underbrace{i[-\cos x + \cos x]}_{0} + \underbrace{[-i(i)\sin x + i(-i)\sin x]}_{\sin x} \right]$$

$$I = \frac{\omega_0^2 G_0}{\omega_d} e^{-\alpha t} \sin x$$

So, in fact,
the solution above
is a pure real
after all and
it satisfies the
initial condition


02-14020

$$\therefore I = \frac{\omega_0^2 Q_0}{\omega_d} e^{-\alpha t} \sin \omega_d t$$



9) We could Now integrate to get $Q(t)$, but we have done enough.

14.5 An LC circuit with a constant emf

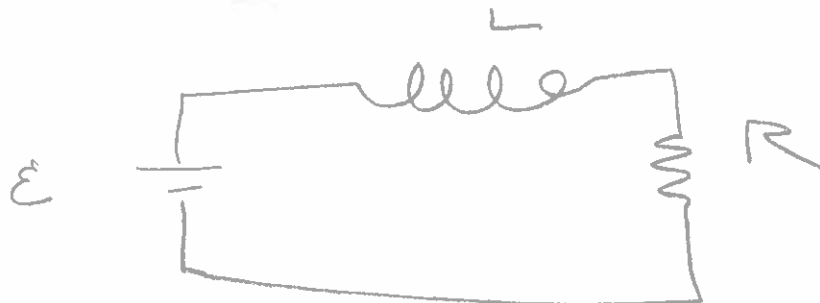

Apply Kirchhoff's Voltage law

$$\mathcal{E} = LI' + IR$$

Question: Initial condition is on I and I' are?

Answer: $I_0 = 0$ because of inductor,
 $I'_0 = \mathcal{E}/L$ to satisfy Kirchhoff's voltage law

Solution

$$L I' = \mathcal{E} - IR$$

$$\frac{L I}{\mathcal{E} - IR} = 1$$


$$\frac{L dI}{\mathcal{E} - IR} = dt$$

$$\frac{L}{-R} \ln(\mathcal{E} - IR) \Big|_0^t = t$$

$$\ln \frac{\mathcal{E} - IR}{\mathcal{E}} = -\frac{R}{L} t$$

$$\frac{\mathcal{E} - IR}{\mathcal{E}} = e^{-\frac{R}{L} t}$$
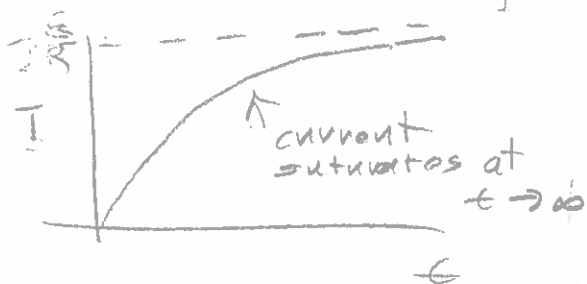
$$\mathcal{E} - IR = \mathcal{E} e^{-\left(\frac{R}{L}\right)t}$$



$$I = \frac{\mathcal{E}(1 - e^{-\left(\frac{R}{L}\right)t})}{R} = \frac{\mathcal{E}(1 - e^{-t/\tau_L})}{R}$$

0 at $t = 0$

$\frac{\mathcal{E}}{R}$ at $t = \infty$

$\tau_L = \frac{L}{R}$ is
the inductive time constant
or inductive e-folding time

When the current
is steady, the
inductor no longer
causes an emf


02-14022

14.6 More on Self-Inductance-

Ordinary circuit self inductance



Approximate as a circular loop.

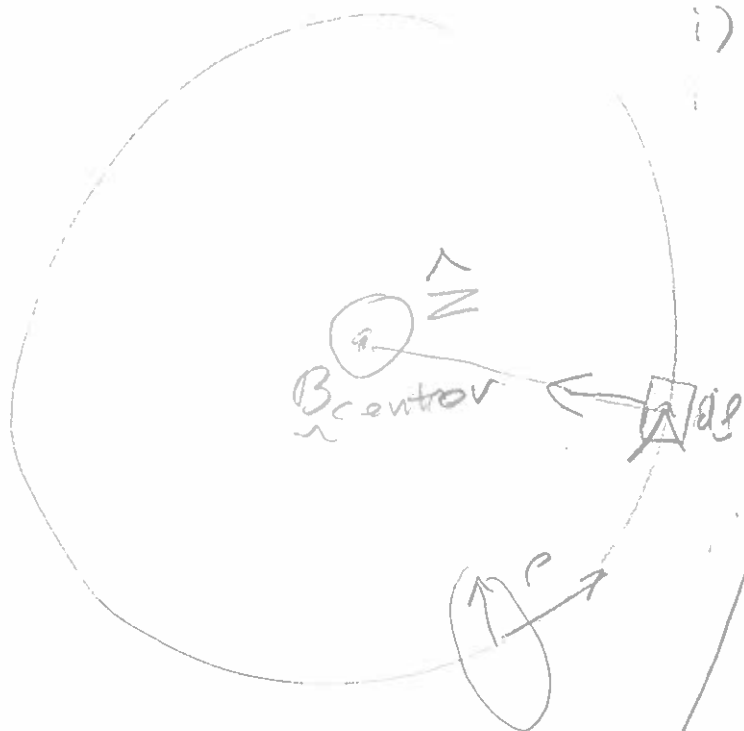

These two approximations suggest that in ordinary circuits

$$B \approx \frac{\mu_0 I}{r}$$

where r is of order loop size

Two approximations:

i) Biot Savart law (Text-502)

$$dB = \frac{\mu_0}{4\pi} \frac{Idl \times \underline{r}}{r^2}$$

So at center

$$B = \frac{\mu_0}{4\pi} \frac{I \cdot 2\pi r}{r^2} \hat{z}$$

$$B = \frac{\mu_0 I}{2r} \hat{z}$$

ii) Ampere's law for an infinite straight wire

$$\oint \underline{B} \cdot d\underline{l} = \mu_0 I_{\text{linked}} \quad (\text{Text-515})$$

$$B \cdot 2\pi r = \mu_0 I$$

$$B(r) = \frac{\mu_0 I}{2\pi r} \hat{z} \quad \text{in plane of loop}$$

$$B(r=r) = \frac{\mu_0 I}{2\pi r} \hat{z}$$

(2026 aug 01)

(02-14023)

$$\begin{aligned} \text{in } \Sigma &= - \frac{d}{dt} \int \underline{B} \cdot d\underline{A} \\ &= - \frac{d}{dt} \frac{\mu_0 I}{r_{\text{loop}}} A_{\text{loop}} \\ &= - \frac{\mu_0 A_{\text{loop}}}{r_{\text{loop}}} \frac{dI}{dt} = -L_{\text{loop}} \frac{dI}{dt} \\ L_{\text{loop}} &= \frac{\mu_0 A_{\text{loop}}}{r_{\text{loop}}} \end{aligned}$$

Now recall from p. 02-13003

$$\Sigma_{\text{ideal solenoid}} = -\mu_0 n^2 \ell \frac{dI}{dt}$$

$$\text{v. 1.0 } L_{\text{solenoid}} = \mu_0 n^2 \ell = \mu_0 \frac{N^2}{\ell^2} A \ell$$

$$= \frac{\mu_0 N^2 A_{\text{solenoid}}}{\ell_{\text{solenoid}}}$$

$$\text{Ratio} = \frac{L_{\text{solenoid}}}{L_{\text{loop}}} = \frac{N^2 A_s / \ell_s}{A_{\text{loop}} / r_{\text{loop}}}$$

For typical
values for
Solenoid from
Google AI- for
small inductors

$$\begin{aligned} &= \frac{(10^3)^2 \frac{(30\text{mm})^2}{30\text{mm}}}{1\text{m}^2 / 1\text{m}} = \frac{10^6 \cdot 0.03\text{m}}{1\text{m}} \\ &= \frac{10^6}{30} = 3 \times 10^4 \end{aligned}$$

02-14029


This ratio suggests to me that the self-inductance of wire loops in a circuit is negligible compared to ordinary inductors, and so probably negligible in general.

But if you are

doing high precision circuitry, you may have to worry about the self-inductance of wires.

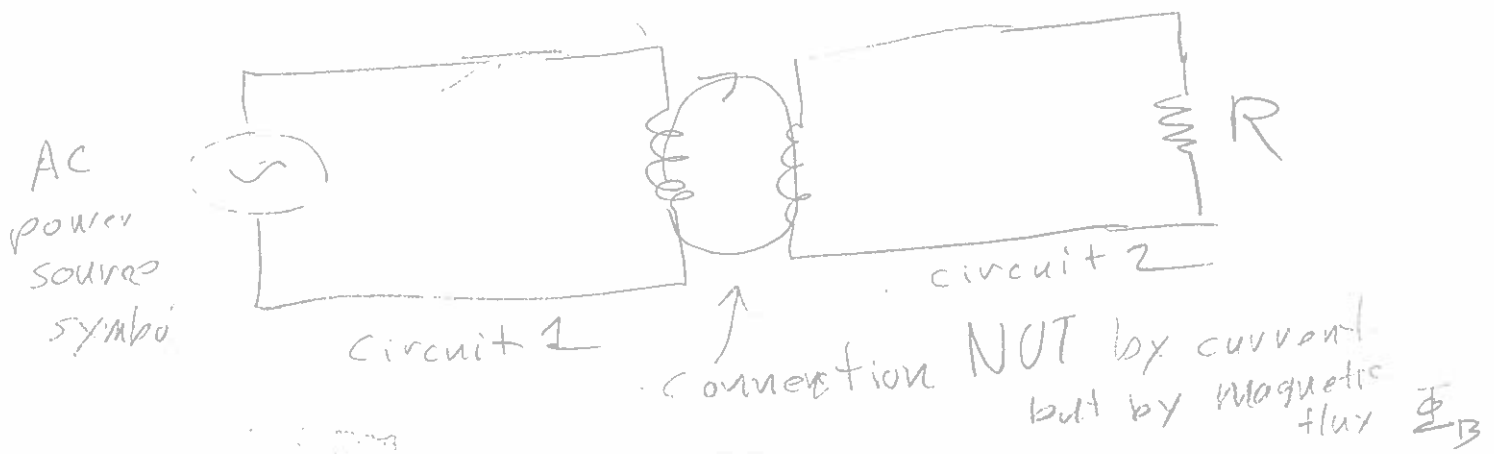14.7 Mutual Inductance M

Clearly, a B-field produced by one circuit can induce an emf in a second circuit



2026aug01

02-14079

Now for self-inductance

$$\mathcal{E} = - \frac{d\Phi_B}{dt} = - \frac{d}{dt} \int \vec{B} \cdot d\vec{A}$$

$$= - L \frac{di}{dt}$$

and

$$\text{and } \Phi_B = Li$$

Flux due
in a circuit
due to
current
in that circuit

Apparently, the
convention to use
small $i = i(t)$ for
alternating current

But one can also have

$$\mathcal{E}_2 = - \frac{d\Phi_{21}}{dt}$$

$$\Phi_{21 \text{ total}} = M_{21} i_1$$

$$\text{Where } \Phi_{21 \text{ total}} = N_2 \Phi_{21}$$

$$\therefore N_2 \Phi_{21} = M_{21} i_1$$

There is also flux
in circuit 1 due to
circuit 2.

$$\text{So } N_1 \Phi_{12} = M_{12} i_2$$

flux in a single turn
of a circuit 2
solenoid (or coil)
which we are assuming
is the device
of interest

Φ_{21} is Flux
in 2
due 1.

Apparently,
the conventional
order
for indices

D214026

Something beyond our scope to prove
(and Google AI gives a proof
using the vector potential of magnetism A)

is that $M_{12} = M_{21}$,

and so here we can
just use M for both.

$$\mathcal{E}_2 = - \frac{d}{dt} (M i_1)$$

$$\mathcal{E}_1 = - \frac{d}{dt} (M i_2)$$

and we will leave this story
(before it gets interesting)

until Chapter 15 on

alternating current (AC),

So far we have been mostly thinking
of DC (direct current)

except for our treatments of

oscillating LC and LRC circuits without drivers,